

LAB 5: CURRENT-VOLTAGE CHARACTERISTIC OF BIPOLAR JUNCTION TRANSISTOR (BJT)

1. Goals

- Understand the working principle of a BJT.
- Verify the current-voltage (V-A) characteristic of a BJT.
- Build up a switch circuit by using a BJT.

2. Exercises

Exercise 1. Investigate the current-voltage characteristic of a BJT (2N2222) in a Common-Emitter amplifier circuit as shown in Figure 1.

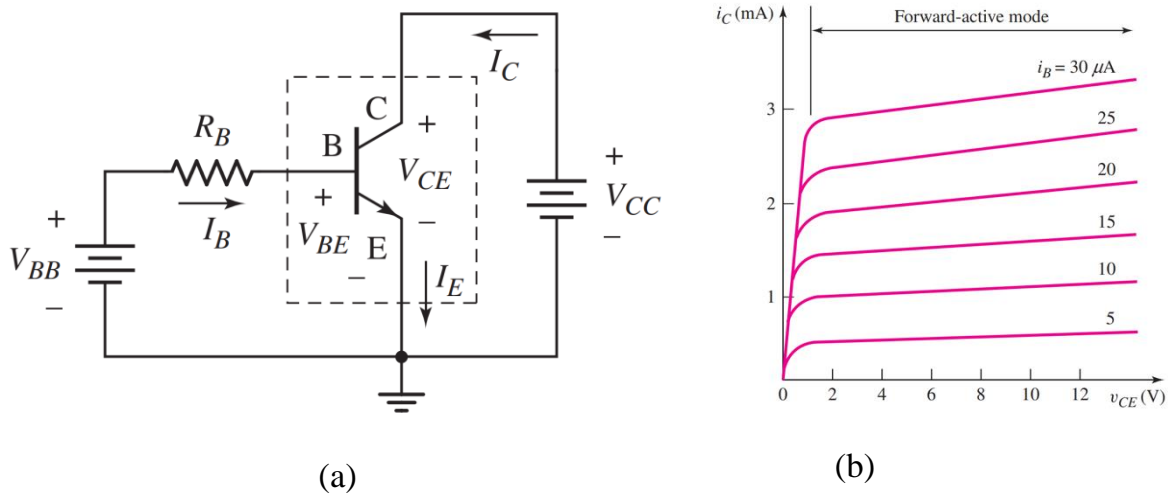


Figure 1. Common-Emitter amplifier circuit (a) and V-A characteristic of the BJT (b)

Requirements:

- Implement the circuit in Figure 1 with a resistor ($R_B = 94 \text{ k}\Omega$) and a transistor 2N2222. Use a DC power supply to provide V_{BB} (input voltage) = 3V, $V_{CC} = 10V$.
- Use a multimeter to measure the base current (I_B) and the collector current (I_C) of the transistor. Compute the *common emitter current gain*, $\beta = \frac{I_C}{I_B}$ of the transistor.
- Keep $V_{BB} = 3V$ so that I_B is unchanged, and then gradually reduce V_{CC} from 9V to 0V (e.g., 9V, 8V, ..., 1V, 0.9V, ..., 0.1V, 0V). For each value of V_{CC} , use a multimeter to measure I_C . Record the measured data.
- Repeat the above procedure with $V_{BB} = 5V$, $V_{BB} = 4V$, $V_{BB} = 2V$, and $V_{BB} = 1V$, respectively.
- Based on the measured data, plot the current-voltage characteristic of the transistor for each value of I_B (see Figure 1(b)). Write your comments on the current-voltage characteristic. Comment on the increase of I_C with respect to the increase of V_{CC} (note: $V_{CC} = V_{CE}$).

Exercise 2. Figure 2 shows a switch circuit. When there is no current flowing through the *Base* (i.e., $V_{IN} = 0$ and the transistor is in the cut-off mode), the *Collector* and *Emitter* are electrically isolated (i.e., like switching OFF), resulting in the LED OFF (because the circuit is open). When there is a small current flowing through the *Base* by increasing V_{IN} ($V_{IN} > V_{BE}$ (on)), the *Collector* and *Emitter* are electrically connected (i.e., like switching ON), resulting in the LED ON (because the circuit is closed).

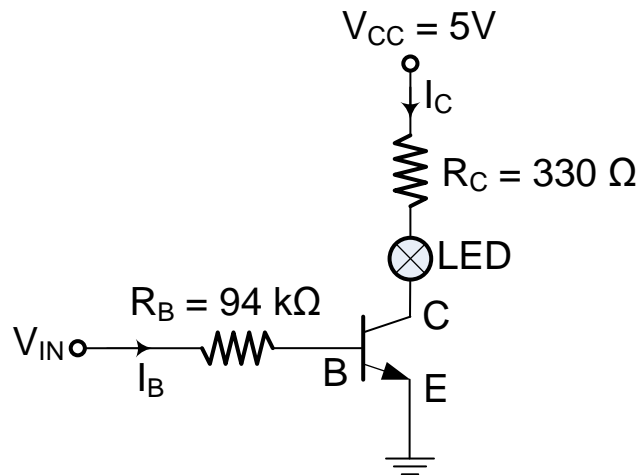



Figure 2. Switch circuit using a BJT.

Requirements:

- Implement the switch circuit in Figure 2 with $R_B = 94 \text{ k}\Omega$ and $R_C = 330 \Omega$. Use a DC power supply to provide the input voltage V_{IN} in the range of 0-10V (i.e., $V_{IN} = 0-10\text{V}$) and $V_{CC} = 5\text{V}$.
- Observe the status of the LED when $V_{IN} = 0\text{V}$ and when $V_{IN} > 0\text{V}$. Comment on the observation.
- Gradually increase V_{IN} from 0V to 10V and observe the brightness of the LED. Comment on the results.
- Use a multimeter to measure I_C (the current flows through R_C and the LED) with $V_{IN} = 1\text{V}$, $V_{IN} = 3\text{V}$, $V_{IN} = 5\text{V}$, $V_{IN} = 7\text{V}$, and $V_{IN} = 9\text{V}$, respectively. Record and explain the measured data.

Components and devices needed for the lab:

Components and Devices	Description	Amount
BJT	2N2222, 50V-1A	1
Resistor	330Ω / 47 or 50 $\text{k}\Omega$	1/2
DC power supply	Aditeg, 0-12V	1
Breadboard		1
Wire		few
Multimeter		1

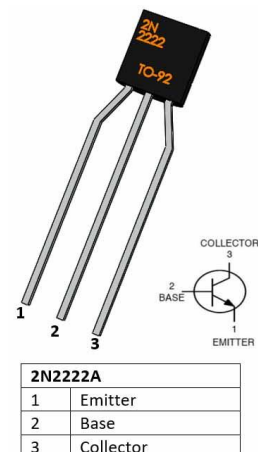

Exercise 1: I-V

V_{BB} (V)	V_{CC} (V)	I_C (mA)
5	9	
	8	
	7	
	6	
	5	
	4	
	3	
	2	
	1	
	0,5	
	0	
4	9	
	8	
	7	
	6	
	5	
	4	
	3	
	2	
	1	
	0,5	
	0	
3	9	
	8	
	7	
	6	
	5	
	4	
	3	
	2	
	1	
	0,5	
	0	
2	9	
	8	
	7	
	6	
	5	
	4	
	3	
	2	
	1	
	0,5	
	0	
1	9	
	8	
	7	
	6	
	5	
	4	
	3	
	2	
	1	
	0,5	
	0	

Exercise 2**LED observation**

V_{CC} (V)	V_{IN} (V)	LED observation
5	0	
	1	
	2	
	3	
	4	
	5	
	6	
	7	
	8	
	9	

 I_C Values

V_{CC} (V)	V_{IN} (V)	I_C (mA)
5	1	
	3	
	5	
	7	
	9	