



# HUST

**TRƯỜNG ĐẠI HỌC BÁCH KHOA HÀ NỘI**  
HANOI UNIVERSITY OF SCIENCE AND TECHNOLOGY

ONE LOVE. ONE FUTURE.



# **School of Electronics and Telecommunications**

## **Electronics Devices – ET2015E**

**ONE LOVE. ONE FUTURE.**



**TRƯỜNG ĐẠI HỌC  
BÁCH KHOA HÀ NỘI**  
HANOI UNIVERSITY  
OF SCIENCE AND TECHNOLOGY

# Chapter 4. Digital logics

**Tutor:** Assoc. Prof. Nguyen Tien Dzung

**Department:** Electronics and Computer Engineering

**Email:** [tiendungbk@gmail.com](mailto:tiendungbk@gmail.com); [dzung.nguyentien@hust.edu.vn](mailto:dzung.nguyentien@hust.edu.vn)

**Mobile:** 0988.355.343

**Office:** 94 Le Thanh Nghi, R102, C-Bulding (Tại chức)

ONE LOVE. ONE FUTURE.

- 4.1. Fundamentals of a logic algebra: number systems, logic variable and logic functions, Boolean algebra and properties**
- 4.2. Representation of a logic function: truth table, logic function expression, Karnaugh table**
- 4.3. Basic logical gates: AND, OR, NOT, NAND, NOR, XOR**
- 4.4. Minimization of a logic function: algebraic method, K-table based method**
- 4.5. Implementation of a logic function using logic gates: OR-AND, AND-OR, NAND-NAND, NOR-NOR**
- 4.6. Some typical logic applications**

## 4.1. Fundamentals of a logic algebra

### 1. Numeral system:

a) Base or radix of a number system:  $X_{10} = \sum_{i=0}^{n-1} a_i d^i$ , where  $d^i$  is weighting

✓ **Decimal**:  $d = 10$ ; digits  $a_i = 0$  to  $9$  – well-known number system

✓ **Binary**:  $d = 2$ ; digits  $a_i = 0, 1$  or bits or FALSE/TRUE

✓ **Hexadecimal**:  $d = 16$ , digits  $a_i = 0$  to  $9$  + letters A, B, C, D, E, F

✓ **Octal**:  $d = 8$ , digits  $a_i = 0$  to  $7$

b) Conversion between number system:

✓ 2 to 10:  $1101_2 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 8 + 4 + 0 + 1 = 13_{10}$ , ( $2^i$  – weighting)

✓ 10 to 2:  $13_{10} = 8 + 4 + 0 + 1 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 1101_2$

✓ **Example**:  $14_{10} = X_2$  ?  $113_{10} = X_2$  ?

c) Binary numeral system and Boolean algebra:

✓ Boolean algebra: Logical operations with bits

✓ Logical constant, variable, function: take values in set  $\{0, 1\}$  (e.g. A,  $F(A, B)$ )

✓ Basic logical functions: **AND** (A AND B or  $F = A.B$ ), **OR** (A OR B or  $F = A+B$ ), **NOT** (or  $F = \bar{A}$ )

## 4.1. Fundamentals of a logic algebra (cont.)

### d) Properties of Boolean algebra

#### ✓ Relation between logic constants:

- AND:  $0.0 = 0$ ,  $0.1 = 0$ ,  $1.0 = 0$ ,  $1.1 = 1$
- OR:  $0+0 = 0$ ,  $0+1 = 1$ ,  $1+0 = 1$ ,  $1+1 = 1$
- NOT:  $\bar{0} = 1$ ,  $\bar{1} = 0$

#### ✓ Relation between logic variables: assuming variables A, B, C ...

- AND:  $0.A = 0$ ,  $A.0 = 0$ ,  $A.1 = A$ ,  $1.A = A$
- OR:  $0+A = A$ ,  $A+0 = A$ ,  $1+A = 1$ ,  $A+1 = 1$ ,
- Involution:  $\bar{\bar{A}} = A$
- Idempotence:  $A.A = A$ ,  $A + A = A$
- Complement:  $\bar{A} + A = 1$ ,  $\bar{A}.A = 0$
- Association:  $A.B + A.C = A(B+C)$ ,  $A + B + C = (A + B) + C = A + (B + C)$
- Distribution:  $A(B+C) = A.B + A.C$

#### ✓ Useful relations:

- $A.(B + \bar{B}) = A.1 = A$ ;  $A.(\bar{A} + B) = A.\bar{A} + A.B = 0 + A.B = A.B$ ;  $A.(A + B) = AB$ ;  $A + A.B = B$ ;

## 4.1. Fundamentals of a logic algebra (cont.)

✓ De Morgan theorem: Applying for multiple variables

- $\overline{A \cdot B} = \bar{A} + \bar{B}$  ;  $\overline{A + B} = \bar{A} \cdot \bar{B}$
- AND  $\Leftrightarrow$  OR, variable  $\Leftrightarrow$  negated variable

✓ **Example:**

- $\overline{A(B + C)} = A + \overline{\overline{B + C}} = A + B + C$
- $\overline{(A + B)(B + C)(A + C)} = \overline{A + B} + \overline{B + C} + \overline{A + C} = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C}$
- $\overline{\bar{A}(B + C)} = \bar{\bar{A}} + \overline{\overline{B + C}} = A + B + C$
- $\overline{\overline{A\bar{B}} + \overline{A\bar{B}}} = ?$
- $\overline{\overline{\bar{A}\bar{B}C} + \overline{B\bar{C}}} = ?$
- $\overline{(A\bar{B} + \bar{A}B) \cdot \bar{B}(\bar{A}CD + \bar{A}C\bar{D})} = ?$

## 4.2. Representation of a logic function

### Truth table, Logic expression, Karnaugh table

a) **True table:** list all  $2^n$  variable combination of a n-variable function and corresponding outputs

- ✓  $n = 2$ : possible  $2^2 = 4$  variable combinations =  $\bar{A}\bar{B}$ ,  $\bar{A}B$ ,  $A\bar{B}$ ,  $AB$  corresponding to 00, 01, 10, 11 – logical combinations
- ✓  $n = 3$ : possible  $2^3 = 8$  variable combinations =  $\bar{A}\bar{B}\bar{C}$ ,  $\bar{A}\bar{B}C$ ,  $\bar{A}B\bar{C}$ ,  $\bar{A}BC$ ,  $A\bar{B}\bar{C}$ ,  $A\bar{B}C$ ,  $AB\bar{C}$ ,  $ABC$  - 000, 001, 010, 011, 100, 101, 110, 111

- ✓  $n = 4$ : possible  $2^4 = 16$  variable combinations

	A	B	F
$\bar{A}\bar{B}$ : 00 $\Rightarrow$ 0	0	0	1
$\bar{A}B$ : 01 $\Rightarrow$ 1	0	1	1
$A\bar{B}$ : 10 $\Rightarrow$ 2	1	0	0
$AB$ : 11 $\Rightarrow$ 3	1	1	0

$$\Rightarrow F = \bar{A}\bar{B} + \bar{A}B$$

$\bar{A}\bar{B}\bar{C}$ : 000  $\Rightarrow$  0  
 $\bar{A}\bar{B}C$ : 001  $\Rightarrow$  1  
 $\bar{A}B\bar{C}$ : 010  $\Rightarrow$  2  
 $\bar{A}BC$ : 011  $\Rightarrow$  3  
 $A\bar{B}\bar{C}$ : 100  $\Rightarrow$  4  
 $A\bar{B}C$ : 101  $\Rightarrow$  5  
 $AB\bar{C}$ : 110  $\Rightarrow$  6  
 $ABC$ : 111  $\Rightarrow$  7

$$\Rightarrow F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1

$$\Rightarrow F = ?$$

A	B	C	D	F
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

- ✓ Question: 1) If function F is given. Show the True table. 2) If  $F = A + BC$ , show its true table. 3) Show  $\bar{F}$



## 4.2. Representation of a logic function (cont.)

### b) Logic expression: canonical form vs non-canonical form

- ✓ Sum of Product (SoP): sum of minterm  $m_i$ , where  $i$  is the order of the corresponding variable combination
  - Example:  $F = \overline{A}\overline{B} + \overline{A}B = m_0 + m_1$  or  $F = \{m_0, m_1\}$ ;  $F = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}\overline{C} + A\overline{B}C = m_0 + m_1 + m_6 + m_7$  or  $F = \{m_0, m_1, m_6, m_7\}$
  - Question:
    - 1) If  $F = \{m_1, m_3, m_5, m_7, m_8, m_{10}, m_{12}, m_{14}\}$ , show the canonical form of  $F$  and Truth table
    - 2) If  $F = A + BC$  show the canonical SoP of  $F$  and its Truth table
- ✓ Product of Sum (PoS): Product of maxterm  $M_i$ , where  $m_i = \overline{M_i}$  or  $M_i = \overline{m_i}$ 
  - ✓ Example:  $F = M_0M_1 = \overline{m_0} \cdot \overline{m_1} = \overline{\overline{A}\overline{B}} \cdot \overline{\overline{A}B} = (A + B) \cdot (A + \overline{B}) \rightarrow M_0 = A + B, M_1 = A + \overline{B}$
  - ✓ Question:
    - 1) If canonical SoP of  $F = \{m_0, m_1, m_6, m_7\}$ , show its canonical PoS
    - 2) If  $F = (A + B)(B + C)(A + C)$ , determine the canonical PoS of  $F$
- ✓ Non-canonical form: OR-AND or AND-OR  $\rightarrow$  convert to canonical form
  - ✓ Question:
    - 1)  $F = A + BC \rightarrow$  SoP? PoS?
    - 2)  $F = (A + B)(B + C)(A + C) \rightarrow$  SoP, PoS?
    - 3)  $F = (\overline{A}\overline{B} + \overline{A}B) \overline{B}(\overline{A}CD + \overline{A}\overline{C}D) \rightarrow$  SoP, PoS?

## 4.2. Representation of a logic function (cont.)

- c) **Karnaugh table**: arrange minterms in array where number of cells is  $2^n$  for n-variable function  
 ✓ Karnaugh table of logic variables: **gray code** and **neighborhood property**

A \ B	0	1	
	$\bar{B}$	B	
0	m <sub>0</sub>	m <sub>1</sub>	$\bar{A}$
1	m <sub>2</sub>	m <sub>3</sub>	A

$$\bar{A} = m_0 + m_1 = \bar{A}\bar{B} + \bar{A}B$$

$$A = m_2 + m_3 = A\bar{B} + AB$$

$$\bar{B} = m_0 + m_2 = \bar{A}\bar{B} + A\bar{B}$$

$$B = m_1 + m_3 = \bar{A}B + AB$$

A \ BC	$\bar{C}$ 00	C 01	$\bar{C}$ 11	C 10	
	$\bar{B}$	B	$\bar{B}$	B	
0	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>	$\bar{A}$
1	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>	A

$$\bar{A} = m_0 + m_1 + m_3 + m_2 = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC$$

$$A = m_4 + m_5 + m_7 + m_6 = A\bar{B}\bar{C} + A\bar{B}C + ABC + AB\bar{C}$$

$$\bar{B} = m_0 + m_2 + m_4 + m_6 = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C$$

$$B = m_1 + m_3 + m_5 + m_7 = \bar{A}B\bar{C} + \bar{A}BC + AB\bar{C} + ABC$$

$$BC = m_3 + m_7 = \bar{A}BC + ABC = BC$$

$$AC = m_5 + m_7 = A\bar{B}C + ABC = AC$$

$$\bar{A}\bar{B} = m_0 + m_2 = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C = \bar{A}\bar{B}$$

AB \ CD	$\bar{D}$ 00	D 01	$\bar{D}$ 11	D 10	
	$\bar{C}$	C	$\bar{C}$	C	
$\bar{B}$ 00	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>	$\bar{A}$
01	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>	$\bar{A}$
B 11	m <sub>12</sub>	m <sub>13</sub>	m <sub>15</sub>	m <sub>14</sub>	A
$\bar{B}$ 10	m <sub>8</sub>	m <sub>9</sub>	m <sub>11</sub>	m <sub>10</sub>	A

$$A = ? \quad B = ? \quad C = ? \quad D = ?$$

$$AB = ? \quad BD = ? \quad BC = ? \quad AD = ?$$

$$A\bar{B} = ? \quad \bar{B}D = ? \quad B\bar{C} = ? \quad \bar{A}\bar{D} = ?$$

$$ABC = ? \quad A\bar{B}D = ? \quad B\bar{C}D = ? \quad \bar{A}B\bar{D} = ?$$

$$\bar{A}\bar{B}D = ? \quad \bar{B}\bar{C}D = ? \quad A\bar{C}D = ? \quad \bar{B}C\bar{D} = ?$$

## 4.2. Representation of a logic function (cont.)

✓ Karnaugh table of logic function:

- Convert the logic function just to OR-AND form
- Determine the number of logic variables and show the Karnaugh table
- Fill 1's in Karnaugh table in the cells corresponding to each product in OR-AND form
- Other cells will be filled by 0's
- Karnaugh table is ready

▪ Example:

$$F = A + B$$

F	A	0	1	
0	0	1		$\bar{A}$
1	1	1		A
		$\bar{B}$	B	

$$F = \bar{A}B + BC + AC$$

F	BC A	$\bar{C}$		C		$\bar{A}$
		00	01	11	10	
0	0	0	0	1	1	A
1	0	0	1	1	0	
		$\bar{B}$		B		

$$F = A + \bar{B}C$$

F	A \ BC	$\bar{C}$ 00	01	11	$\bar{C}$ 10	
0	0	1	0	0	$\bar{A}$	
1	1	1	1	1	A	
		$\bar{B}$	B			

$$F = (A + B)(B + C)(A + C)$$

$$\bar{F} = \overline{(A + B)(B + C)(A + C)} = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C}$$

Hint: Karnaugh table of  $\bar{F}$ , then  $\rightarrow F$

$\overline{F}$	$\overline{C}$	$C$	$\overline{C}$	
$\overline{A}$	00	01	11	10
0				
1				
	$\overline{B}$	$B$		

F	<b>BC</b> <b>A</b>	$\overline{C}$		C		$\overline{C}$
		00	01	11	10	
0						$\overline{A}$
1						A
		$\overline{B}$		B		

▪ Question:

- 1) Determine Karnaugh table of  $\bar{F}$
- 2) Determine canonical form of  $\bar{F}$

## 4.2. Representation of a logic function (cont.)

- Question:** Determine Karnaugh tables of the following logic functions

$$F = A + \bar{B}C + \bar{A}B\bar{D} + A\bar{B}C\bar{D}$$

$$F = \overline{(A + \bar{B})(B + \bar{C})(C + \bar{D})(\bar{A} + D)}$$

$$F = \overline{(\bar{A}\bar{B} + \bar{A}B)\bar{B}(\bar{A}CD + \bar{A}C\bar{D})}$$

F	CD				
	$\bar{D}$ 00	01	11	$\bar{D}$ 10	
AB	$\bar{B}$ 00				$\bar{A}$
	01				
	B 11				A
	$\bar{B}$ 10				
		$\bar{C}$	C		

F	CD				
	$\bar{D}$ 00	01	11	$\bar{D}$ 10	
AB	$\bar{B}$ 00				$\bar{A}$
	01				
	B 11				A
	$\bar{B}$ 10				
		$\bar{C}$	C		


F	CD				
	$\bar{D}$ 00	01	11	$\bar{D}$ 10	
AB	$\bar{B}$ 00				$\bar{A}$
	01				
	B 11				A
	$\bar{B}$ 10				
		$\bar{C}$	C		

## 4.3. Basic logical gates

### a. Example for 2-input:


✓ AND:  $F = AB$

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

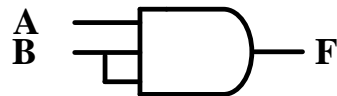


✓ OR:  $F = A + B$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

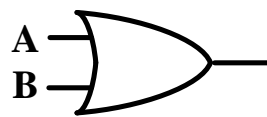



✓ NOT:  $F = \bar{A}$

A	F
0	1
1	0

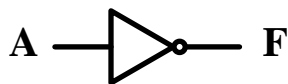


✓ NAND:  $F = \overline{A \cdot B}$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

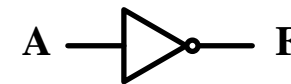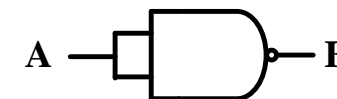

✓ NOR:  $F = \overline{A + B}$

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

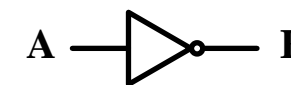

✓ XOR:  $F = A\bar{B} + \bar{A}B$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0



**Question:** 1) Implement function  $F = \overline{A \cdot B \cdot C}$  using 2-input NAND gates

**Question:** 2) Implement function  $F = \overline{A + B + C}$  using 2-input NOR gates

## 4.4. Minimization of a logic function

### 4. Minimization of logic function

a. Type of logic function expression: utilization in function implementation using desired gates

✓ OR-AND:  $F = \overline{A}B + BC + AC = X + Y + Z$

✓ AND-OR:  $F = (A + B)(B + C)(A + C) = X.Y.Z$

✓ NAND-NAND:  $F = \overline{\overline{A}B} \cdot \overline{BC} \cdot \overline{AC} = \overline{X.Y.Z}$

✓ NOR-NOR:  $F = \overline{\overline{A + B} + \overline{B + C} + \overline{A + C}} = \overline{X + Y + Z}$

b. Optimization concept

✓ Output optimization in OR-AND form

✓ Fewest number of products in the OR-AND form

✓ Fewest number of variables/negated variables in each product above

✓ Optimization methods:

- Algebraic method: Utilization of Boolean algebra to minimize a logic function, but not guaranteed
- Karnaugh-table based method: Obvious and intuitive minimization of a logic function

## 4.4. Minimization of a logic function (cont.)

### a. Algebraic optimization method:

✓ Utilization of properties in Boolean algebra and flexible use of De Morgan theorem

✓ Example:

- $F = A\bar{B}C + A\bar{B}\bar{C} = A\bar{B}(C + \bar{C}) = A\bar{B}$
- $F = A(BC + \bar{B}\bar{C}) + A(\overline{BC + \bar{B}\bar{C}}) = A((BC + \bar{B}\bar{C}) + (\overline{BC + \bar{B}\bar{C}})) = A$
- $F = A\bar{B} + A\bar{B}CD(\overline{A\bar{B}} + \overline{BD}) = A\bar{B}(1 + CD[\overline{A\bar{B}} + \overline{BD}]) = A\bar{B}$

### b. Karnaugh-table based method: Follow the following steps

- **Step 1:** Represent logic function F in Karnaugh table (KT)
- **Step 2:** Group  $2^k$  neighbor cells containing 1's following the rules (of course, always there is exception!)
  - Group size as largest as possible
  - Groups must not be nested
  - All 1's cells in KT must be included in a group
  - 1's cells may be re-used in grouping, however these cells must be included in different groups
- **Step 3:** Assign each group to the corresponding product of variable/negated variables
- **Step 4:** The minimization function is an OR-AND form of the products above
- **Notes:** The corner cells are neighbors; the end-most cells in a row or a column are also neighbors.

## 4.4. Minimization of a logic function (cont.)

### Example:

Diagram 1: Karnaugh map for function F with variables A, B, and  $\bar{A}$ .

	$\bar{B}$	B
$\bar{A}$	1	0
A	1	1

Diagram 2: Karnaugh map for function F with variables A, B, and  $\bar{B}$ .

	$\bar{C}$	C
$\bar{A}$	0	1
A	1	0

Diagram 3: Karnaugh map for function F with variables A, B, and  $\bar{C}$ .

	$\bar{D}$	D
$\bar{A}$	1	0
A	1	1

Diagram 4: Karnaugh map for function F with variables A, B, and  $\bar{D}$ .

	$\bar{D}$	D
$\bar{A}$	1	0
A	1	1

Diagram 5: Karnaugh map for function F with variables A, B, and  $\bar{D}$ .

	$\bar{D}$	D
$\bar{A}$	1	0
A	1	1

Diagram 6: Karnaugh map for function F with variables A, B, and  $\bar{B}$ .

	$\bar{C}$	C
$\bar{A}$	1	1
A	1	1

Diagram 7: Karnaugh map for function F with variables A, B, and  $\bar{B}$ .

	$\bar{C}$	C
$\bar{A}$	0	1
A	1	1

Diagram 8: Karnaugh map for function F with variables A, B, and  $\bar{C}$ .

	$\bar{D}$	D
$\bar{A}$	0	1
A	1	1

Diagram 9: Karnaugh map for function F with variables A, B, and  $\bar{D}$ .

	$\bar{D}$	D
$\bar{A}$	1	0
A	1	1

Diagram 10: Karnaugh map for function F with variables A, B, and  $\bar{D}$ .


	$\bar{D}$	D
$\bar{A}$	1	0
A	1	1




## 4.5. Implementation of a logic function using logic gates

a. OR-AND expression form: Typical output from minimization process


$$F = AB + \bar{A}\bar{B}$$

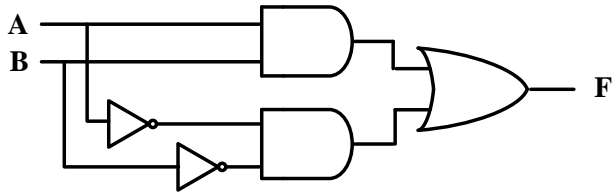
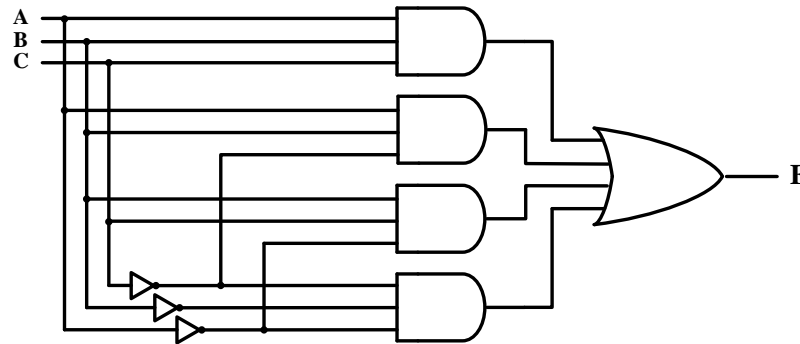
$$F = ABC + \bar{A}\bar{B}\bar{C} + AB\bar{C} + \bar{A}BC$$



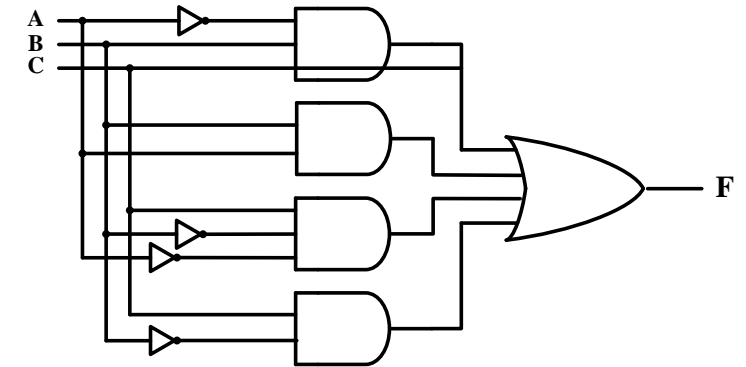
$$F = \bar{A}BC + AB + \bar{A}\bar{B}C + B\bar{C}$$




b. AND-OR expression:

$$F = (A + B)(\bar{A} + \bar{B})$$

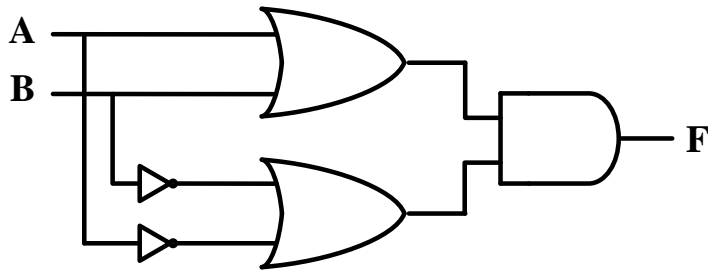

$$F = (A + B)(B + C)(A + C)$$


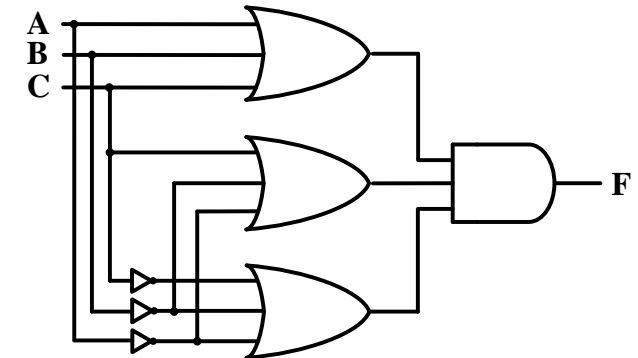


## 4.5. Implementation of a logic function using logic gates (cont.)

c. **NAND-NAND expression:** Derive to OR-AND expression and apply De Morgan to get NAND-NAND form

$$\text{OR - AND: } F = \bar{A}B + \bar{B}C + A\bar{C} = \overline{\overline{\bar{A}B + \bar{B}C + A\bar{C}}} = \overline{\bar{A}B \cdot \bar{B}C \cdot A\bar{C}}$$

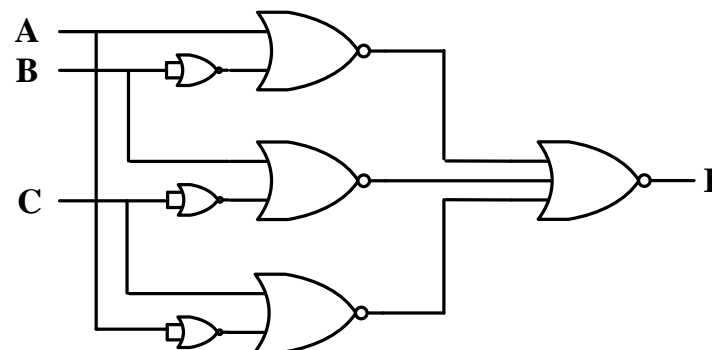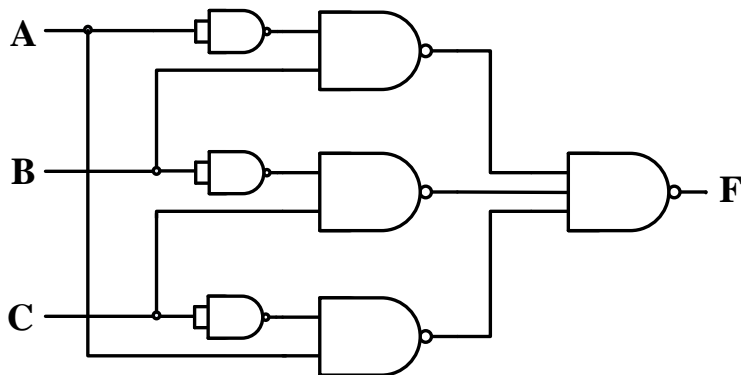**Question:** Implement function F using NOR gate



d. **NOR-NOR expression:** Derive OR-AND of  $\bar{F}$ .

Take negation of  $\bar{F}$  to get  $\bar{\bar{F}} = F$ , and apply De Morgan 1<sup>st</sup> time. Take involution of F to result  $\bar{\bar{F}}$  and apply De Morgan 2<sup>nd</sup> time for first negation to get NOR-NOR form

$$\text{OR - AND of } \bar{F} = \bar{A}B + \bar{B}C + A\bar{C}$$







$$\text{Negation of } \bar{F} \Rightarrow \bar{\bar{F}} = F = \overline{\bar{A}B + \bar{B}C + A\bar{C}} = \overline{\bar{A}B} \cdot \overline{\bar{B}C} \cdot \overline{A\bar{C}} = (A + \bar{B})(B + \bar{C})(\bar{A} + C)$$

$$\text{Involution of } F \Rightarrow \bar{\bar{F}} = F = \overline{(A + \bar{B})(B + \bar{C})(\bar{A} + C)} = \overline{A + \bar{B}} + \overline{B + \bar{C}} + \overline{\bar{A} + C}$$

**Question:** Implement function  $F_{\text{NOR-NOR}}$  using 2-input NOR gates only

## 4.5. Implementation of a logic function using logic gates (cont.)

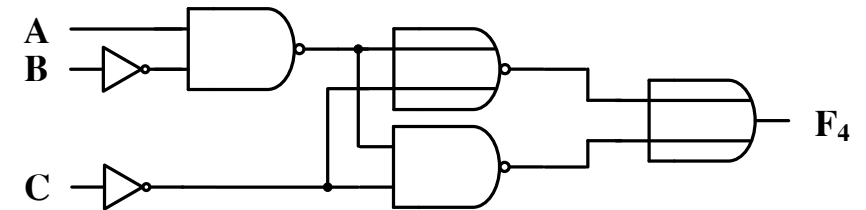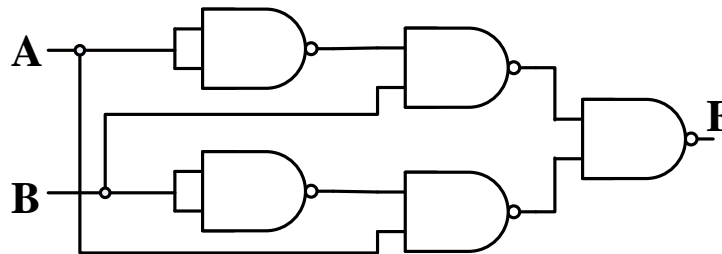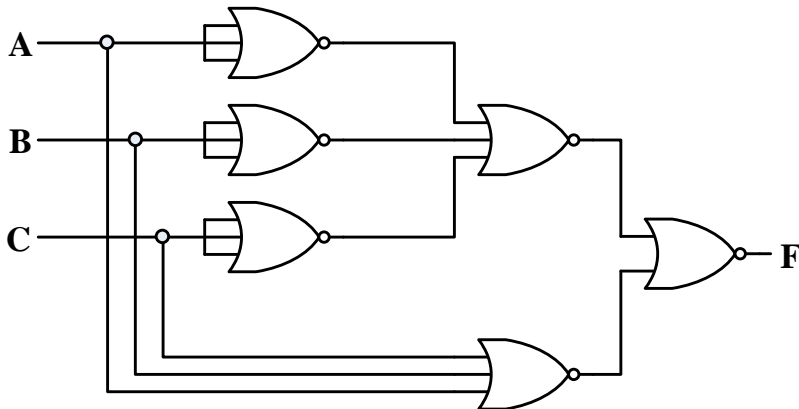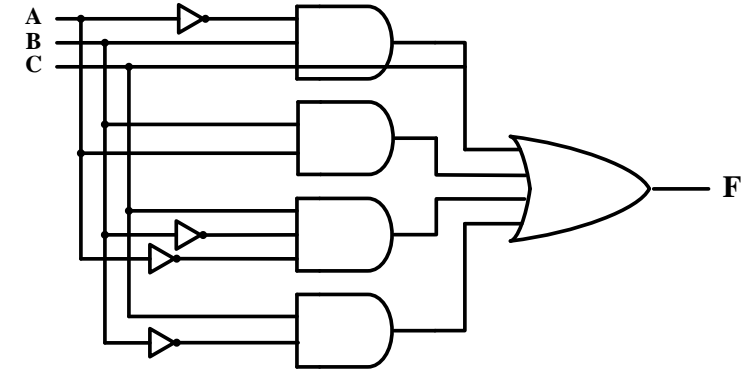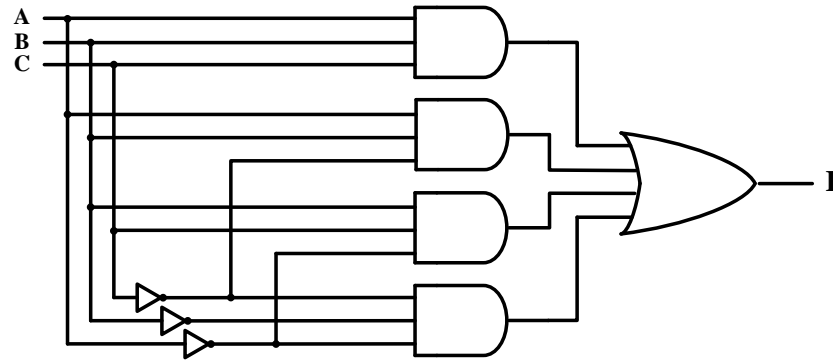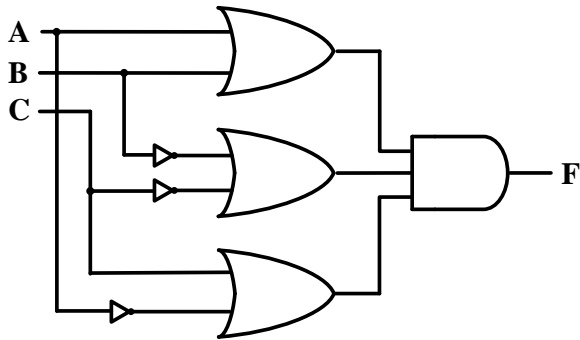- **Example:** Determine logic function of the following logic circuits




## 4.6. Some typical logic applications

### a. One-bit half adder: Determine Truth table

- $a_i, b_i$  : i-th bits of binary numbers A and B to be added
- $S_i$ : Sum bit, adding bits  $a_i$  and  $b_i$
- $C_i$ : carry bit

$$S_i = \bar{a}_i b_i + a_i \bar{b}_i$$

$$C_i = a_i b_i$$

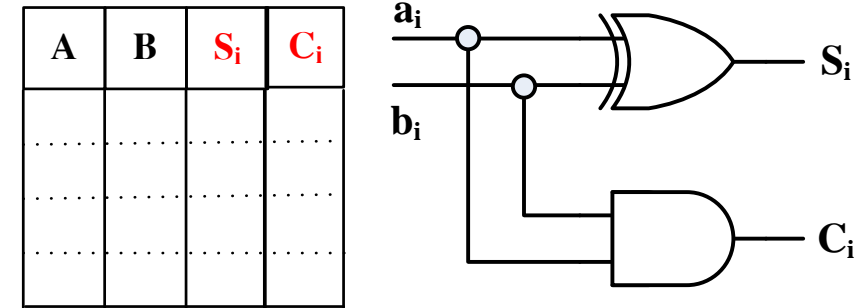


### b. One-bit full adder: Determine Truth table

$S_i =$

$C_i =$

$a_i$	$b_i$	$C_{i-1}$	$S_i$	$C_i$

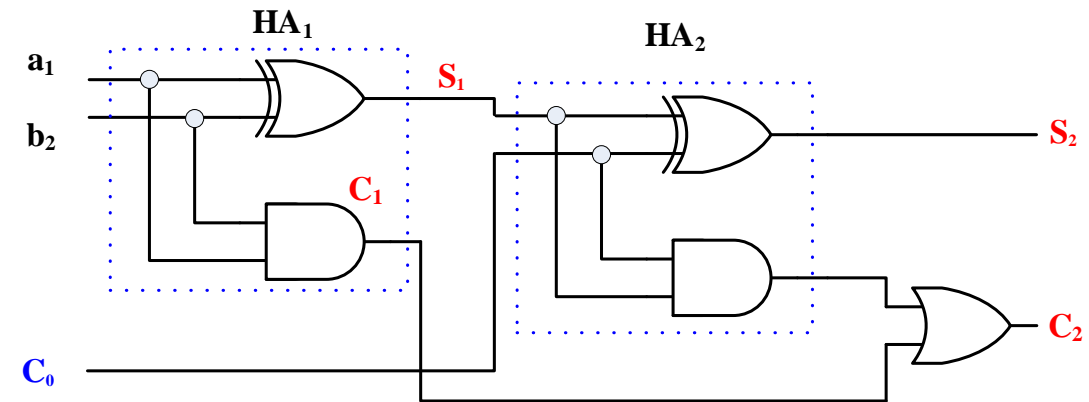

## 4.6. Some typical logic applications

- a. Comparator: Compare two binary number
- b. Binary Coded Decimal (BCD): encode numbers 0-9 to corresponding binary outputs
- c. 7-segment coder: encode number 0-9 to monitor in led-segments
- d. Carry-Look-Ahead adder (CLA): Fast implementation of an n-bit adder

A large, stylized graphic of the letters 'HUST' in white, centered within a circular pattern of red dots of varying sizes on a dark red background.

# HUST



[hust.edu.vn](http://hust.edu.vn)



[fb.com/dhbkhn](https://fb.com/dhbkhn)





**HUST**

**THANK YOU !**