


## LAB 10: 1-BIT FULL ADDER

### 1. Goals

- Know how to use basic logic gates.
- Build an *Exclusive OR* (XOR) using NAND and OR gates.
- Build a 1-bit full adder using NAND, OR and XOR gates.

### 2. Exercises

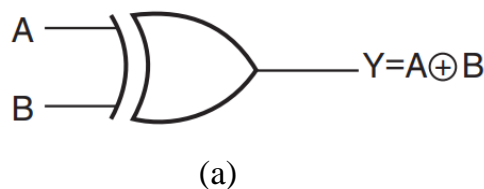**Exercise 1.** Build a XOR gate using AND, OR and NOT gates. The symbol and truth table of a XOR gate are shown in Figure 1.



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

(b)

Figure 1. Symbol (a) and truth table (b) of XOR.

### Requirements:

- Test all ICs and equipment.
- Assemble a XOR gate on a breadboard using IC 74LS00 (AND), 74LS32(OR), 74LS04 (NOT), resistors, LEDs, and buttons (or switches).
- Supply 5V/GND power to the circuit.
- Use a function generator and an oscilloscope to define the circuit's activities, i.e., checking circuit's output for all input states.
- Write comments on the experimental results.

**Exercise 2.** Build a 1-bit full adder using basic logic gates. Figure 2 shows the block diagram of a 1-bit full adder:

- 3 1-bit inputs: A, B,  $C_{in}$
- 2 1-bit output: S,  $C_{out}$

From the truth table, the Boolean expressions of the SUM and CARRY outputs are:

- $S = A \oplus B \oplus C_{in}$
- $C_{out} = A \cdot B + (C_{in} \cdot (A \oplus B))$

### Requirements:

- Test all ICs and equipment.
- Assemble a full adder on a breadboard using the given ICs (74LS00, 74LS32, and 74LS86), resistors, LEDs, and buttons (or switches).
- Supply 5V/GND power to the circuit.
- Use a function generator and an oscilloscope to define the circuit's activities, i.e., checking circuit's output for all input states.
- Write comments on the experimental results.


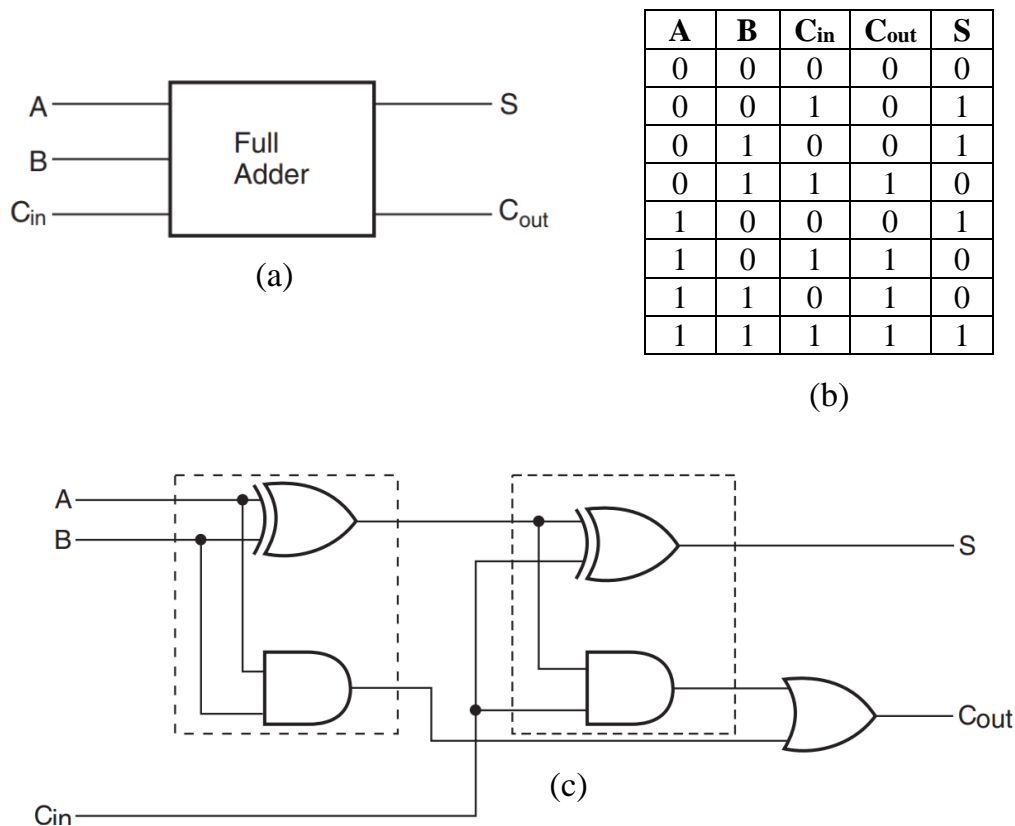


Figure 2. Block diagram (a), truth table (b) and logic diagram (c) of 1-bit FA.

### Components and devices needed for the lab:

Components and Devices	Description	Amount
74LS (or HC) 08/32/04/86	AND/OR/NOT/XOR	2/2/1/1
Resistor	330 $\Omega$ /10 k $\Omega$	Few
LED	2V-2.5V, 20mA	5
Switch or Button	3-pin/4-pin	3
Power Supply	Aditeg PS-3030DD	1
Breadboard		1
Connecting Wires		Few
Multimeter/function generator/oscilloscope		1/1/1

Datasheet of 74LS08 [here](#).

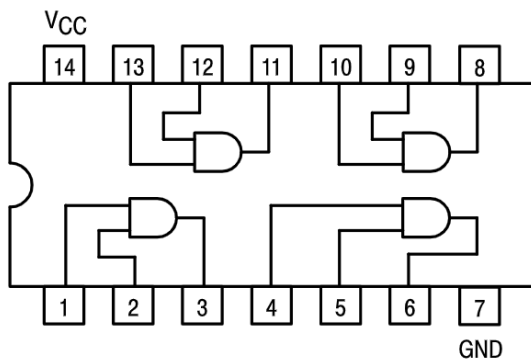


**74LS08 Pinout**

A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1




Datasheet of 74LS32 [here](#).

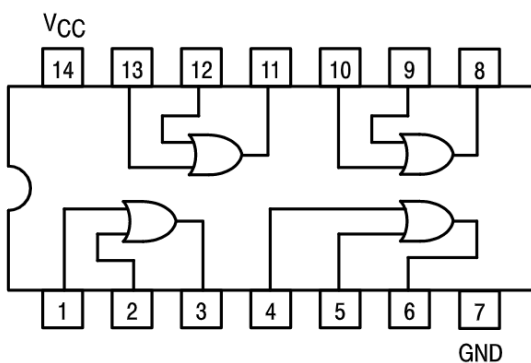


**74LS32 Pinout**

A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1

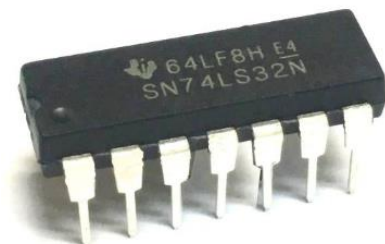

Datasheet of 74LS86 [here](#).

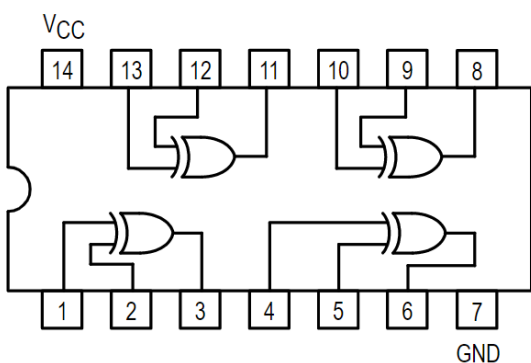


**74LS86 Pinout**

A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0



Datasheet of 74LS04 [here](#).

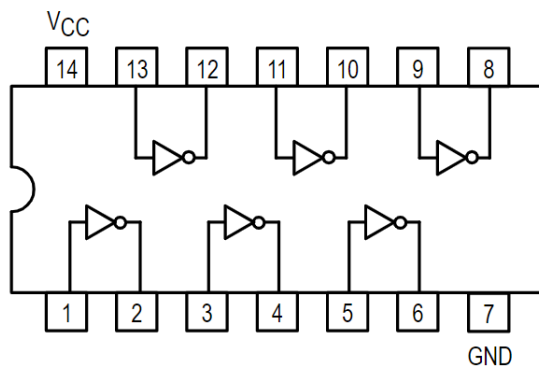

**74LS04 Pinout**

A	$\bar{A}$
0	0
0	1
1	1
1	0

