

School of Electronics and Telecommunications

Electronics Devices – ET2015E

Tutor: Assoc. Prof. Nguyen Tien Dzung

Department: Electronics and Computer Engineering


Email: tiendungbk@gmail.com; dzung.nguyentien@hust.edu.vn

Mobile: 0988.355.343

Office: 94 Le Thanh Nghi, R102, C-Bulding (Tàì chức)


Sources: + Independent: $\begin{cases} U \\ I \end{cases}$ | Ideal
 + Dependent: $\begin{cases} U \\ I \end{cases}$ | Real

Ideal Voltage Source

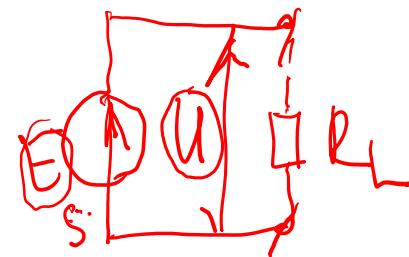

$$U = E_S$$

Real voltage source

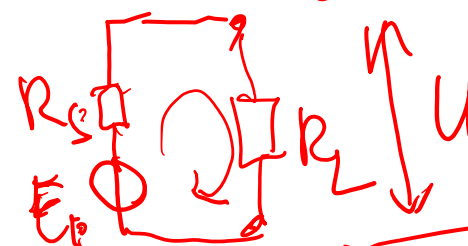

$$U = E_S \cdot \frac{R_L}{R_S + R_L}$$


\downarrow
0

$[R_S \approx \text{small}]$

$$1 + \frac{R_L}{R_S} \rightarrow \infty$$

$[R_S \approx \text{large}]$

Ideal Current Source

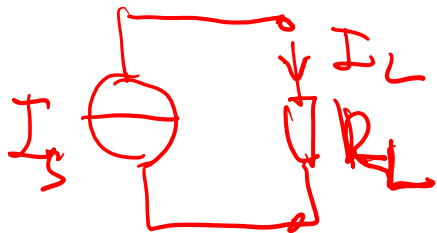


$$I_L = I_S$$

$$U_L = U_1$$

$$I_L = I_1$$

Real current source:

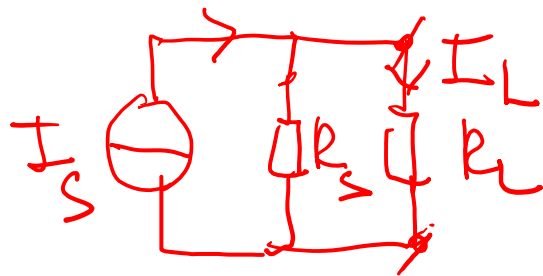

$$I_L = I_S \cdot \frac{R_S}{R_S + R_L}$$

$$= I_S \cdot \frac{1}{1 + \frac{R_L}{R_S}}$$

$$I_S$$

$$1$$

$$1 + \frac{R_L}{R_S}$$

$$\rightarrow 0$$

$$\rightarrow \infty$$

Chapter 2. Semiconductor Devices

Outline

2.1. PN Junction - Diode and application

2.2. Bipolar Junction Transistor (BJT) and applications

2.3. Operational amplifier (OPAM) and applications

Chapter 2. Semiconductor Devices

2.1. PN Junction - Diode and application

2.2. Bipolar Junction Transistor (BJT) and applications

2.3. Operational amplifier (OPAM) and applications

2.4. Voltage regulation

Chapter 2. Semiconductor Devices

2.1.1. N and P semiconductor

ATOMIC STRUCTURE

Nucleus: Protons (positive charge) + Neutron (uncharged)

Electrons: Negative charged particles

Atomic number: = # of protons = # of electrons

Atomic shells and orbits

Electrons orbit its nucleus at certain distances → orbit

Electrons near nucleus have less energy






Energy levels: each orbit corresponds to energy levels

Orbits are grouped into energy bands known as shells

Valence shell: outermost shell

Valence electrons: located in the valence shell

Number of electrons in each shell: $N = 2n^2$

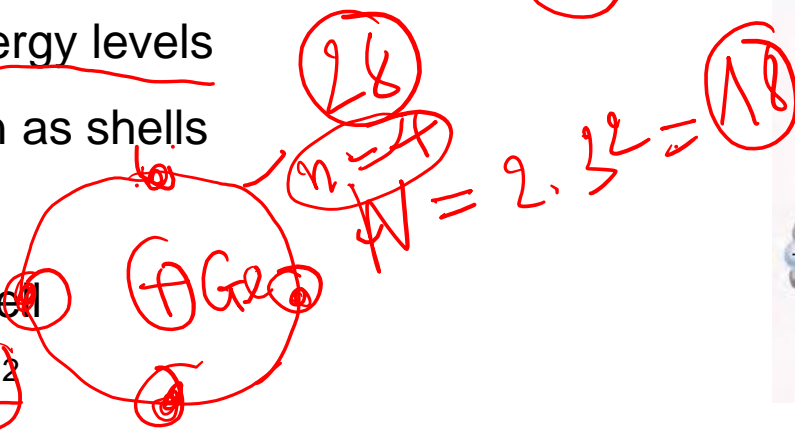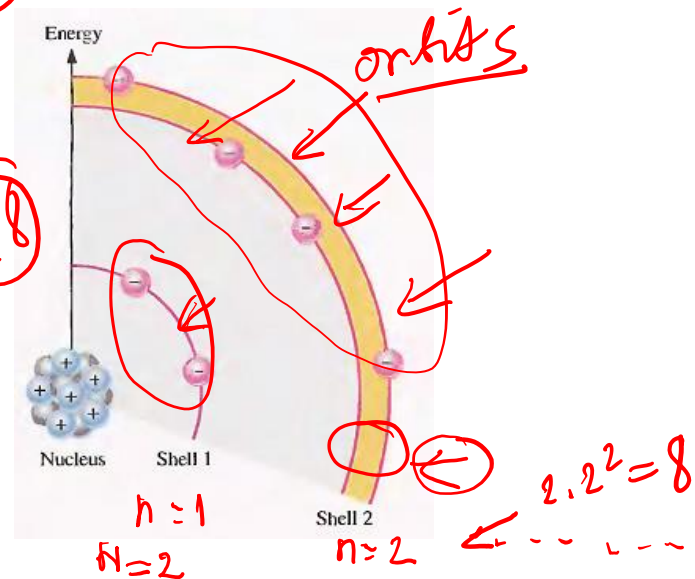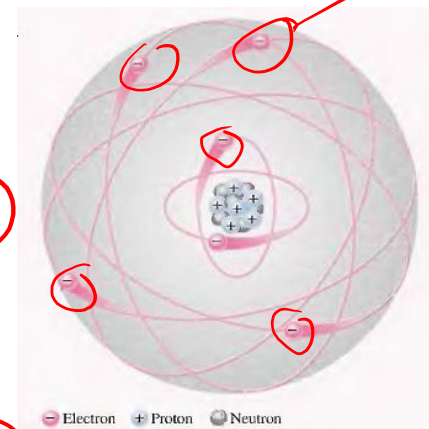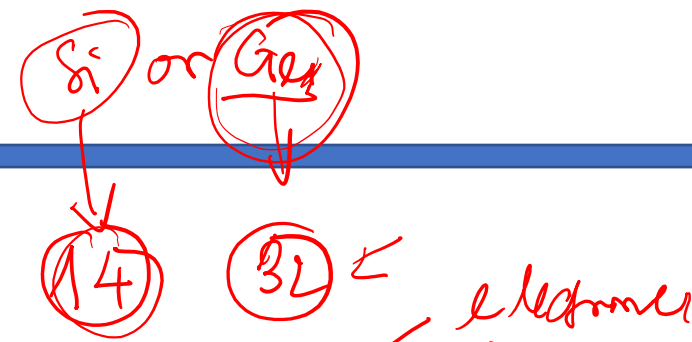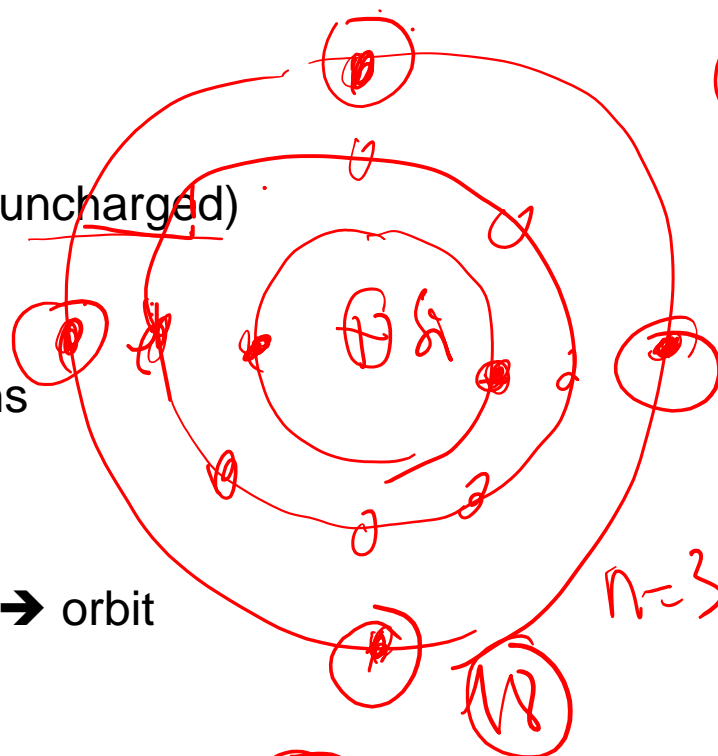

Chapter 2. Semiconductor Devices



CONDUCTORS , INSULATORS, SEMICONDUCTORS

Conductor: easily conducts elec. current

Insulator: no elec. current conducted in normal condition

Semiconductors: ability to conduct elec. current


Energy bands

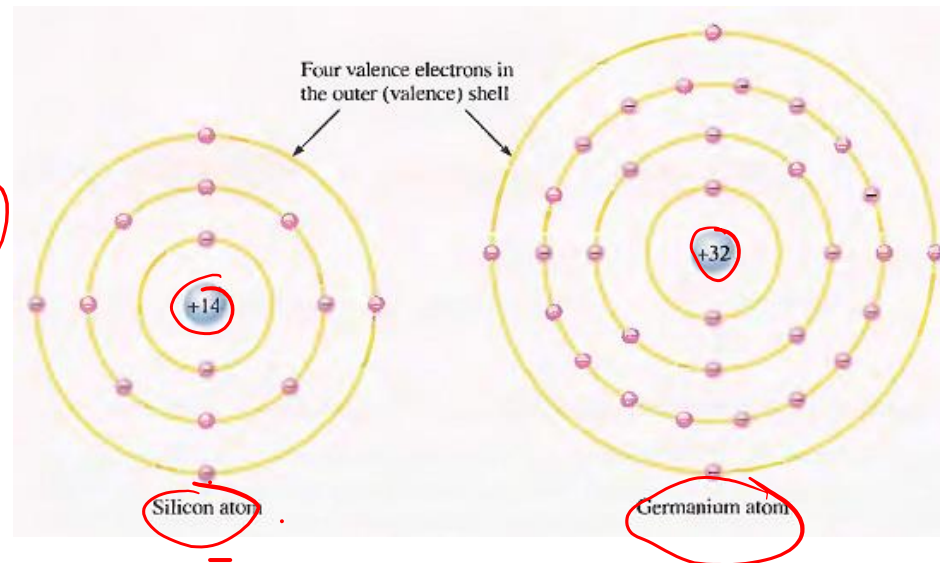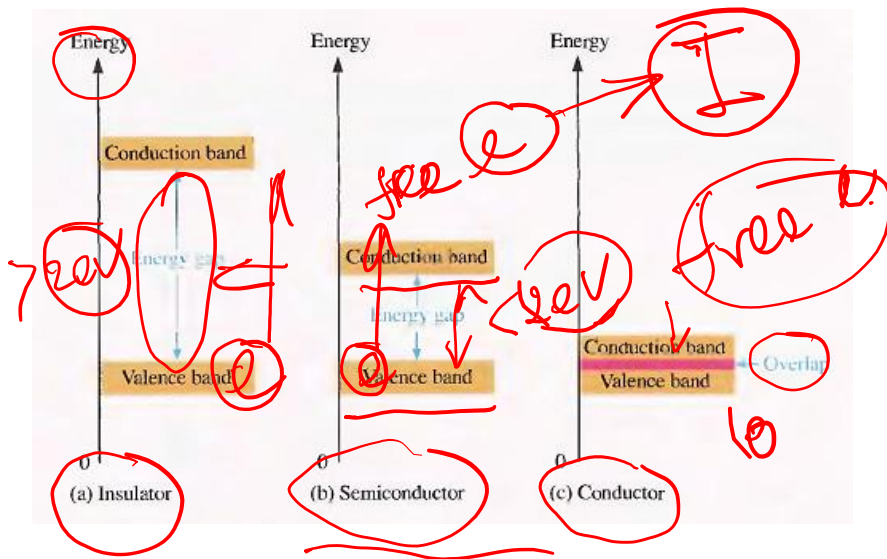

Chapter 2. Semiconductor Devices

COVALENT BONDS



Shared electrons

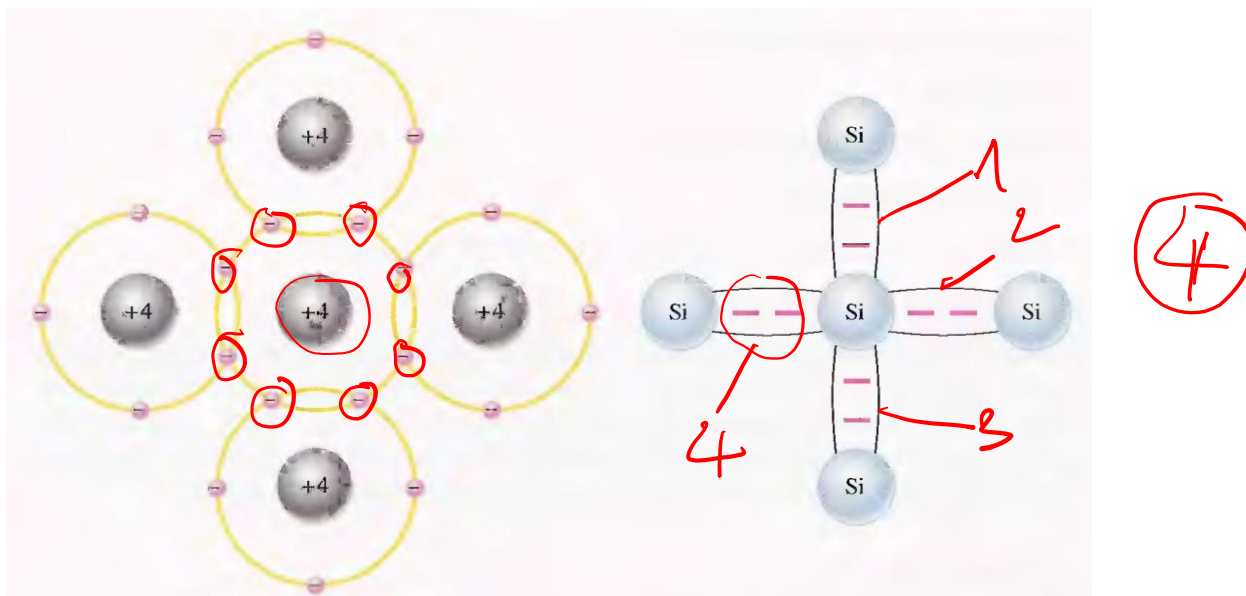


Chapter 2. Semiconductor Devices

CONDUCTION IN SEMICONDUCTORS

Electron-hole pairs

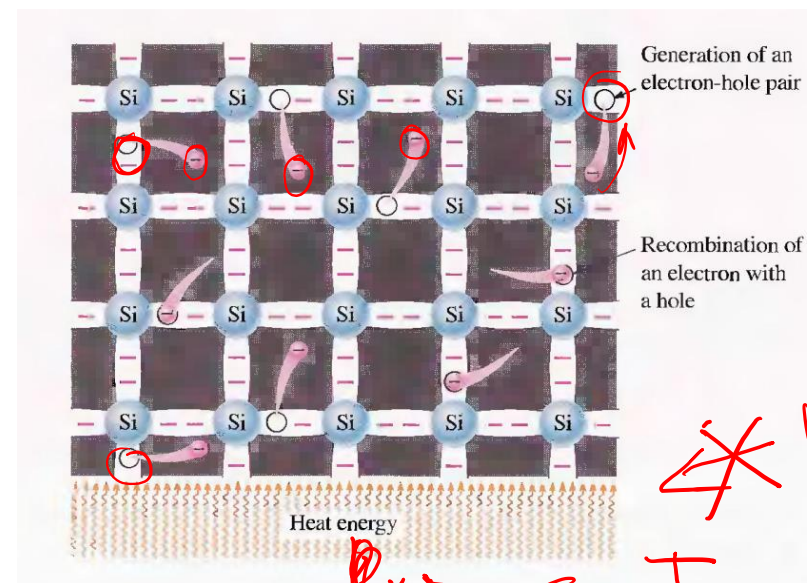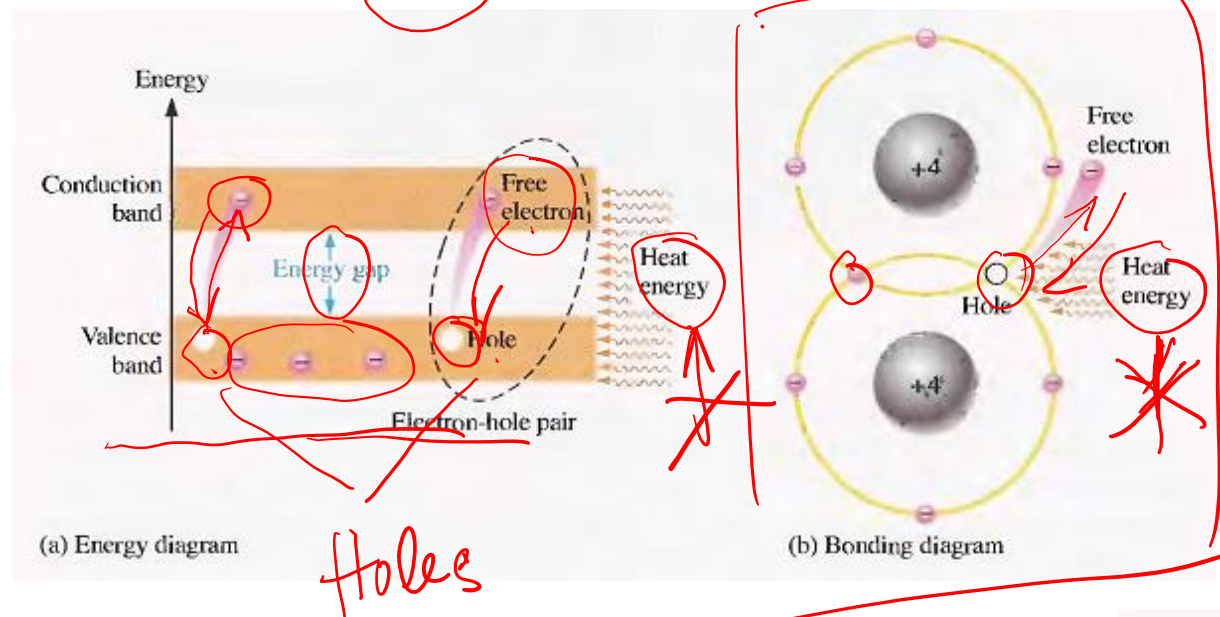


Electron and hole currents

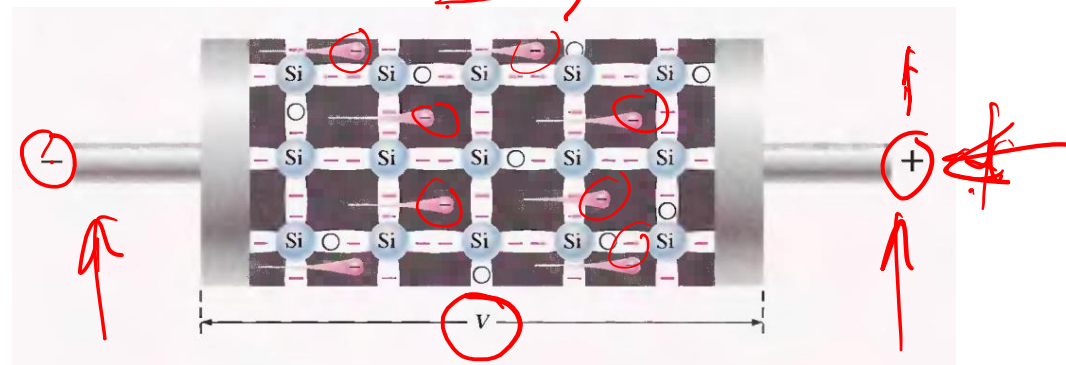

Chapter 2. Semiconductor Devices

N-type & P-type SEMICONDUCTORS

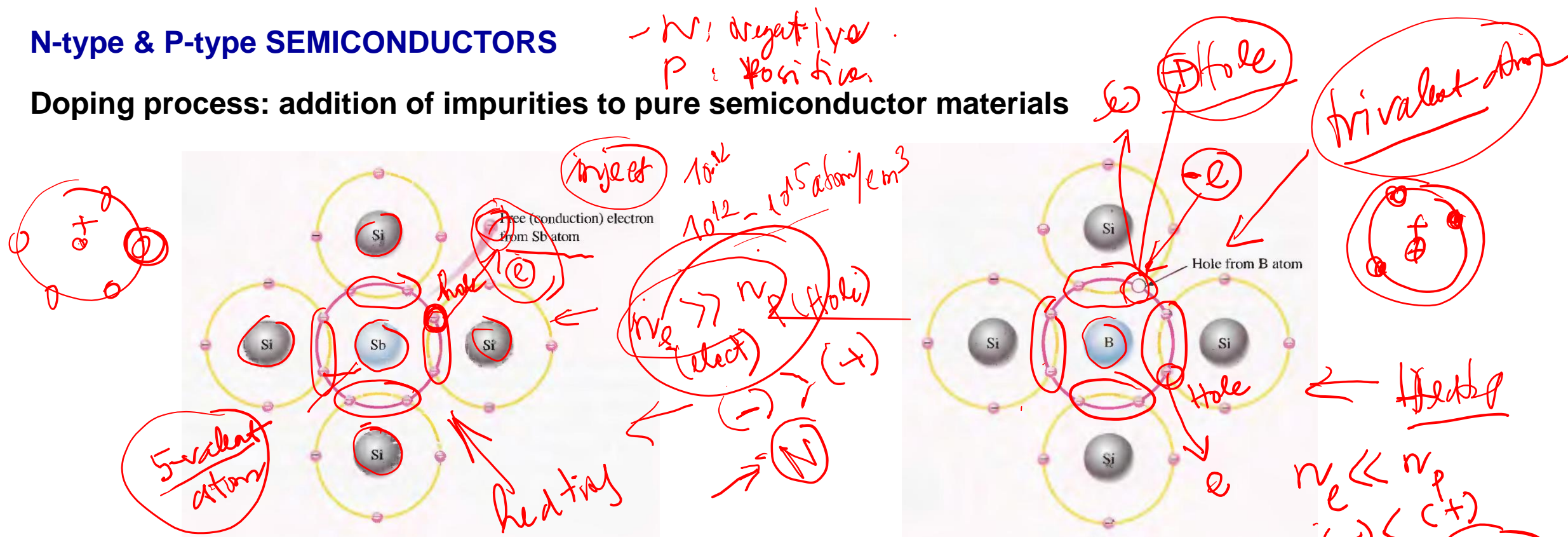Doping process: addition of impurities to pure semiconductor materials



N-type (pentavalent Arsenic/phosphorus atoms)

P-type (trivalent Boron/Gallium atoms)

Majority and minority carriers

N-type vs P-type

e⁻ - major
p⁺ - minor

p - major - da so!
e⁻ - minor - thin so!




Chapter 2. Semiconductor Devices


2.1. PN Junction - Diode and application

2.1.1. N and P semiconductor

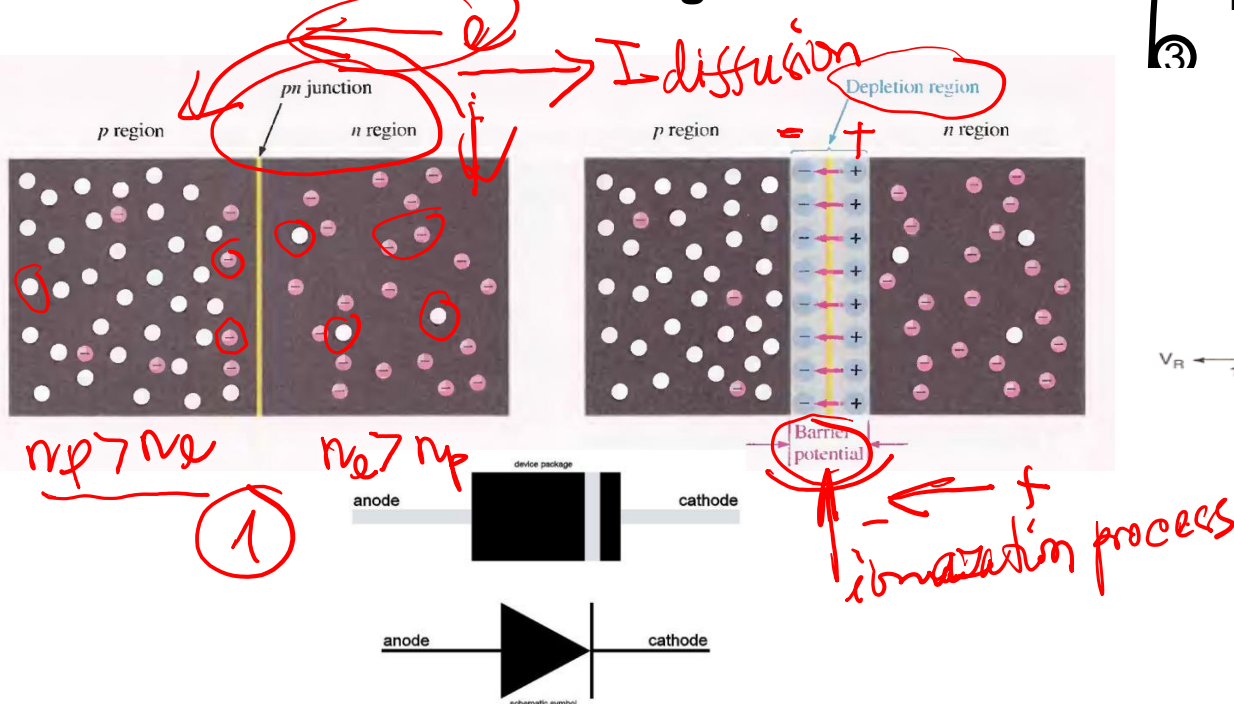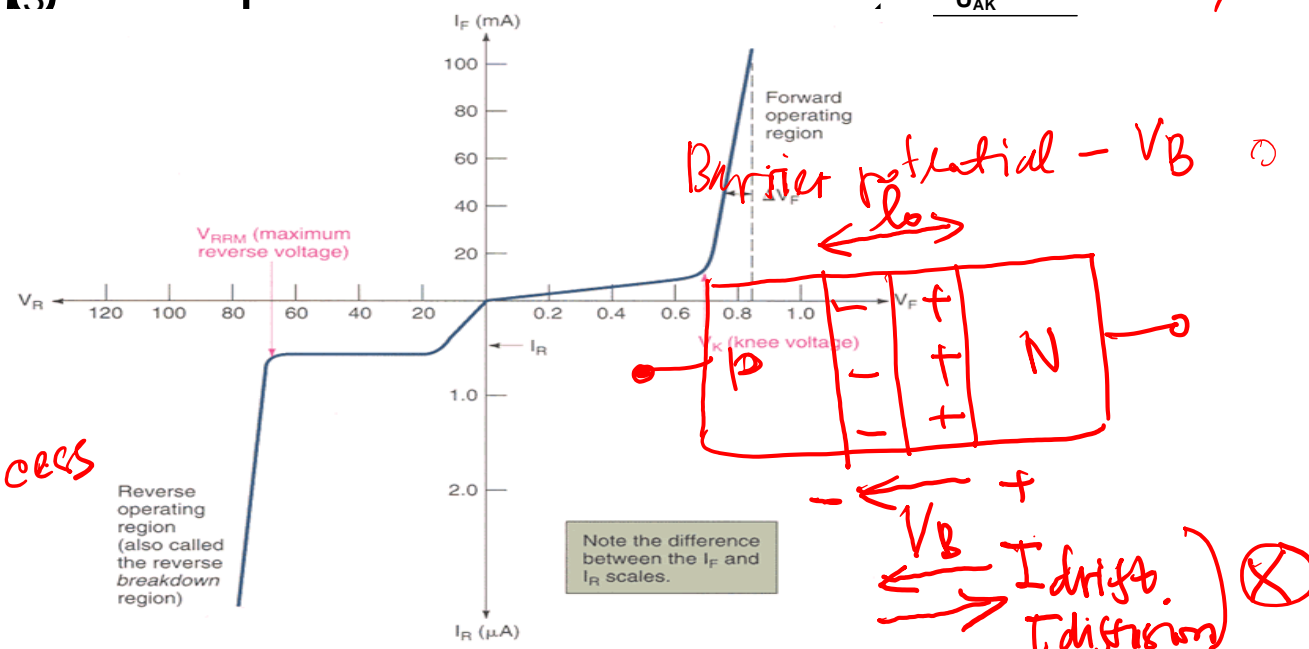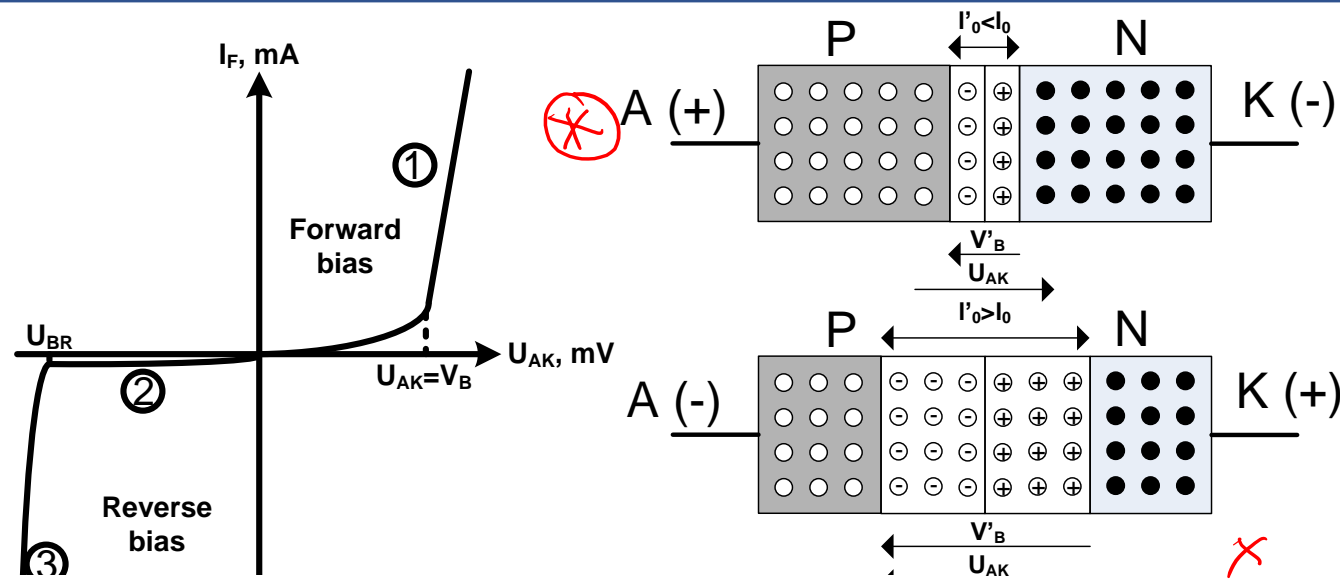2.1.2. PN junction - Diode

- Forward bias vs reverse bias
- V-A characteristic
- Breakdown: tunneling vs Zener diode




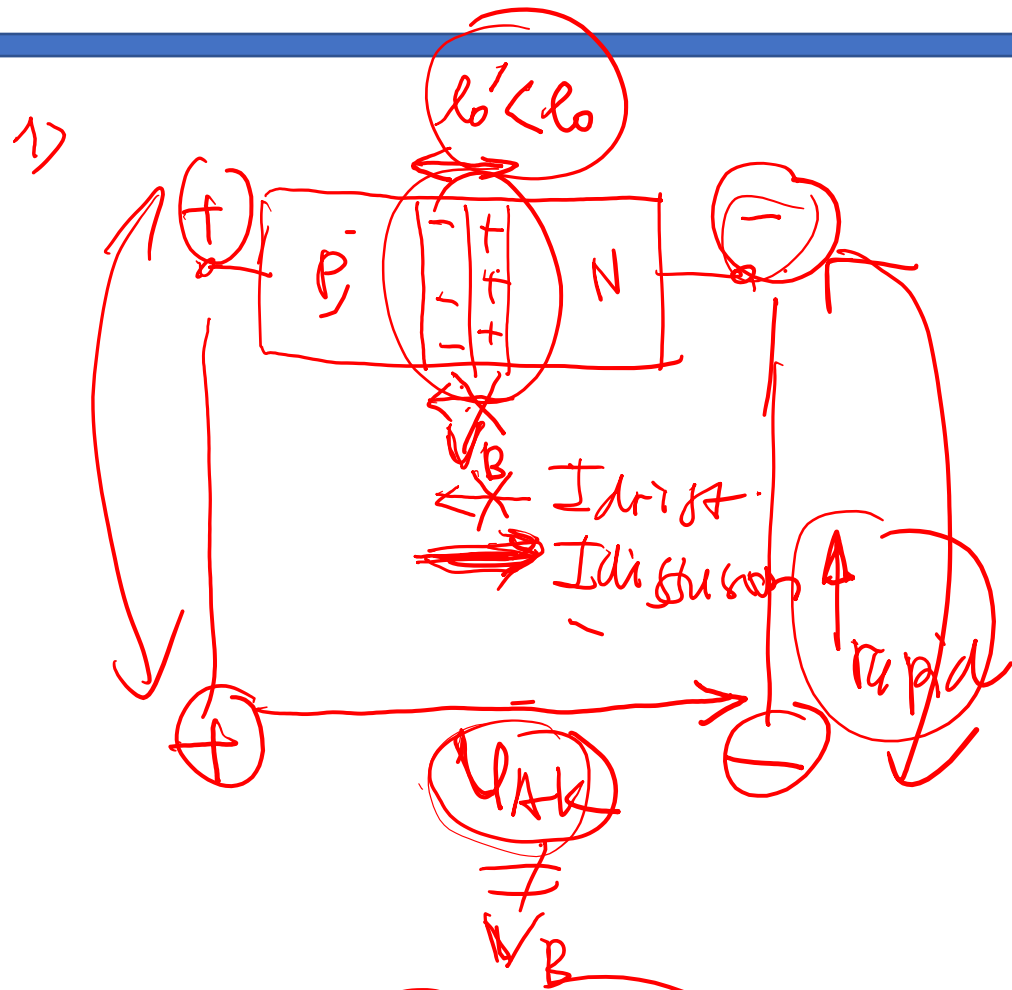

→ Forward Bias













P/n junction is forward biased

→ $I_{diffusion} \equiv$ Forward current $- I_A \neq I_S$ small

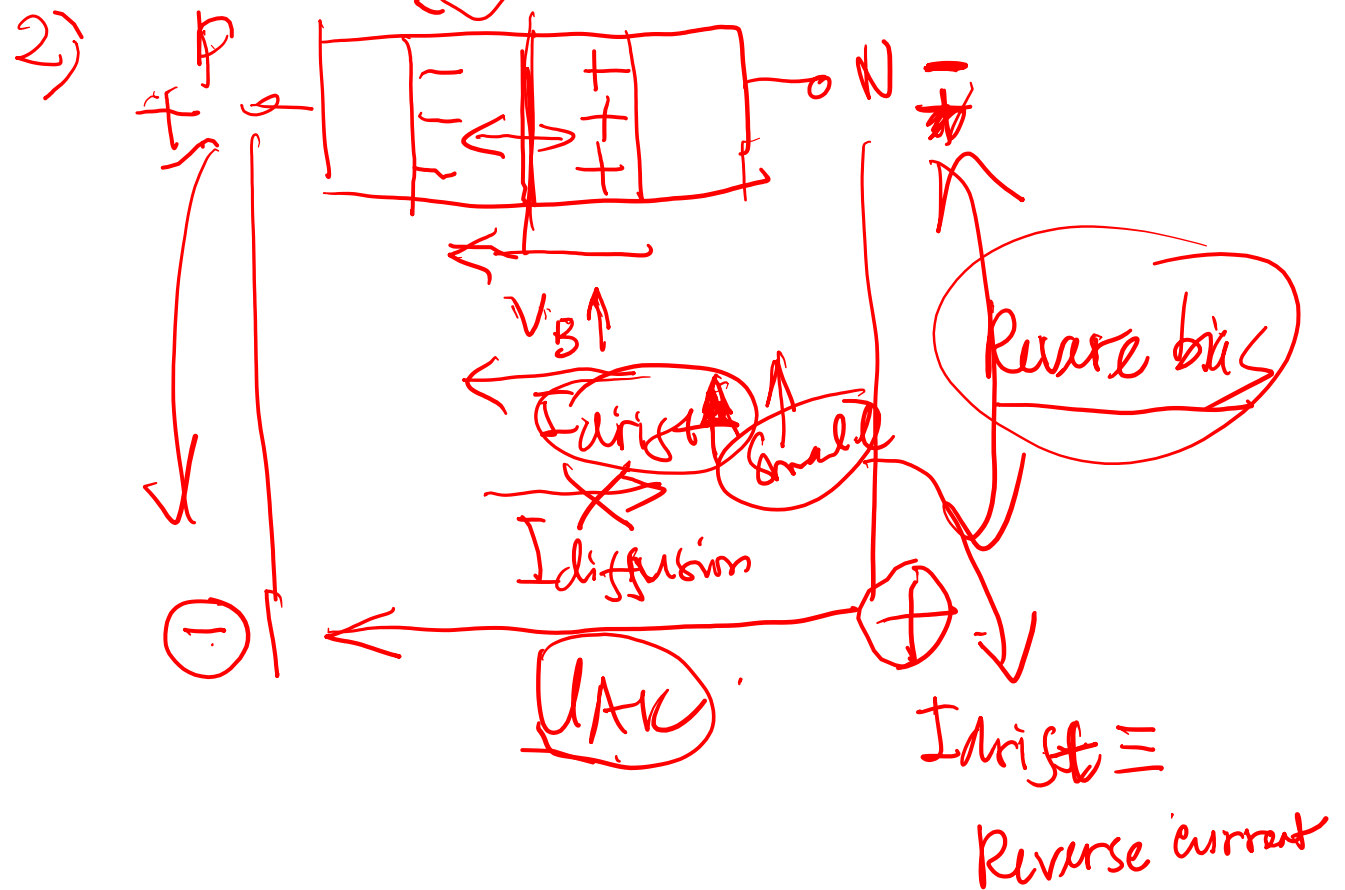

Chapter 2. Semiconductor Devices (Cont.)

- **Some types of diode**

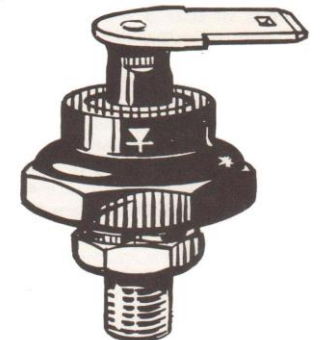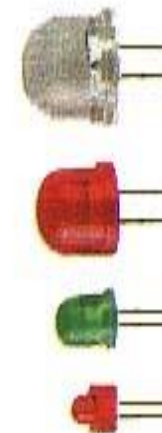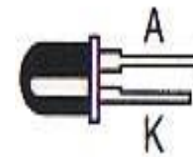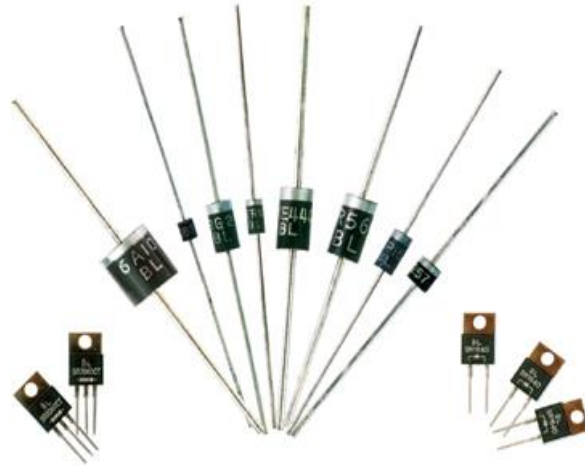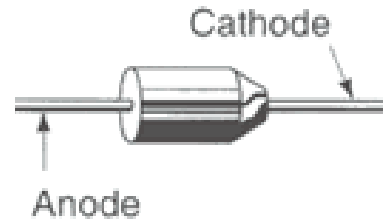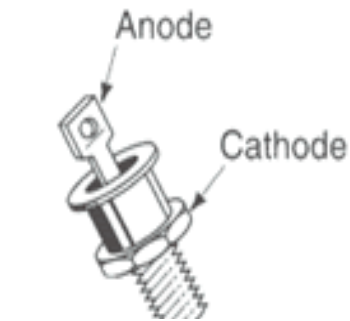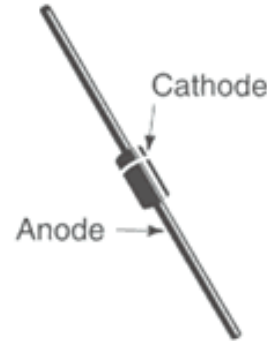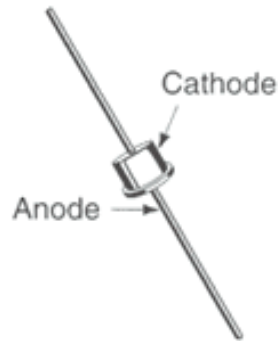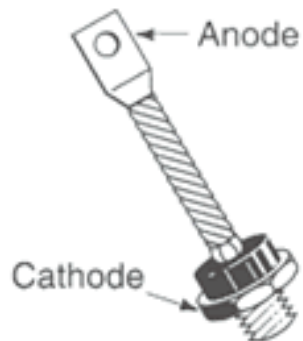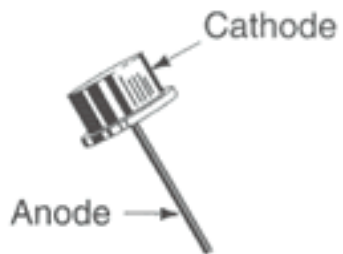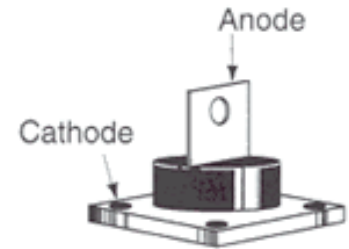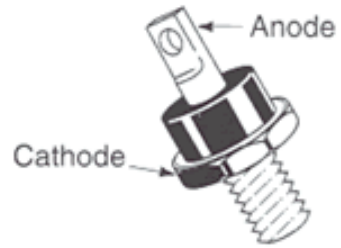





2.1.2. System applications

a. Half-wave rectifier

- Positive half-wave: D_1 FB, $U_{out} = U_L = U_2$
- Negative half-wave: D_1 RB, $U_{out} = 0$



b. Full-wave (center-tapped) rectifier

- $U_{21}+$, $U_{22}-$: D_1 FB, D_2 RB, $U_{out} = U_L = U_{21}$
- $U_{21}-$, $U_{22}+$: D_1 RB, D_2 FB, $U_{out} = U_L = U_{22}$

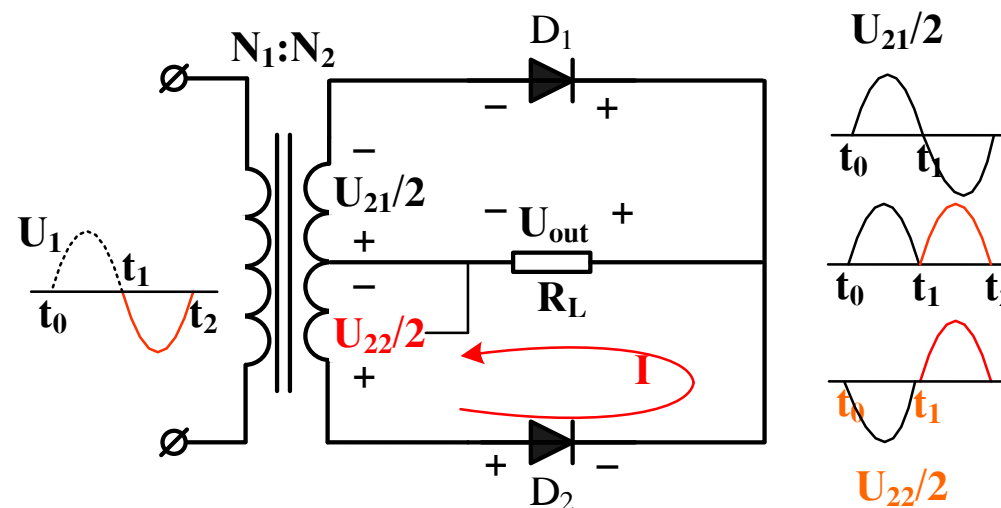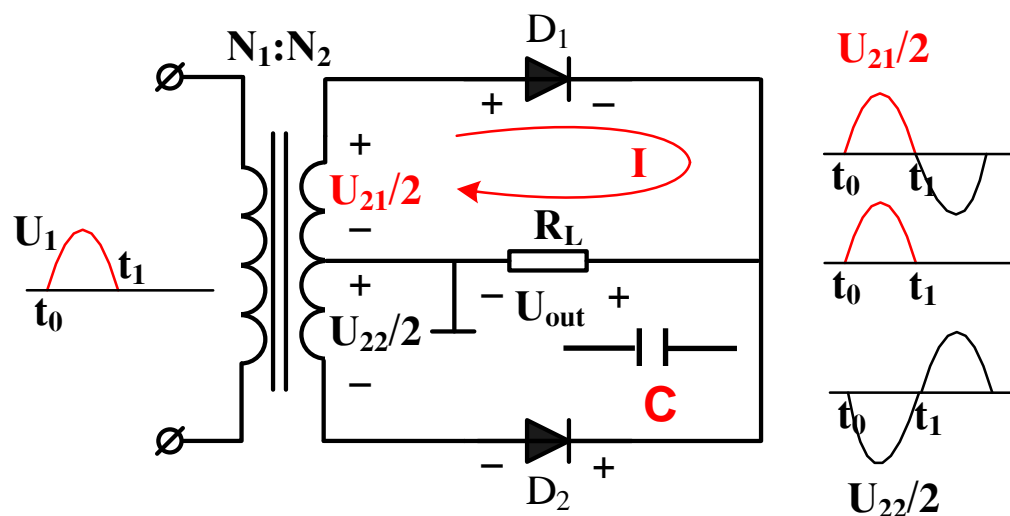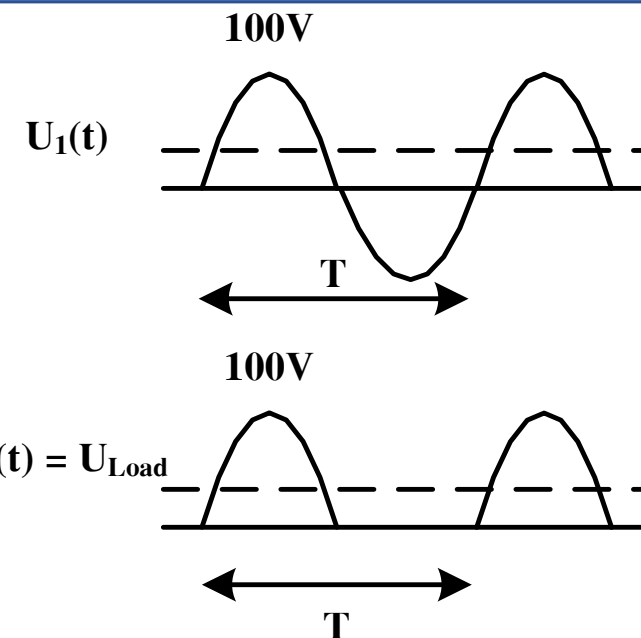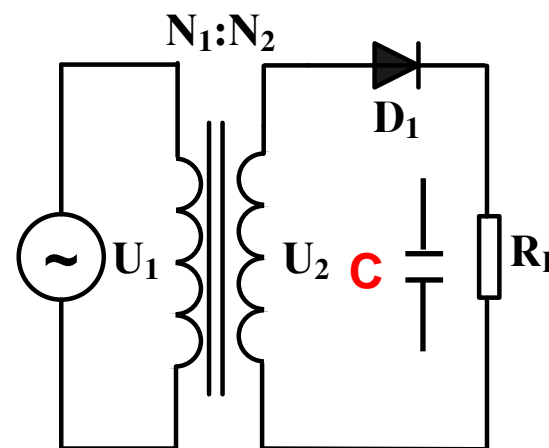


Chapter 2. Semiconductor Devices (Cont.)


c. Bridge rectifier

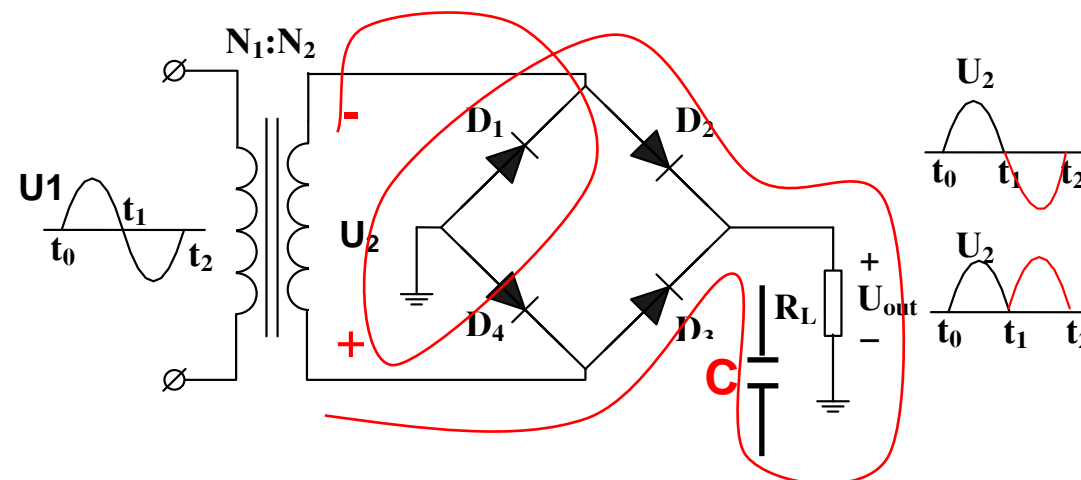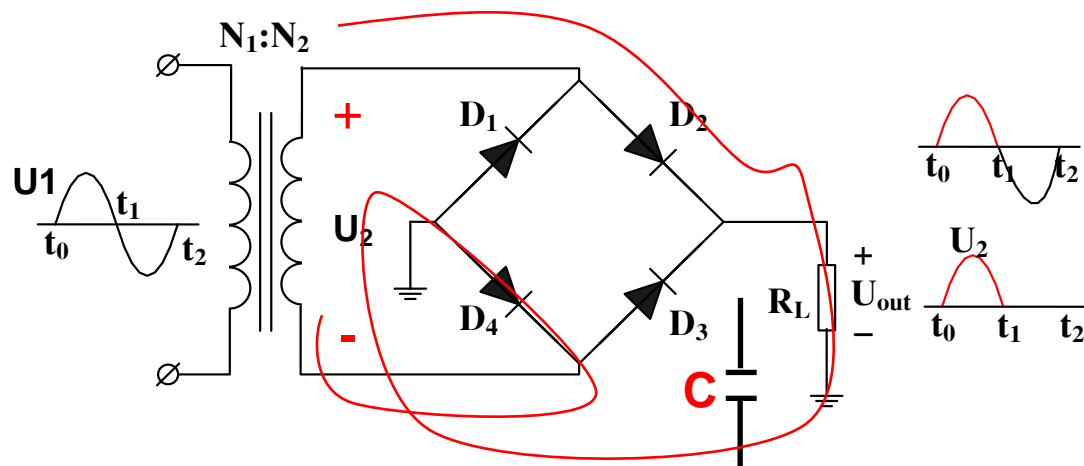

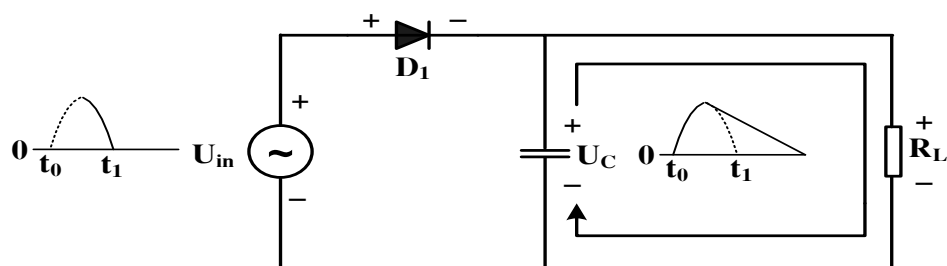
- **Positive half-wave:** D_2 - D_4 FB, D_1 - D_3 RB, $U_{out} = U_L = U_2$
- **Negative half-wave:** D_2 - D_4 RB, D_1 - D_3 FB, $U_{out} = U_L = U_2$



- **Positive half-wave**

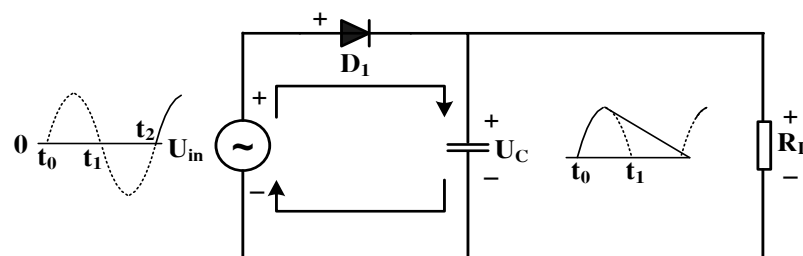

- **Positive half-wave**

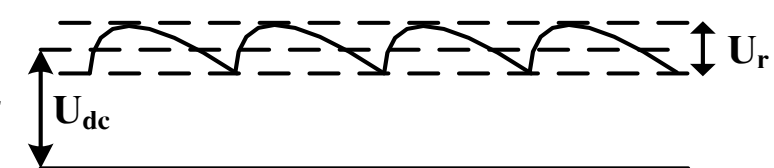


- **Ripples factor = U_r/U_{DC}**

Chapter 2. Semiconductor Devices (Cont.)

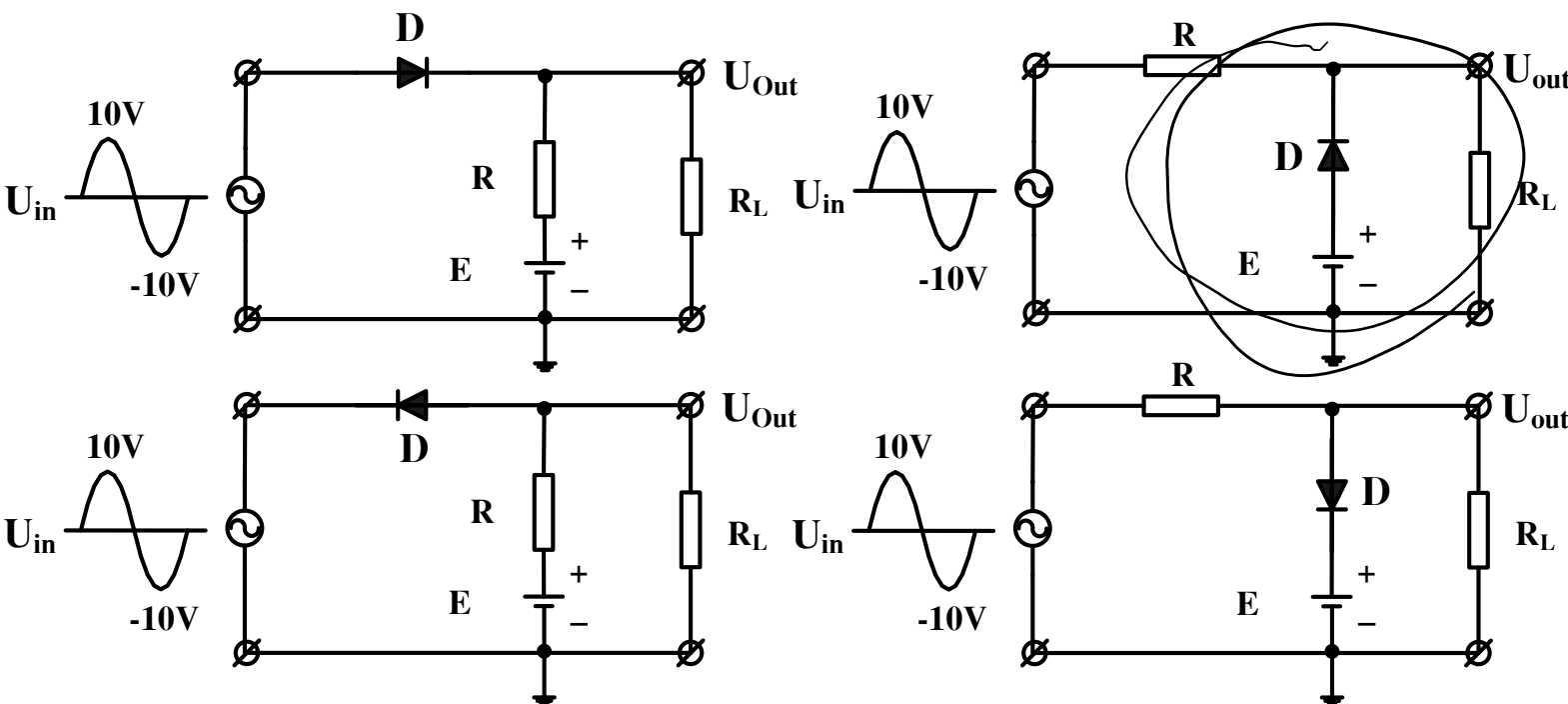
d. Voltage limiter

- Lower limiter: Limit a voltage signal under a given threshold
- Upper limiter: Limit a voltage signal above a given threshold
- Serial limiter: Diode connected in serial to the load
- Parallel limiter: Diode connected in parallel to the load



QUESTIONS!

1. The other 2 lower circuits?
2. If $E < 10V$ or $E > 10V$?
3. If E removed?

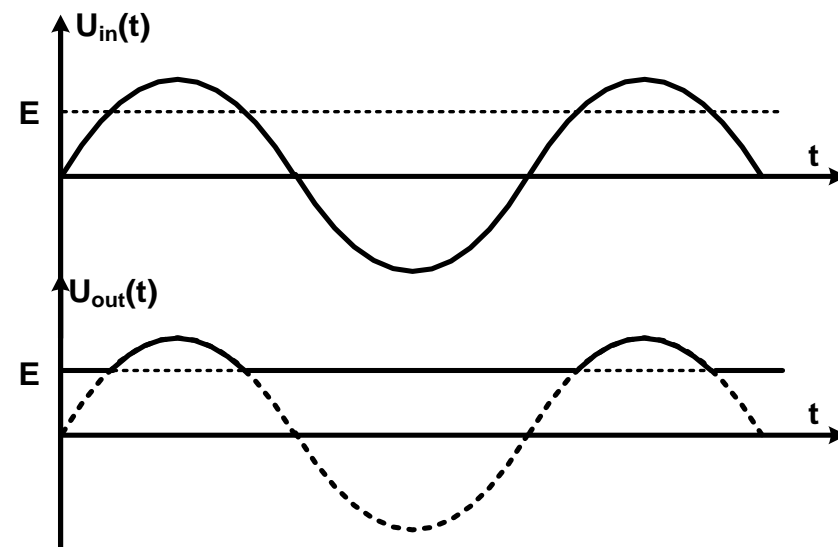

Chapter 2. Semiconductor Devices (Cont.)

2.1. PN Junction - Diode and application


2.2. Bipolar Junction Transistor (BJT) and applications

2.3. Operational amplifier (OPAM) and applications

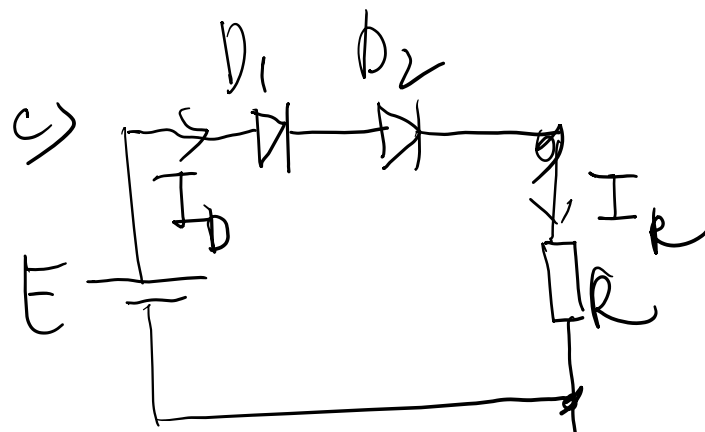
2.4. Voltage regulation



$$\begin{aligned} V_B = V_0 &= 0,7V & U_R &= ? \\ E &= +8V & I_R &= ? \\ R &= 2k\Omega \end{aligned}$$



$$U_{D1}(Si) = 0.7V \quad | \quad U_R = ?$$
$$U_{D2}(Ge) = 0.3V \quad | \quad I_R = ?$$
$$E = +12V, R = 6k\Omega$$

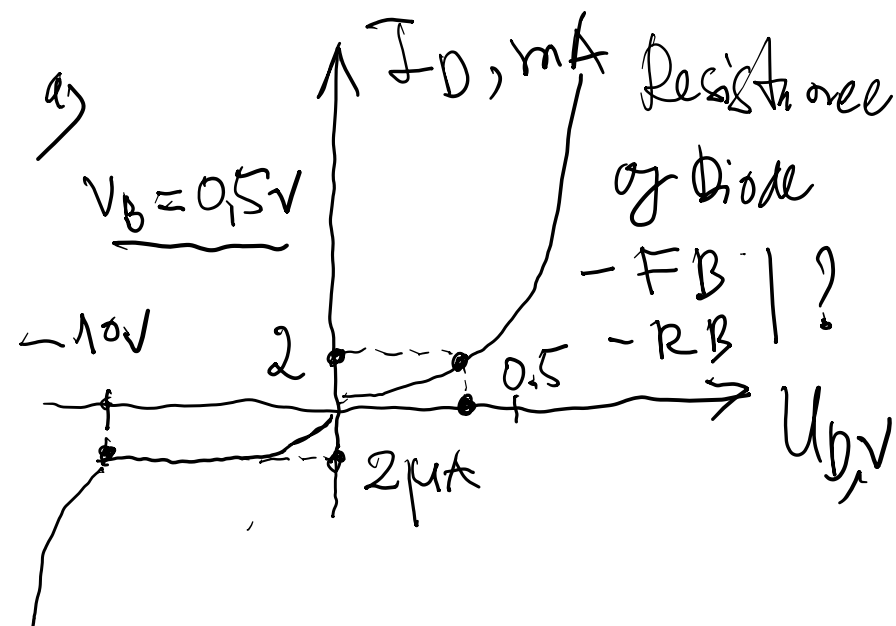

Chapter 2. Semiconductor Devices (Cont.)

2.2. Bipolar Junction Transistor (BJT) and applications

2.2.1. Basic construction

- J_E = PN junction between E-B; J_C = PN junction between B-C
- For amplification: J_E – Forward biased, J_C = Reverse biased

- NPN: $U_E < U_B < U_C$

- PNP: $U_E > U_B > U_C$


- Basic equations:

- Currents $I_E = I_C + I_B$ (1)



- DC current amplifier gain: $\beta = \frac{I_C}{I_B}$ (2)

- DC current transfer gain: $\alpha = \frac{I_C}{I_E}$ (3)
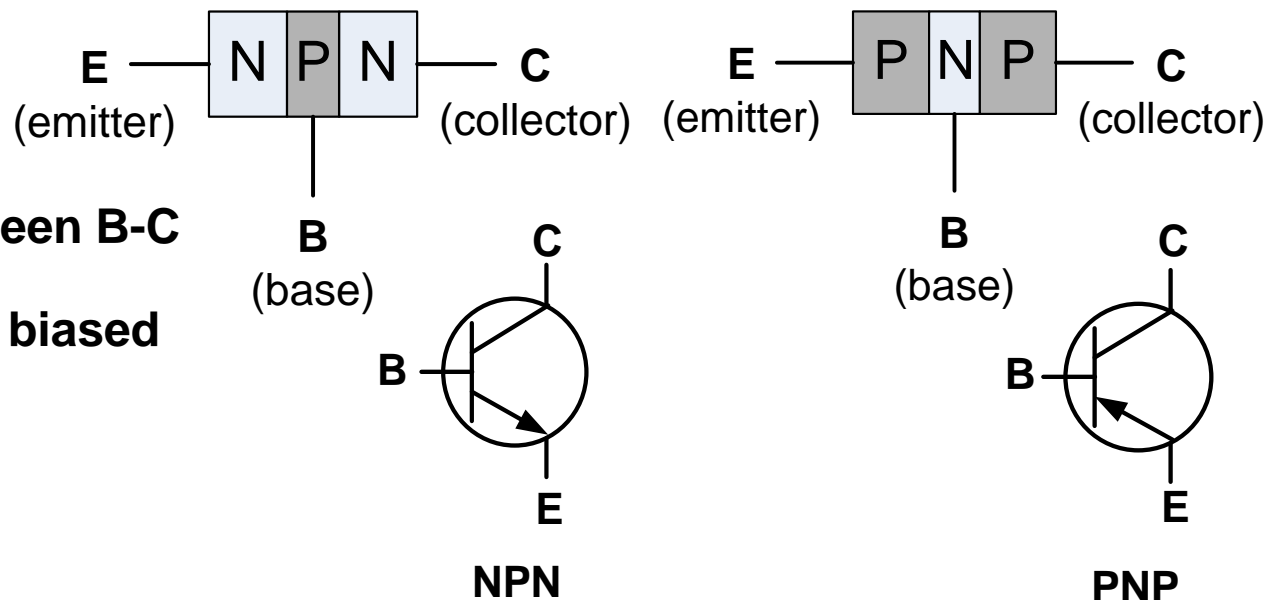
$$\beta = \frac{\alpha}{1 - \alpha} \quad \alpha = \frac{\beta}{\beta + 1}$$



2N3904 NPN Transistor

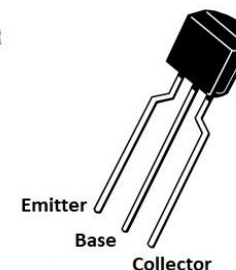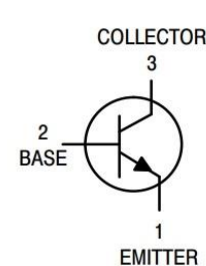

C-E Voltage: 40V
C-B Voltage: 60V
Collector Current: 200mA

Chapter 2. Semiconductor Devices (Cont.)

2.2.2. Transistor as a 4-Terminal system

- System of impedance equations

$$U_1 = r_{11}I_1 + r_{12}I_2$$

$$U_2 = r_{21}I_1 + r_{22}I_2$$

r_{ij} : impedance parameters

- System of susceptance equations

$$I_1 = g_{11}U_1 + g_{12}U_2$$

$$U_2 = g_{21}U_1 + g_{22}U_2$$

g_{ij} : susceptive parameters

- System of hybrid equations

$$U_1 = h_{11}I_1 + h_{12}U_2$$

$$I_2 = h_{21}I_1 + h_{22}U_2$$

h_{ij} : hybrid parameters



Input susceptance/resistance: $h_{11} = \frac{\partial I_1}{\partial U_1} = \frac{1}{r_{11}}$ keeping $U_2 = \text{const}$

Voltage amplifier gain: $h_{12} = \frac{\partial U_1}{\partial U_2} = \frac{1}{K_u}$ keeping $I_1 = \text{const}$

Current amplifier gain: $h_{21} = \frac{\partial I_1}{\partial I_2} = \frac{1}{K_i}$ keeping $U_2 = \text{const}$

Output susceptance/resistance: $h_{22} = \frac{\partial I_2}{\partial U_2} = \frac{1}{r_2}$ keeping $I_1 = \text{const}$

Input characteristic: $I_1 = f(U_1)$ keeping $U_2 = \text{const}$







Output characteristic: $I_2 = f(U_2)$ keeping $I_1 = \text{const}$

Transfer characteristic: $I_1 = f(I_2)$ keeping $U_2 = \text{const}$

Chapter 2. Semiconductor Devices (Cont.)

2.2.3. Amplifier schemes


- EC: Emitter in common; CC: Collector in common; BC: Base in common

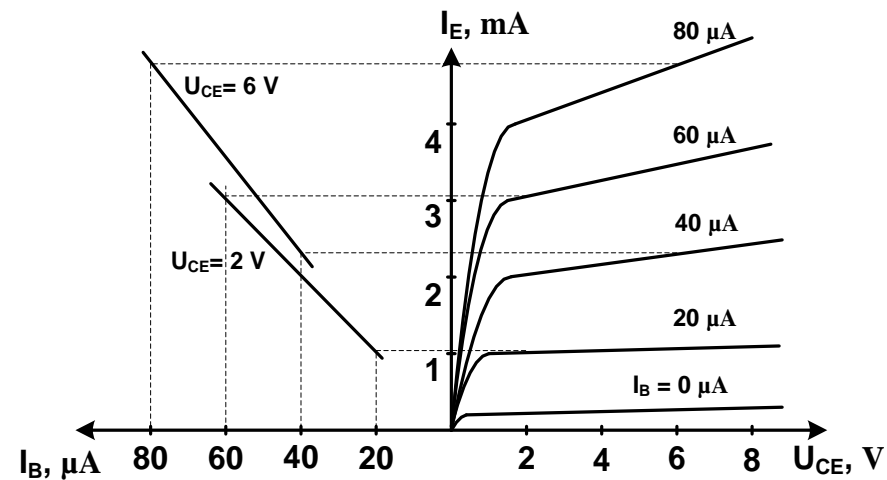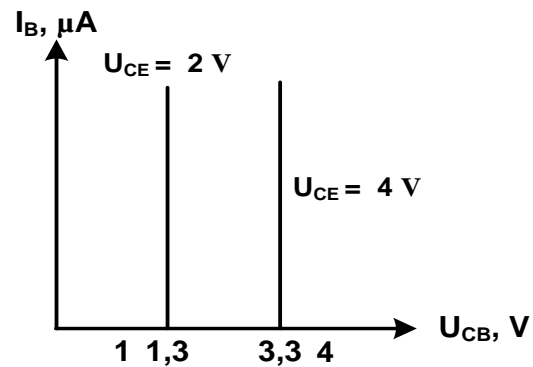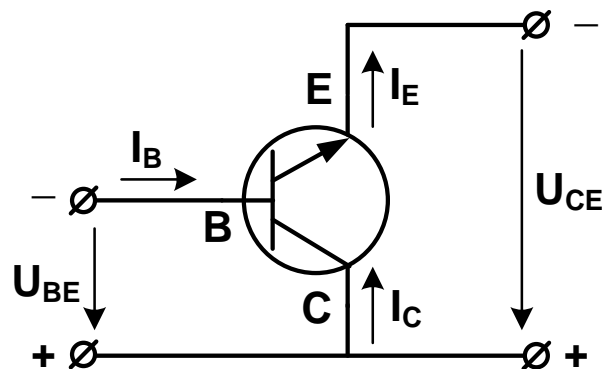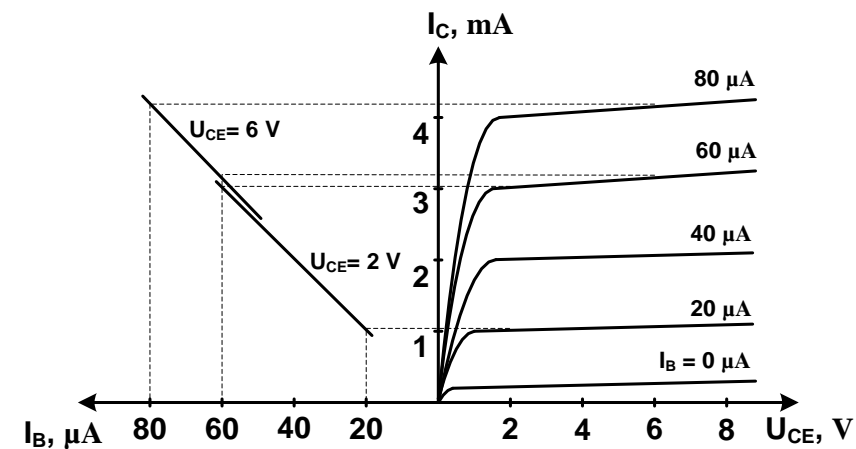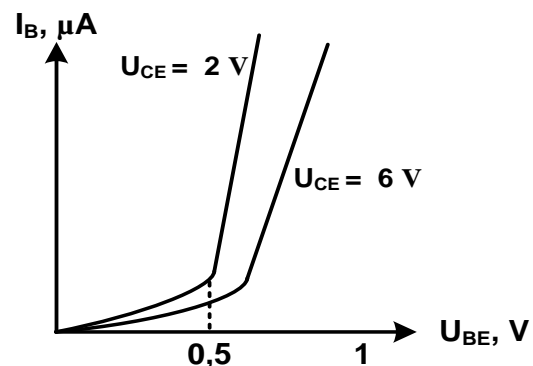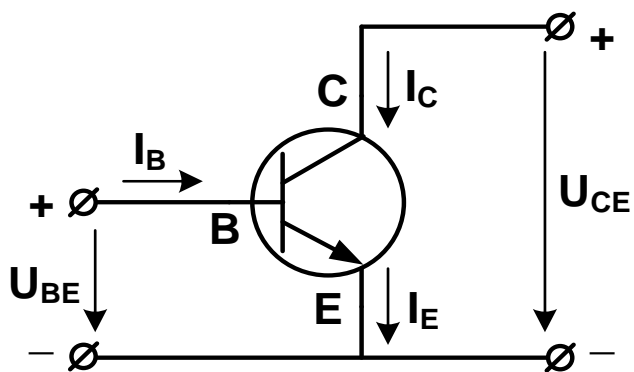


Chapter 2. Semiconductor Devices (Cont.)

2.2.4. BJT amplifier: DC mode


- Why DC mode? What DC bias?

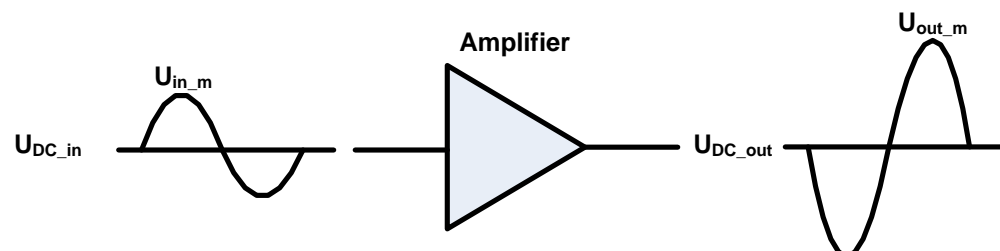


Linear amplification

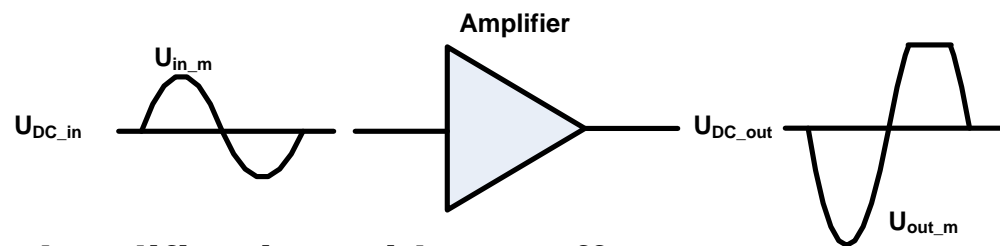

Amplification with cut-off

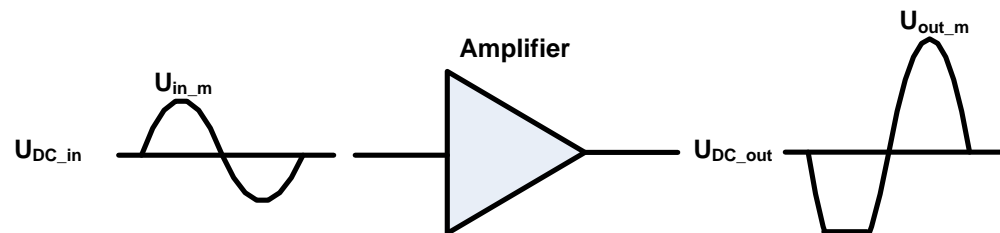

Amplification saturation

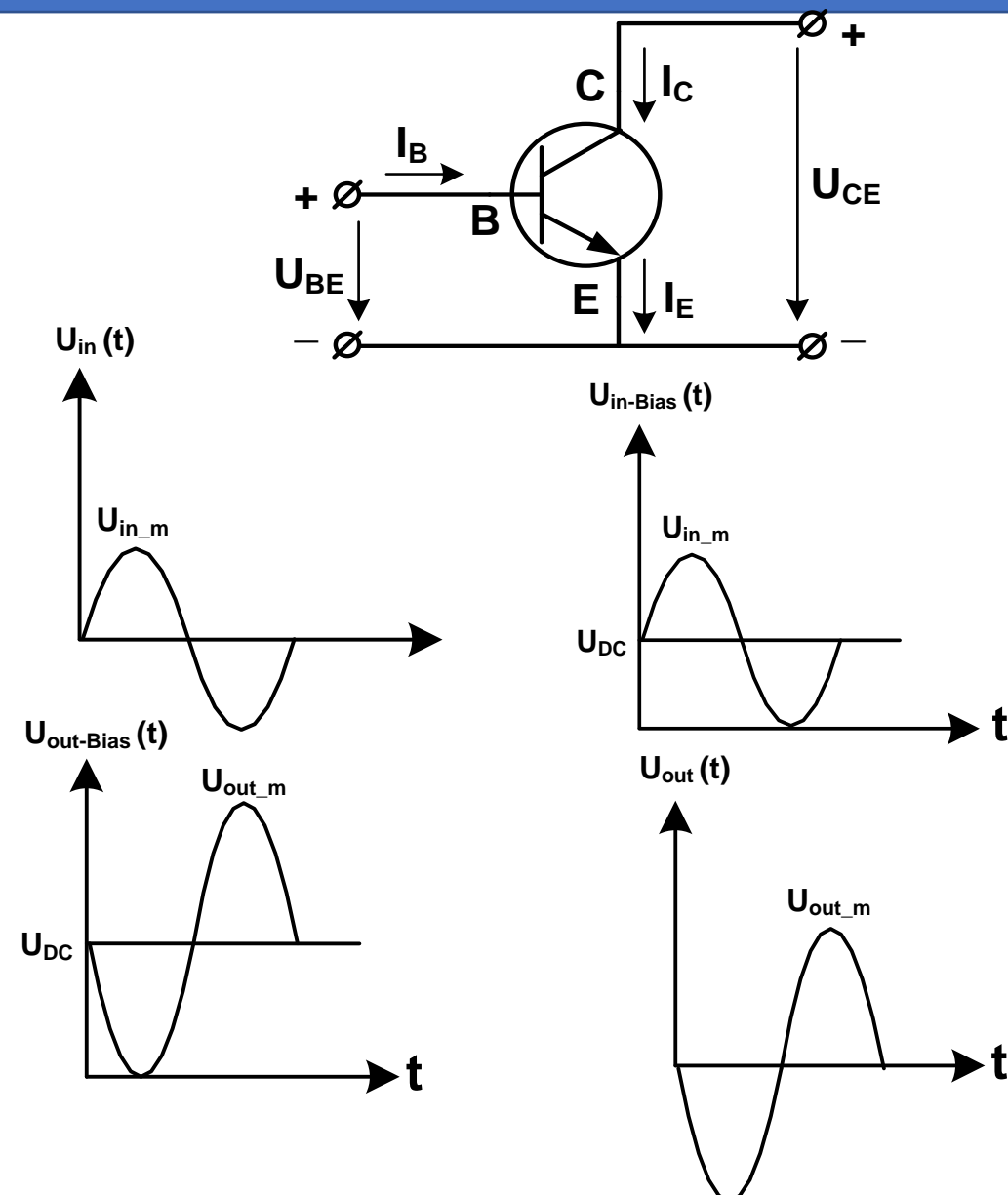

Chapter 2. Semiconductor Devices (Cont.)




- DC mode: Q (quiescent) point; DC load line, DC load)

- Q-point** (Input current, Output current, Output voltage)

Question: Q point of EC, CC, BC? **Answer:** **EC:** $Q(I_B, I_C, U_{CE})$; **CC:** $Q(I_B, I_E, U_{CE})$; **BC:** $Q(I_E, I_C, U_{BC})$

- DC load line:** Determine on output characteristic, where Q is intersection with DC load line

- DC load**

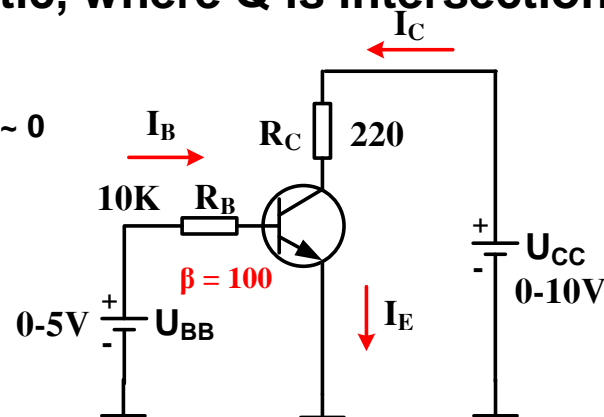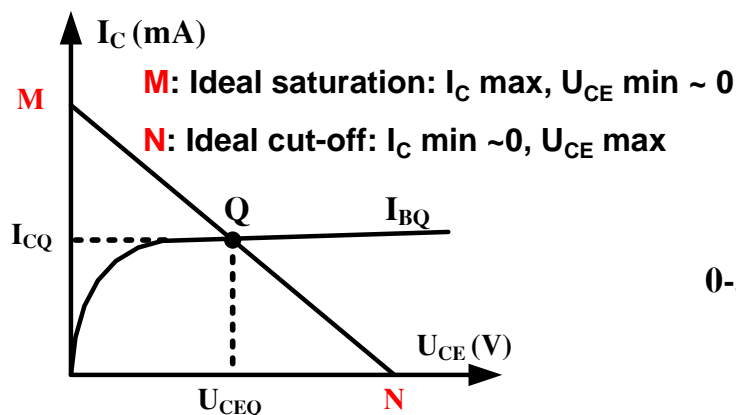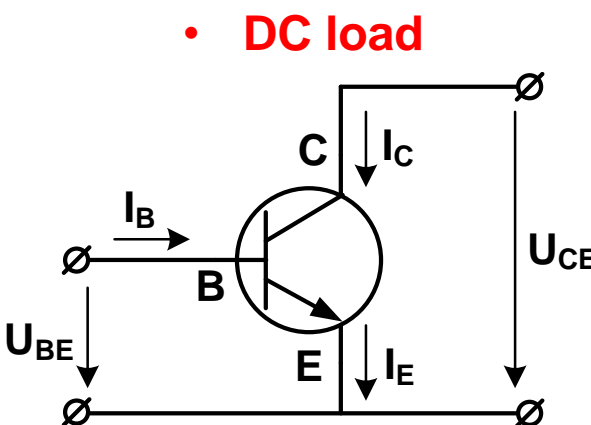





$$I_B = 100\mu A \rightarrow I_C = 100 \cdot 100\mu A = 10\text{mA}$$

$$I_B = 200\mu A \rightarrow I_C = 100 \cdot 200\mu A = 20\text{mA}$$

$$I_B = 300\mu A \rightarrow I_C = 100 \cdot 300\mu A = 30\text{mA}$$


$$I_B = 400\mu A \rightarrow I_C = 100 \cdot 400\mu A = 40\text{mA}$$

$$U_{CE} = U_{CC} - U_{RC} = U_{CC} - I_C R_C$$

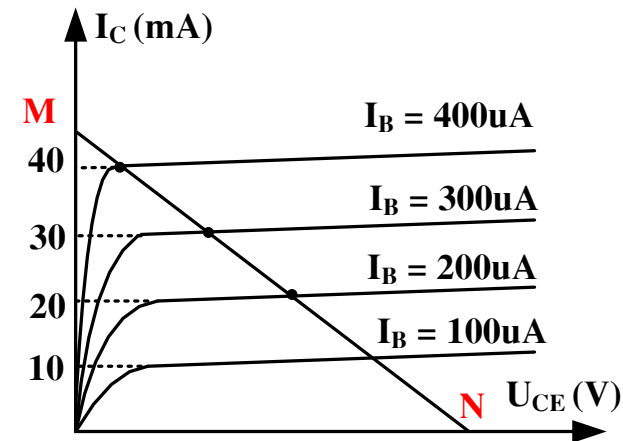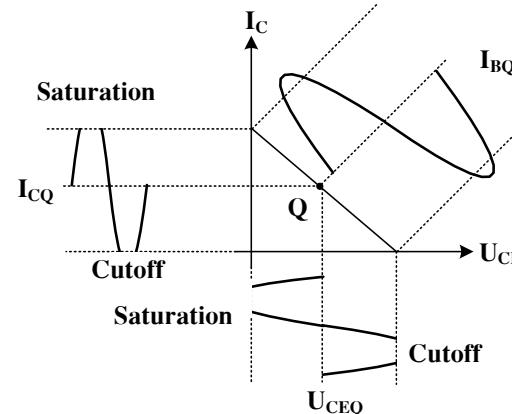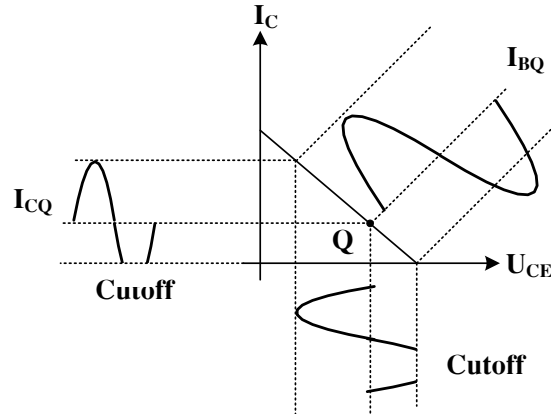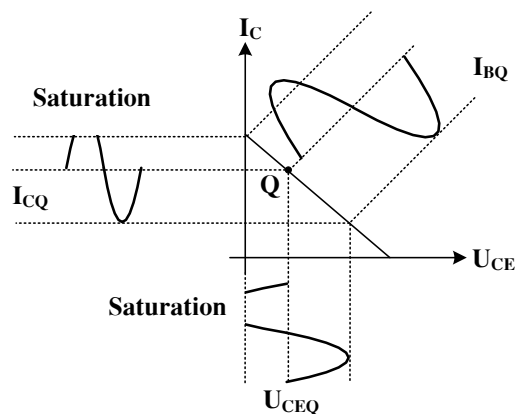

Chapter 2. Semiconductor Devices (Cont.)

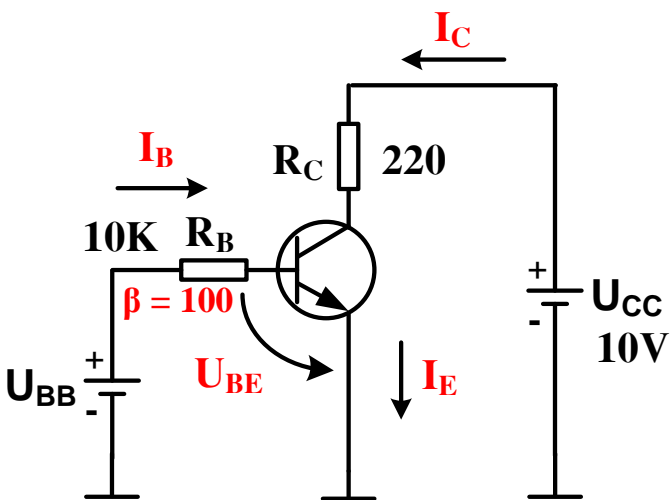- Example 1:** $U_{BE} = 0.7V$. Determine Q point with 1) $U_{BB} = 2.7V$; 2) $U_{BB} = 3.7V$; 3) $U_{BB} = 4.7V$



1. **From input:** $U_{BB} = 2.7V \rightarrow I_{BQ} = (U_{BB} - U_{BE})/R_B = (2.7-0.7)10K = 200 \mu A \rightarrow I_{CQ} = \beta I_B = 20 \text{ mA}$

From output: $U_{CEQ} = U_{CC} - I_C R_C = 10V - 20mA \cdot 220 = 5.6V$

2. $U_{BB} = 3.7V \rightarrow I_{BQ} = (U_{BB} - U_{BE})/R_B = (3.7-0.7)10K = 300 \mu A \rightarrow I_{CQ} = \beta I_B = 30 \text{ mA}$


From output: $U_{CEQ} = U_{CC} - I_C R_C = 10V - 30mA \cdot 220 = 3.4V$

3. $U_{BB} = 4.7V \rightarrow I_{BQ} = (U_{BB} - U_{BE})/R_B = (4.7-0.7)10K = 400 \mu A \rightarrow I_{CQ} = \beta I_B = 40 \text{ mA}$

From output: $U_{CEQ} = U_{CC} - I_C R_C = 10V - 40mA \cdot 220 = 1.2V$

- Example 2:** Draw DC load line

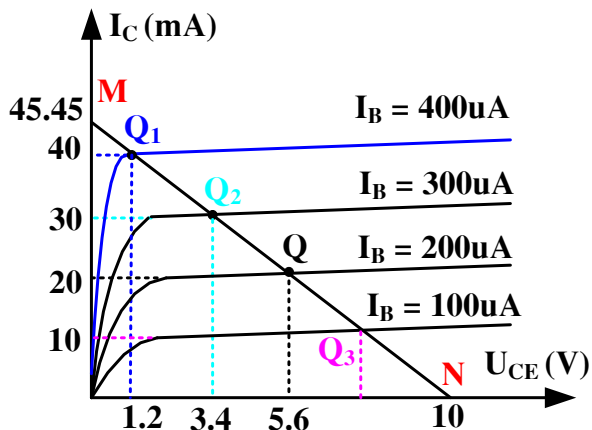- Example 3:** Max variation of $I_B = ?$ for linear operation in case 1, 2, 3



1. $I_{Cmax} = I_{C(sat)} = U_{CC}/R_C = 10/220 = 45.45mA$, $I_{CQ} = 20mA \rightarrow \text{Max var} = 45.45 - 20 = +25.45 \text{ mA}/-20mA$

2. Analogy, $I_{CQ} = 30mA \rightarrow \text{Max var} = 45.45 - 30 = +15.45 \text{ mA}/-30mA$

3. Analogy, $I_{CQ} = 40mA \rightarrow \text{Max var} = 45.45 - 40 = +5.45 \text{ mA}/-40mA$

Therefore for linear operation:

\rightarrow Max variation of I_B 1) $I_B = I_C/\beta = 20/100 = 200\mu A$; 2) $I_B = 15.45/100 = 155\mu A$; 3) $I_B = 5.45/100 = 54.5\mu A$

Chapter 2. Semiconductor Devices (Cont.)

- DC bias methods: a) Fixed base current; b) Feedback current; c) Emitter current (self-bias); d) Emitter bias

Goal: + Setup Q-point for best linear amplification

+ Steps for determination of DC mode

a) Fixed base current

✓ Q-point:

- From input: $E_C = U_{RB} + U_{BE} = I_B R_B + U_{BE}$

→ $I_{BQ} = (E_C - U_{BE}) / R_B \sim \text{constant}$

→ $I_{CQ} = \beta I_{BQ} = \beta(E_C - U_{BE}) / R_B$

- From output:



$E_C = U_{RC} + U_{CE}$

$= I_C R_C + U_{CE}$

→ $U_{CEQ} = E_C - I_{CQ} R_C$


✓ DC load line: Linear equation $U_{CE} = E_C - I_C R_C$

✓ DC load: $R_{DC} = R_C$

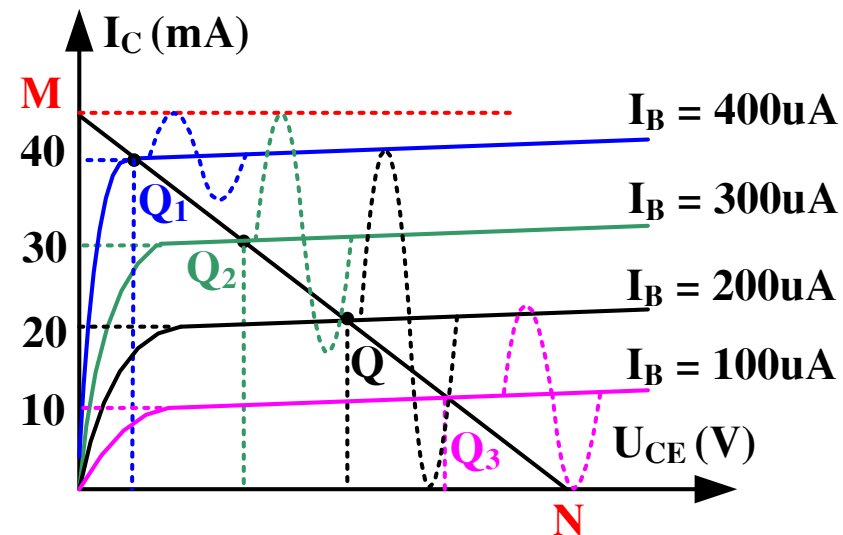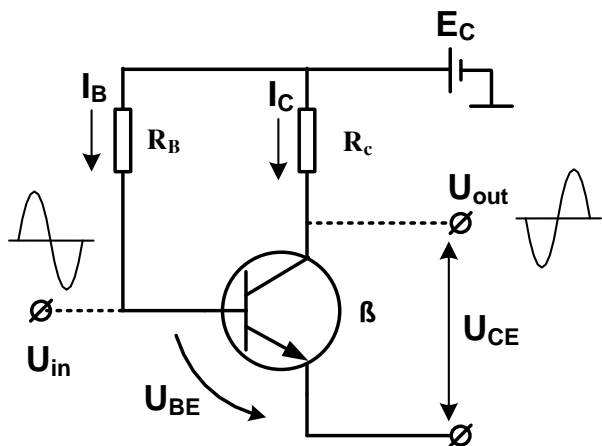

✓ NOTE:

- For best amplification, Q is designed to be at the center of DC load line
- Stability of Q-point

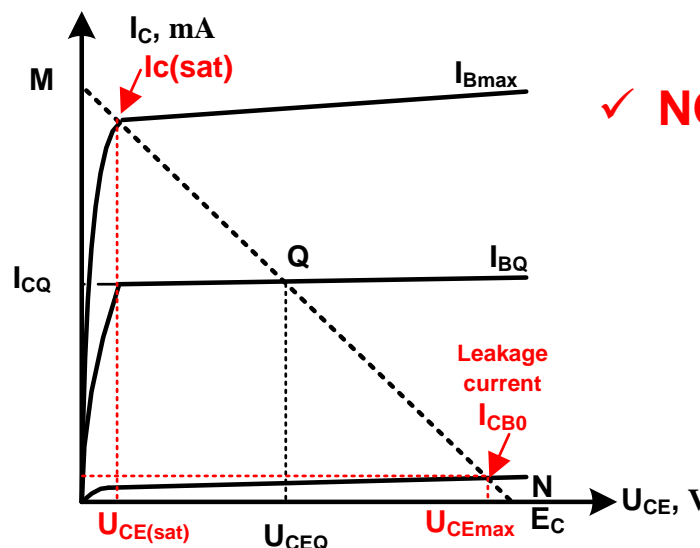


Chapter 2. Semiconductor Devices (Cont.)


Quick test 1: Given a circuit in the figure below.

a) Determine I_B , I_C , I_E , U_{CE} , assuming that $\beta = 200$. Verify whether the transistor operating in amplification mode.

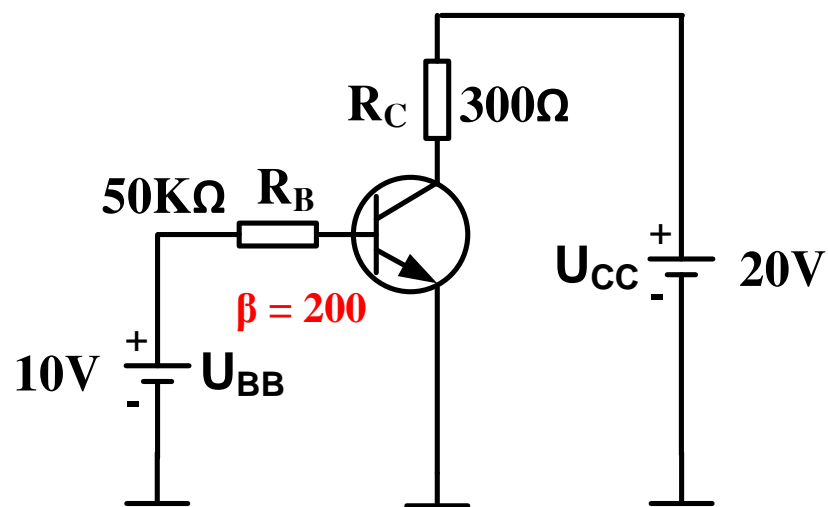b) Determine Q-point, the maximum peak value (variation) of I_B for linear operation, and the DC load line of the transistor.




Quick test 2: $E_C = 12\text{V}$, $R_B = 100\text{K}\Omega$, $R_C = 560\Omega$. Investigate the change of Q-point when 1) β change from 85 to 100 and 2) U_{BE} change from 0.7V to 0.6V. Demonstrate on the output characteristic and DC load line for each case.

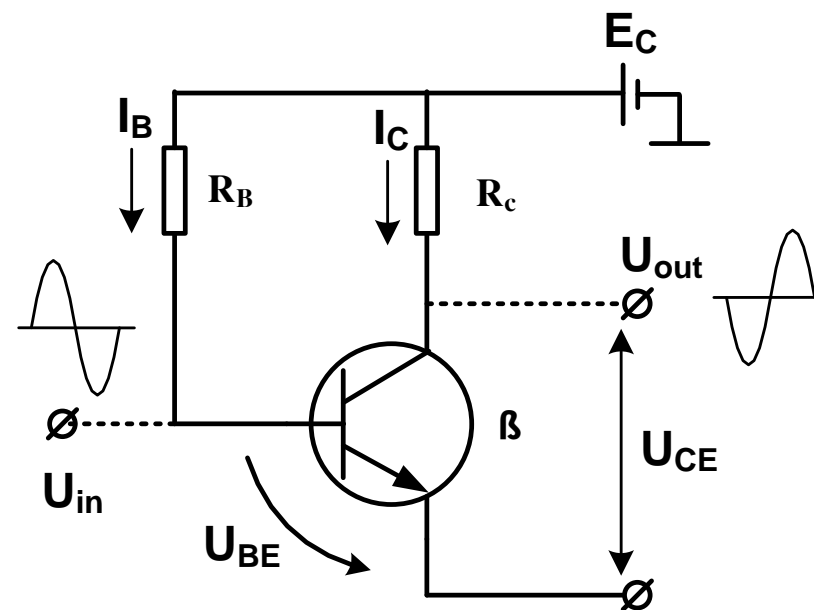

Chapter 2. Semiconductor Devices (Cont.)

b) Feedback (collector) current

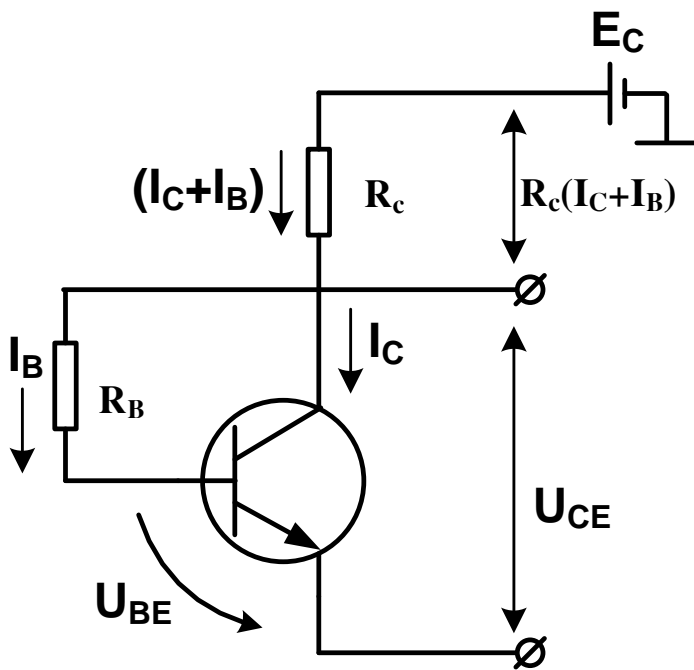

✓ Q-point:

- From input: $E_C = U_{RC} + U_{RB} + U_{BE} = I_B R_B + I_E R_C + U_{BE} = I_B [R_B + (1 + \beta) R_C] + U_{BE}$

$$\Rightarrow I_{BQ} = (E_C - U_{BE}) / [R_B + (1 + \beta) R_C] \sim (E_C - U_{BE}) / (R_B + \beta R_C)$$

$$\Rightarrow I_{CQ} = \beta I_{BQ} = \beta (E_C - U_{BE}) / (R_B + \beta R_C) = (E_C - U_{BE}) / (R_B / \beta + R_C)$$

- From output:

$$E_C = U_{RC} + U_{CE} = (I_B + I_C) R_C + U_{CE} = I_E R_C + U_{CE} \sim I_C R_C + U_{CE}$$

$$\Rightarrow U_{CEQ} = E_C - I_{CQ} R_C$$

✓ DC load line: Linear equation $U_{CE} = E_C - I_C R_C$

✓ Stability of Q-point

✓ DC load: $R_{LDC} = R_C$

Chapter 2. Semiconductor Devices (Cont.)

c) Emitter current (self-bias): Voltage-divider bias – VDB (Single bias source)

- Use of VDB of R_1 - R_2 instead of V_{BB} for input biasing
- If $I_B \ll I_2$: $\Rightarrow I_{R1} = I_{R2} = I_2$; o.w: Equivalent input resistance $R_{IN(base)}$ is investigated


- DC mode analysis:

- From input: $R_{IN(base)} = U_{IN}/I_{IN} = (I_E R_E + U_{BE})/I_B \sim (1+\beta)I_B R_E/I_B \sim \beta R_E$; and $U_{IN} = \beta I_B R_E$
- Total input resistance: $R_{IN(total)} = R_2 // R_{IN(base)} = R_2 // \beta R_E$
- Total input resistance: $U_{IN} = U_B = E_C [R_2 // R_{IN(base)}] / [R_1 + R_2 // R_{IN(base)}]$

If $R_2 \ll R_{IN(base)} \Rightarrow U_{IN} = E_C R_2 / (R_1 + R_2)$

- Q-point:

- $U_E = U_B - U_{BE} \Rightarrow I_E \sim I_{CQ} = (U_E - U_{BE})/R_E \Rightarrow I_{CQ} \sim U_E/R_E \Rightarrow I_{BQ} = I_{CQ}/\beta$
- $U_{CE} = E_C - I_C(R_C + R_E) \Rightarrow U_{CEQ} = E_C - I_{CQ}(R_C + R_E)$
- DC load line equation: $U_{CE} = E_C - I_C(R_C + R_E)$
- $R_{LDC} = R_C + R_E$

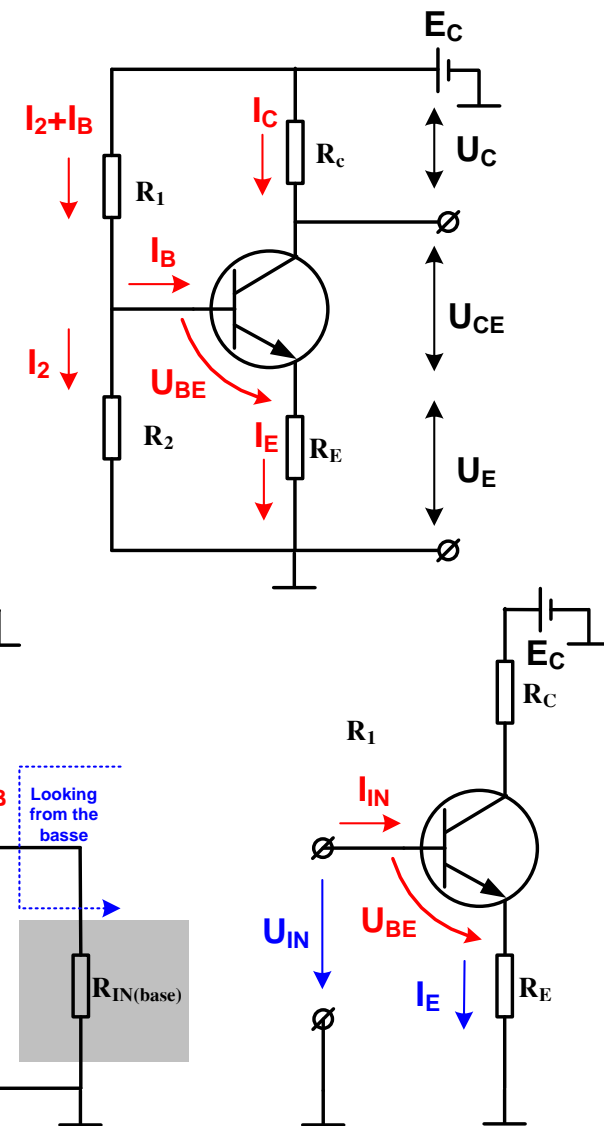

Chapter 2. Semiconductor Devices (Cont.)

- Equivalent Thevenine theorem: $U_{TH} = U_B = E_C R_2 / (R_1 + R_2)$ and $R_{TH} = R_B = R_1 // R_2 = R_1 R_2 / (R_1 + R_2)$
→ utilization of equivalent DC circuit

- Q-point:

- From input loop: $U_B = I_B R_B + U_{BE} + I_E R_E \Rightarrow U_B = I_E / (1 + \beta) R_B + I_E R_E + U_{BE} \Rightarrow I_E \sim (U_B - U_{BE}) / (R_E + R_B / \beta)$

If $R_E \gg R_B / \beta \Rightarrow I_E \sim (U_B - U_{BE}) / R_E$ or $U_E = U_B - U_{BE}$ (proven) $\Rightarrow I_{CQ} \sim I_E \Rightarrow I_{BQ} = I_{CQ} / \beta$: I_E independent from β

- $U_{CE} = E_C - I_C (R_C + R_E) \Rightarrow U_{CEQ} = E_C - I_{CQ} (R_C + R_E)$


- Stability of Q-point: I_E independent to $\beta \Rightarrow$ most stable

In practice: If $R_E \gg R_B / \beta \Rightarrow$ select R_E at least 10 times greater than R_B / β

- d) Emitter bias: Double bias sources E_{CC} and E_{EE} \Rightarrow self reading

- $I_C = (E_{EE} - U_{BE}) / (R_E + R_B / \beta)$


- $U_{CE} = E_{CC} + E_{EE} - I_C (R_C + R_E)$

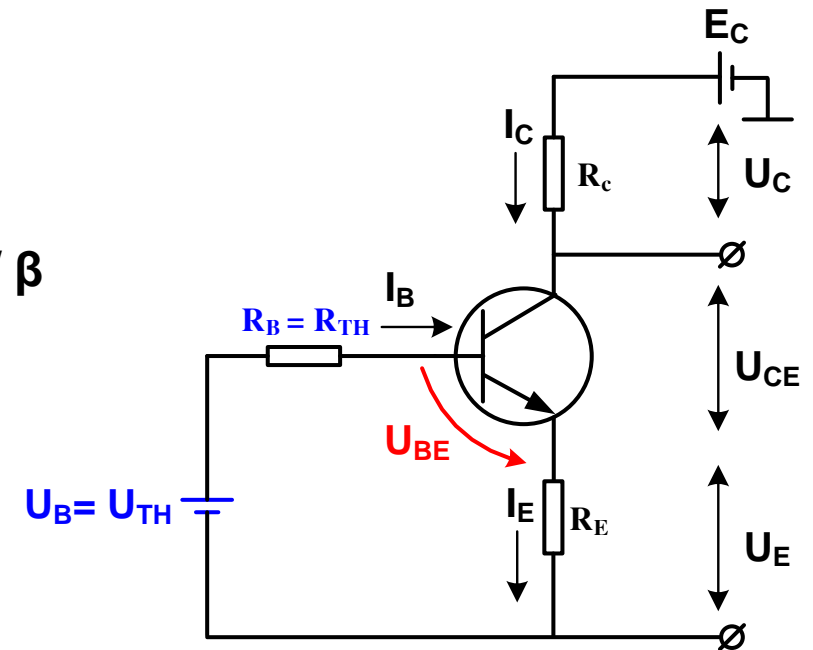

Chapter 2. Semiconductor Devices (Cont.)


Quick test 3: Given a circuit in the figure below.

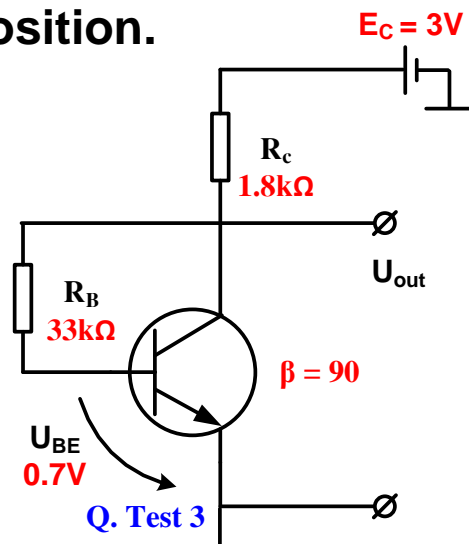Determine DC mode. Investigate the Q-point position.




Quick test 4: Given a circuit in the figure below.

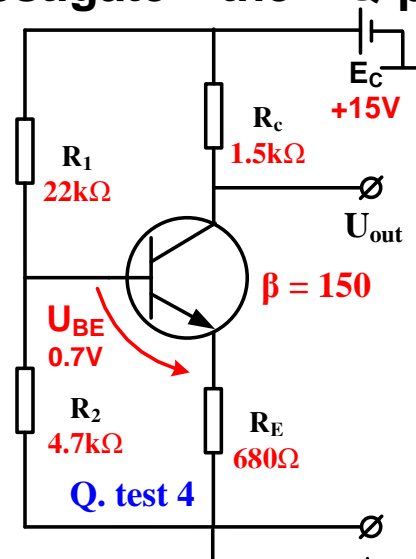- $\beta_{min} = ?$ in order to set up $R_{IN(base)} \gg 10R_2$
- If R_2 is replaced by 15k Ω potentiometer. What is the minimum resistance setting causes saturation?
- Set R_2 at 2k Ω . Determine DC mode.




Quick test 5: Given a circuit in the figure below.

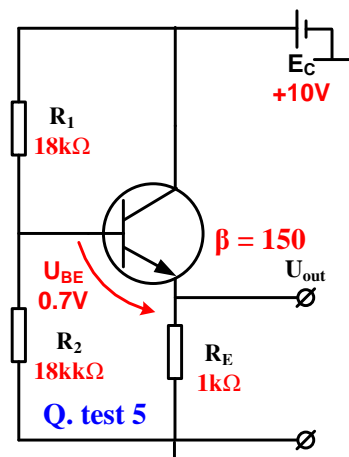- Determine type of amplifier
- Investigate DC mode



Quick test 6: Given a circuit in the figure below.


- Determine type of amplifier
- Investigate DC mode

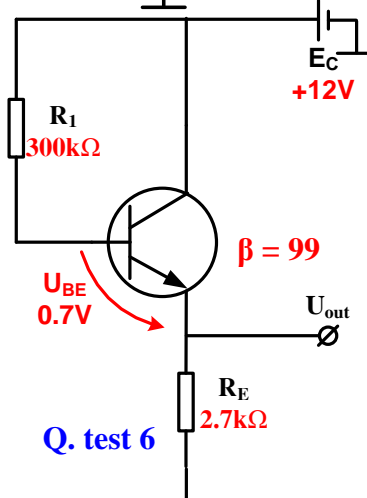

Chapter 2. Semiconductor Devices (Cont.)

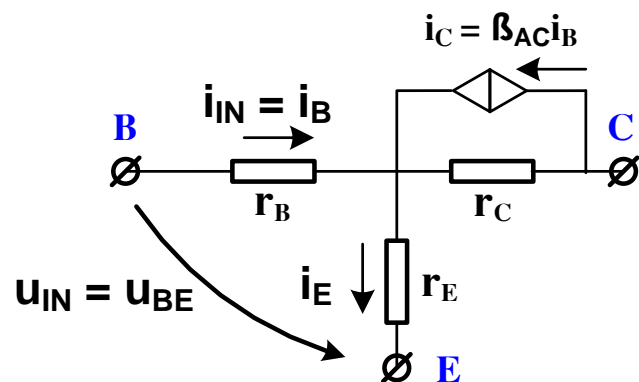2.2.5. BJT amplifier: AC mode

- What is AC mode: AC signal is amplified, once DC mode has been setup
- In AC mode: 1) Voltage gain K_U (or A_U), 2) Current gain K_i (or A_i), 3) AC load
- AC equivalent of a transistor:




- AC input voltage: $u_{IN} = u_{BE} = i_B r_B + i_E r_E = i_B [r_B + (1 + \beta_{AC}) r_E]$
- ➔ AC input resistance: $r_{IN(base)} = u_{IN} / i_{IN} = U_{BE} / i_B = r_B + (1 + \beta_{AC}) r_E$
- r_B : small \rightarrow neglected and replaced by a short
- r_C : large (hundreds $k\Omega$) \rightarrow replaced by an open
- r_E : temperature dependent and $r_E = 0.25mV / I_E$ at $20^\circ C$

a) EC amplifier: voltage divider bias

- C_1, C_2 : capacitively coupled; C_E : bypass
- In AC mode: C_1, C_2, C_E replaced by shorts ($X_C \sim 0$)
- Effect of CE on voltage gain: $X_C \sim 0$ if:

$$\Leftrightarrow 10X_{CE} \leq R_E \Leftrightarrow X_{CE} \leq R_E/10 \Leftrightarrow 1/(\omega C_E) \leq R_E/10$$

$$\rightarrow C_E \geq 10/(2\pi f R_E)$$

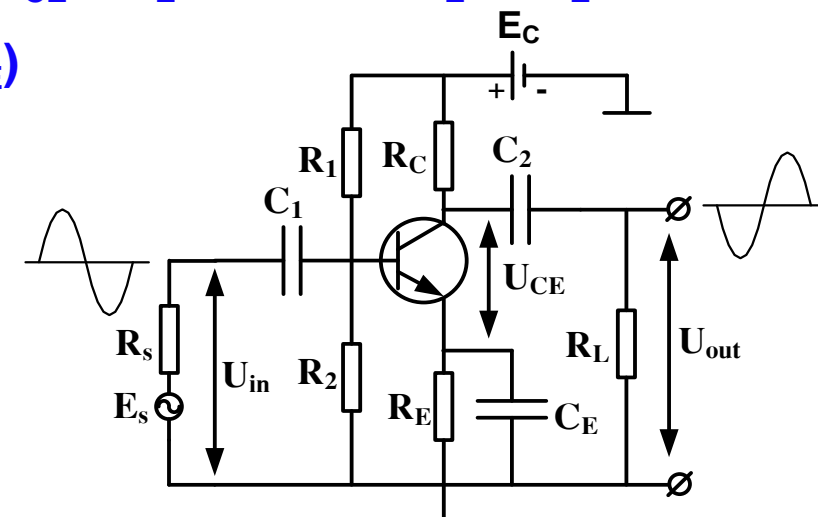

Chapter 2. Semiconductor Devices (Cont.)

- **Example: DC analysis** → Q-point, DC load line, DC load

➤ Don't take into account **AC components**

➤ **Q-point:**

✓ $R_{IN(base)} = \beta R_E = 150 \cdot 560\Omega = 84k \gg 10R_2 = 68k$

✓ $I_{EQ} = (U_B - U_{BE})/R_E$, where $U_B = E_C R_2 / (R_1 + R_2) = 2.83\text{ V}$

→ $I_{CQ} \sim I_{EQ} = (2.83\text{V} - 0.7\text{V})/560 = 3.8\text{ mA} \rightarrow I_{BQ} = I_{CQ}/\beta = 25.33\text{ }\mu\text{A}$


✓ $U_{CEQ} \sim E_C - I_C(R_C + R_E) = 12\text{V} - 3.8\text{mA} (1k + 560) = 6.07\text{V}$

➤ **DC load line equation:** $U_{CEQ} \sim E_C - I_C(R_C + R_E)$; $R_{DCLoad} \sim R_C + R_E$

- **Example:** If input signal with frequency $f > 2\text{kHz}$. Determine by C_{Emin} so that R_E is shorten

➤ R_E shorten = 0 → $R_E \gg 10X_{CE}$ since $R_E // X_{CE}$, where $X_{CE} = 1/(\omega C_E) = 1/(2\pi f C_E)$ is reactance of C_E




➤ $X_{CE} < 56 \rightarrow 1/(2\pi f C_E) < 56 \rightarrow C_E > 1/(2\pi f \cdot 56) = 1.42\text{ }\mu\text{F} \rightarrow C_{Emin} = 1.42\text{ }\mu\text{F}$

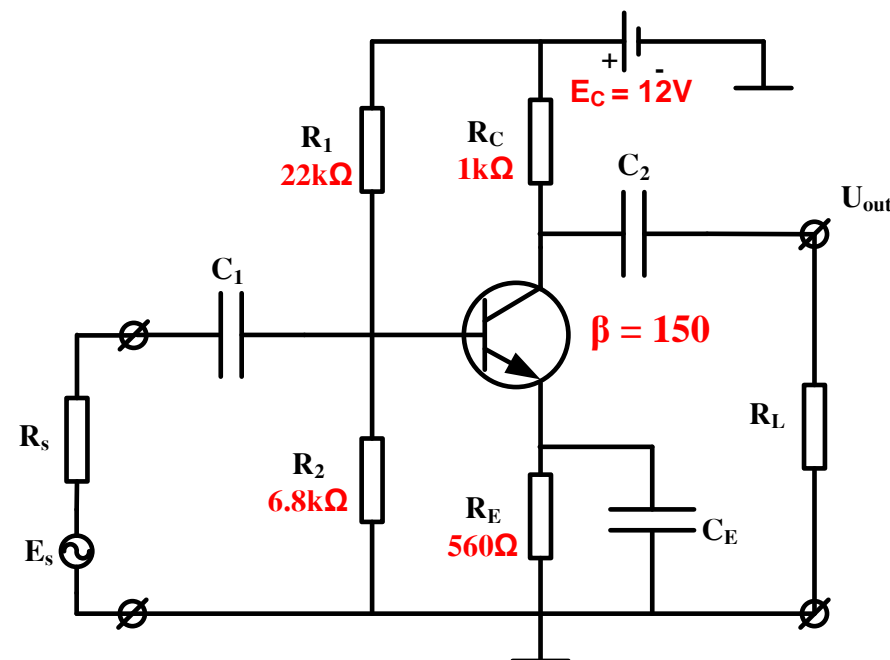

Chapter 2. Semiconductor Devices (Cont.)

- **AC analysis:** K_u , K_i , AC load

- AC equivalent:

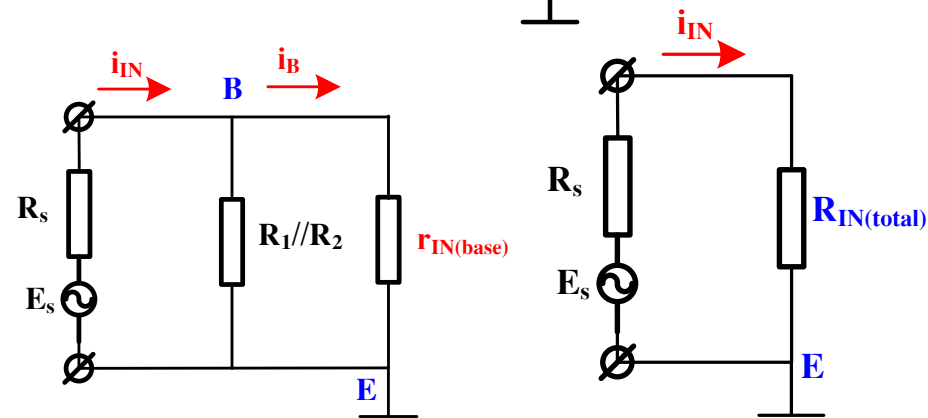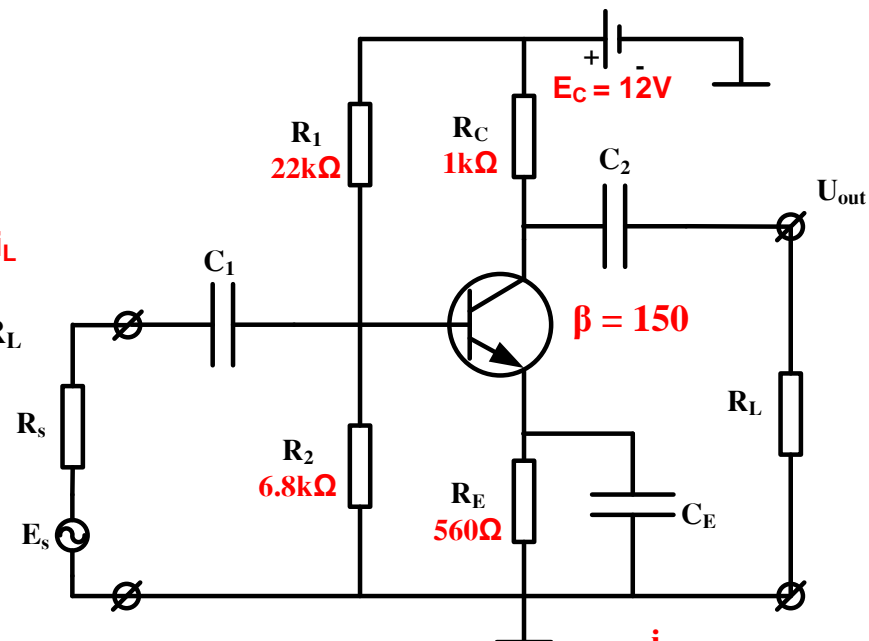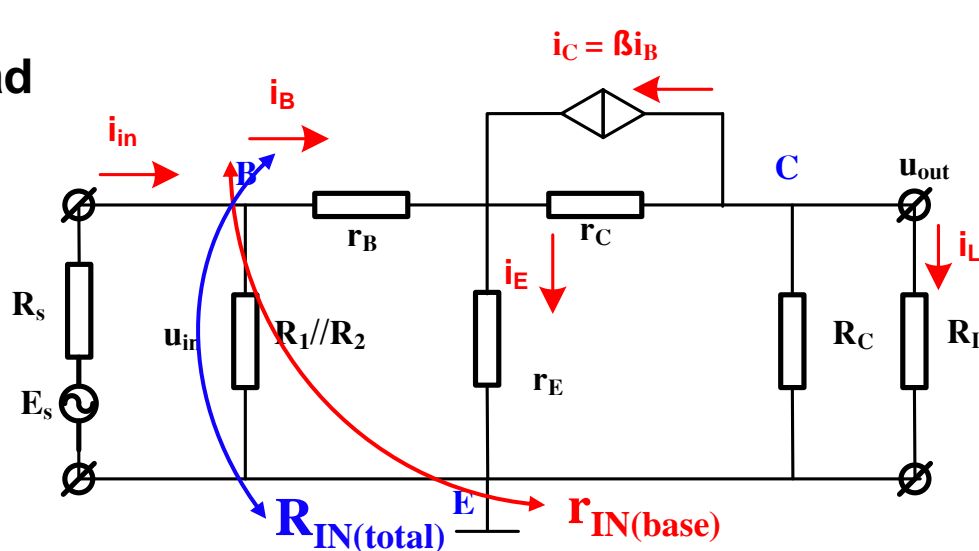

- Input resistance of transistor at the base: $r_{IN(base)}$

$$r_{IN(base)} = U_{BE}/i_B = [i_B r_B + (1 + \beta_{AC}) i_B r_E] / i_B = r_B + (1 + \beta_{AC}) r_E \sim \beta_{AC} r_E$$

- Input resistance of amplifier: $R_{IN(total)} = R_1 // R_2 // r_{IN(base)} = R_1 // R_2 // \beta_{AC} r_E$

- Voltage gain (with R_L): $K_u = u_{out} / u_{IN}$

$$u_{IN} = i_{IN} (R_s + R_{in(total)}) \sim I_B (R_s + R_{IN(total)}), \text{ assuming } R_1 // R_2 \gg r_{IN(base)}$$

$$u_{out} = i_L R_L = I_C R_C R_L / (R_L + R_C) = \beta_{AC} I_B (R_L // R_C) \Rightarrow K_u = u_{out} / u_{IN} = \beta_{AC} (R_L // R_C) / (R_s + R_{IN(total)})$$


Chapter 2. Semiconductor Devices (Cont.)

- Investigate without R_L : $K_u = \beta_{AC}(R_L // R_C) / (R_s + R_{IN(total)}) \sim \beta_{AC}R_C / (\beta_{AC}r_E) = R_C / r_E$
- Since $(R_C // R_L) < R_C \rightarrow K_u$ reduced; If $R_L \gg R_C$, $(R_C // R_L) \sim R_C \rightarrow R_L$ no effect on gain
- In practice: attenuation from source to base $\rightarrow U_B/E_s = R_{IN(total)} / (R_s + R_{IN(total)})$
 $\rightarrow K'_u = (U_B/E_s)K_u$

- Current gain: $K_i = i_{out} / i_{IN}$, where $i_{IN} \sim i_B$

$$i_{out} = i_L = I_C R_C / (R_L + R_C) = \beta_{AC} i_B (R_L // R_C) / R_L \rightarrow K_i = i_{out} / i_{IN} = \beta_{AC} (R_L // R_C) / R_L$$

- AC load: $R_{LAC} = R_C // r_c$, however in fact $r_c \gg R_C \rightarrow R_{LAC} \sim R_C$

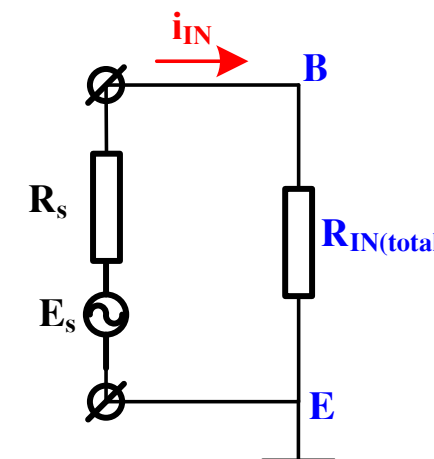

Chapter 2. Semiconductor Devices (Cont.)

- Example:** Given a circuit, R_E is partially bypassed by $C_E \rightarrow R_{in(base)} = \beta_{AC}(r_E + R_{E1})$


a) Determine DC I_C , U_C

➤ Since $R_{IN(base)} = \beta(R_{E1} + R_{E2}) = 150 \times 0.94k = 141k > 10R_2 = 100k$

➤ $I_C \sim I_E = (U_B - U_{BE})/(R_{E1} + R_{E2})$; $U_B = E_C R_2/(R_1 + R_2) = 1.75V \rightarrow I_{CQ} = 1.12mA$

➤ $U_C \sim E_C - I_C R_C = 4.74V$

➤ $I_{BQ} = I_{CQ}/\beta = 7.47\mu A$

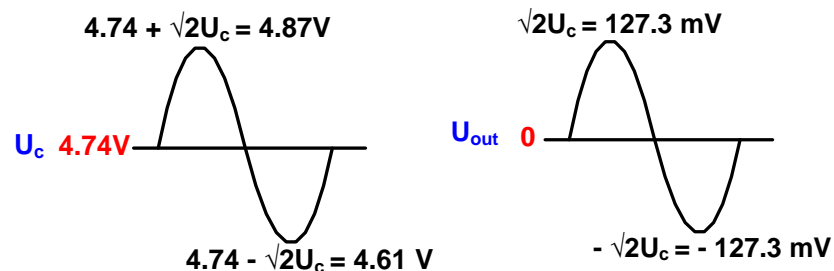

b) Determine AC i_c , u_c

➤ With C_2 : $R_{IN(base)} = \beta_{AC}(r_E + R_{E1})$, and $r_E = 25mV/I_E = 22\Omega \rightarrow R_{IN(base)} = 86k$


➤ $K_u = \beta_{AC}(R_L // R_C)/(R_s + R_{IN(total)}) \sim \beta_{AC}(R_L // R_C)/\beta_{AC}(r_E + R_{E1}) = (R_L // R_C)/R_{E1}$ and $R_L // R_C = 4.27k \rightarrow K_u \sim 9.09$

$\rightarrow U_c = K_u E_s = 9.09 \times 10mV = 90mV$ and $R_{IN(total)} = R_1 // R_2 // r_{IN(base)} = 8.24k // 86k = 7.53k$

With attenuation: $U_b = [R_{IN(total)}/(R_s + R_{IN(total)})] E_s$ and $U'_c = [(U_b/E_s) K_u] E_s \rightarrow U'_c = 0.93 \times 9.09 \times 10mV = 84.5mV$

➤ $K_i = \beta_{AC}(R_L // R_C)/R_L = 175 \times 4.27k/47k = 15.9 \rightarrow i_c = K_i I_s = K_i E_C/(R_s + R_{IN(total)}) = 15.9 \times 10V/7.53k = 21.11mA$


c) Draw total input and output signals in two cases

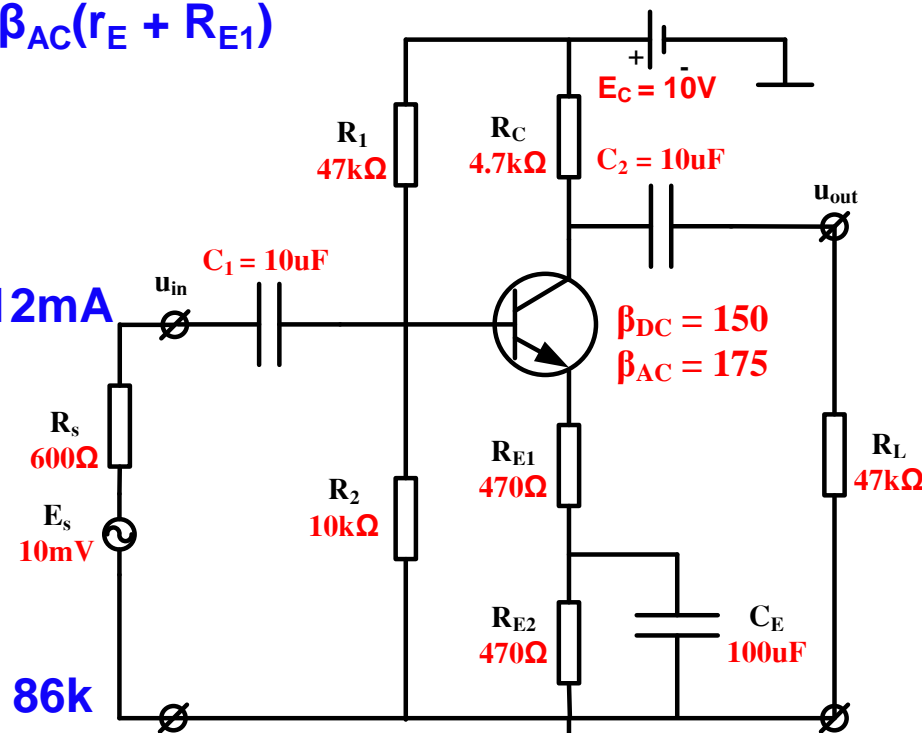

Chapter 2. Semiconductor Devices (Cont.)

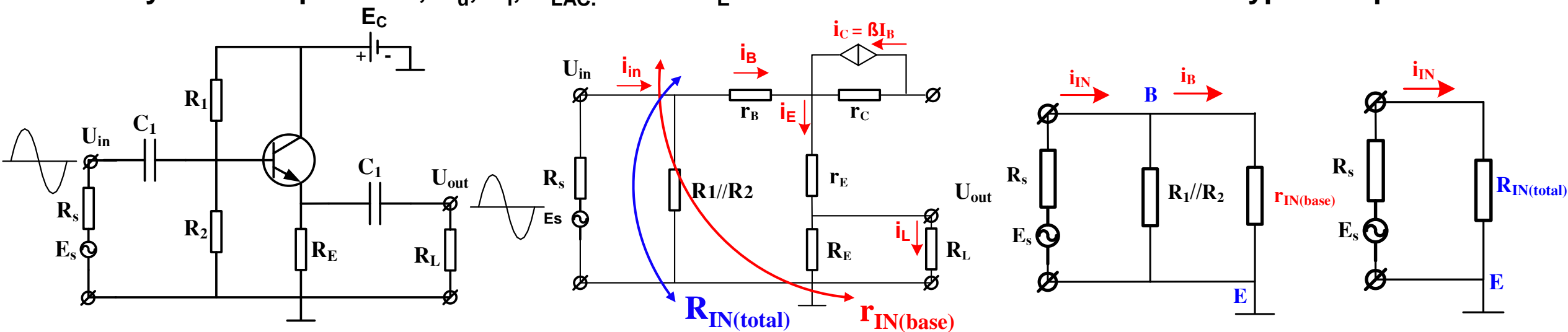b) CC amplifier:

- DC analysis: Q-point, DC load line, R_{LDC}
- AC analysis: AC equivalent, K_u , K_i , R_{LAC} . **Note:** R_E still included in AC mode since no bypass capacitor



- Input resistance to the base: $r_{IN(base)} = r_B + (1 + \beta_{AC})(r_E + R_E // R_L)$. If $r_B \ll \rightarrow r_{IN(base)} \sim (1 + \beta_{AC})(r_E + R_E // R_L)$
- Input resistance of amplifier: $R_{IN(total)} = R_1 // R_2 // r_{IN(base)}$. If $R_1 // R_2 \gg r_{IN(base)} \rightarrow R_{INtotal} \sim r_{INbase}$
- Voltage gain $K_u = (1 + \beta_{AC})(R_E // R_L) / (R_s + R_{INtotal})$. If $R_s = 0$, $r_E \ll R_E // R_L \rightarrow K_u \sim 1 \rightarrow$ **No voltage amplification**
- Current gain: $K_i = i_{out} / i_{IN} = i_E / i_{IN} = [u_{out} / (R_E // R_L)] / (U_{in} / R_{IN(total)})$; AC load $R_{LAC} = R_E // r_E$

Chapter 2. Semiconductor Devices (Cont.)

- **Example:** Determine the DC mode of CC amplifier. Find K_u , K_i , $K_p = K_u K_i$, R_{ACLoad} , $R_{IN(total)}$, R_{out} .

➤ **DC mode:** By yourself

- ✓ $Q (I_{BQ}, I_{EQ}, U_{CEQ}) = (28.67\mu A, 4.3mA, 5.7V)$
- ✓ DC load line equation: $U_{CE} = E_C - I_E R_E$; $R_{LoadDC} = R_E = 1k$

➤ **AC mode:**


- ✓ $K_u = (1 + \beta_{AC})(R_E // R_L) / (R_s + R_{IN(total)}) \rightarrow K_u \sim (R_E // R_L) / (r_E + R_E // R_L)$
- ✓ $r_E \sim 25mV / I_E = 5.8 \Omega$; $R_E // R_L = 0.5k$; $r_{IN(base)} = (1 + \beta_{AC})(r_E + R_E // R_L) = 87.5k$
- ✓ $R_{IN(total)} = R_1 // R_2 // r_{IN(base)} \sim 9k // 87.5k = 8.16k$

- ✓ $K_u \sim (R_E // R_L) / (r_E + R_E // R_L) = 0.5k / 508.8 \Omega \sim 0.989$

➤ $K_i = i_E / i_{IN} = [u_{out} / (R_E // R_L)] / (U_{in} / R_{IN(total)})$


- ✓ $u_{out} / (R_E // R_L) = K_u u_{in} / (R_E // R_L) = 1mV / 0.5k = 2\mu A$; $u_{in} / R_{IN(total)} = 1mV / 8.16k = 0.122 \mu A \rightarrow K_i = 2 / 0.122 = 16.39$

➤ $K_p = K_u K_i = 0.989 \times 16.39 = 16.21$; $R_{ACLoad} = R_E // R_L = 0.5k \rightarrow$ **Power dissipated on $R_L = 1/2 K_p = 8.1$**

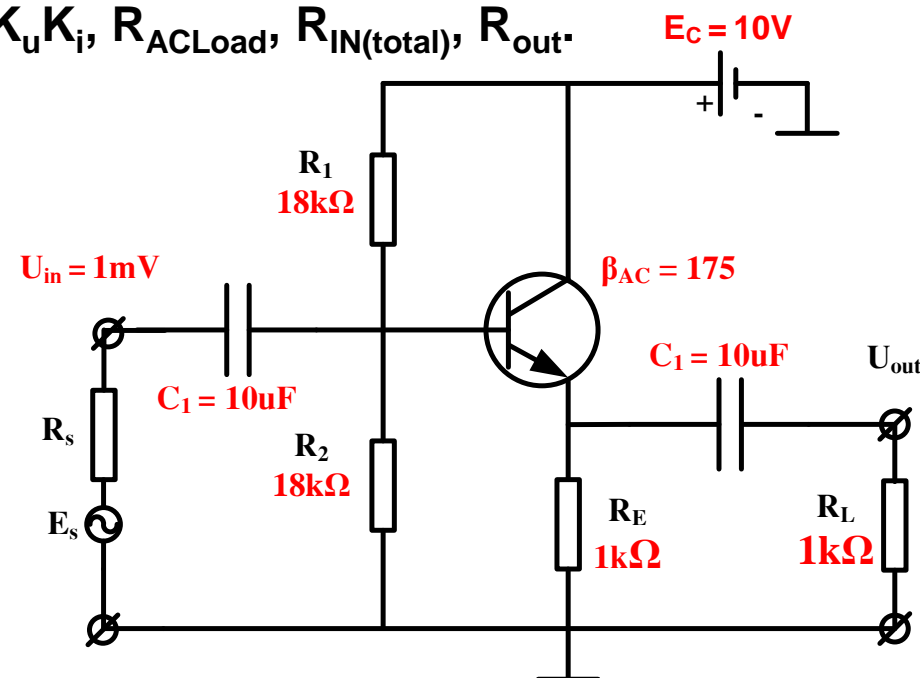

Chapter 2. Semiconductor Devices (Cont.)



- Darlington pair: for greater input resistance
- Effective current gain: $\beta_{AC} = \beta_{AC1}\beta_{AC2}$
- If $r_E \ll R_E \rightarrow R_{IN} = \beta_{AC}R_E$

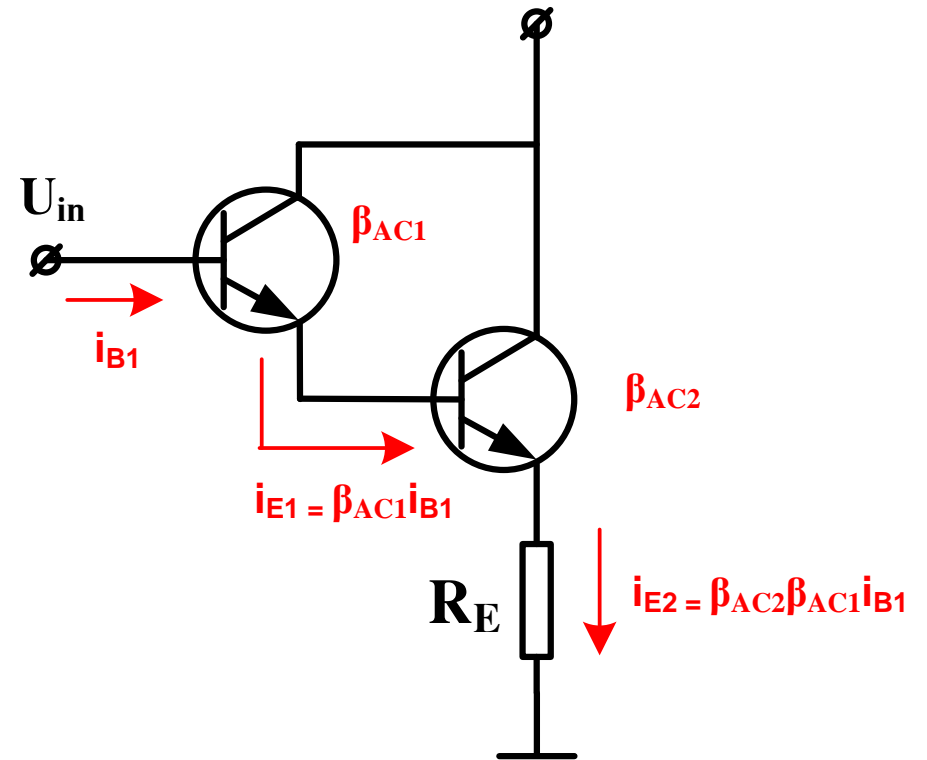

Chapter 2. Semiconductor Devices (Cont.)

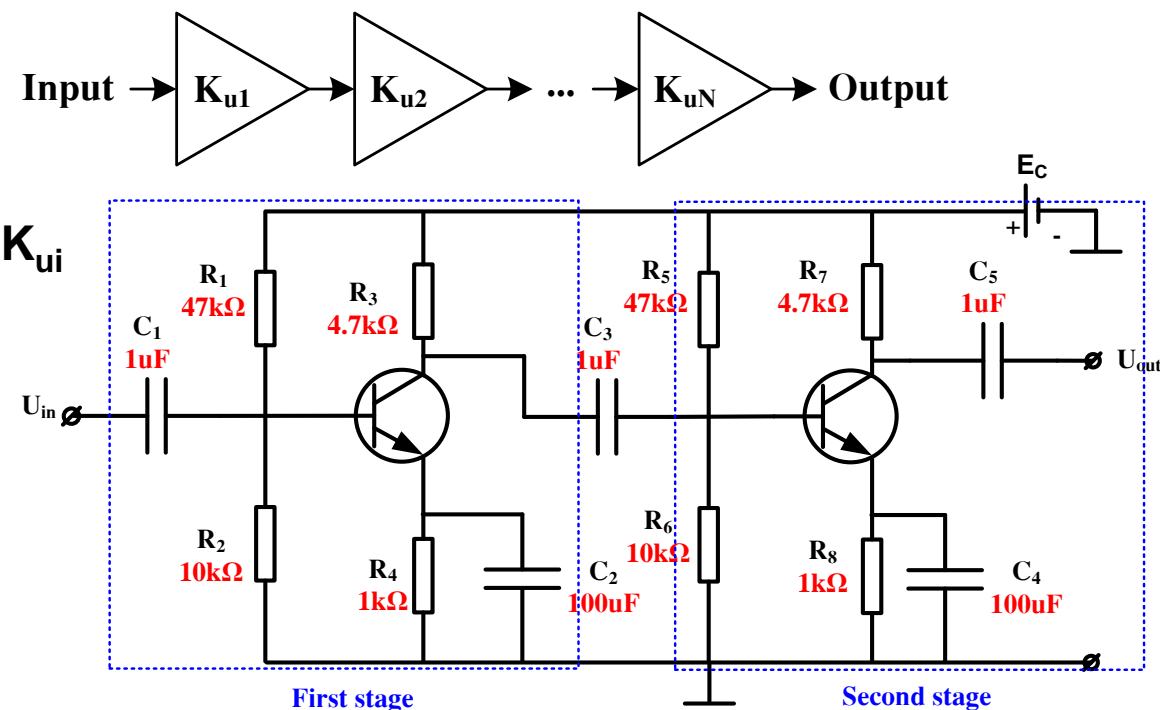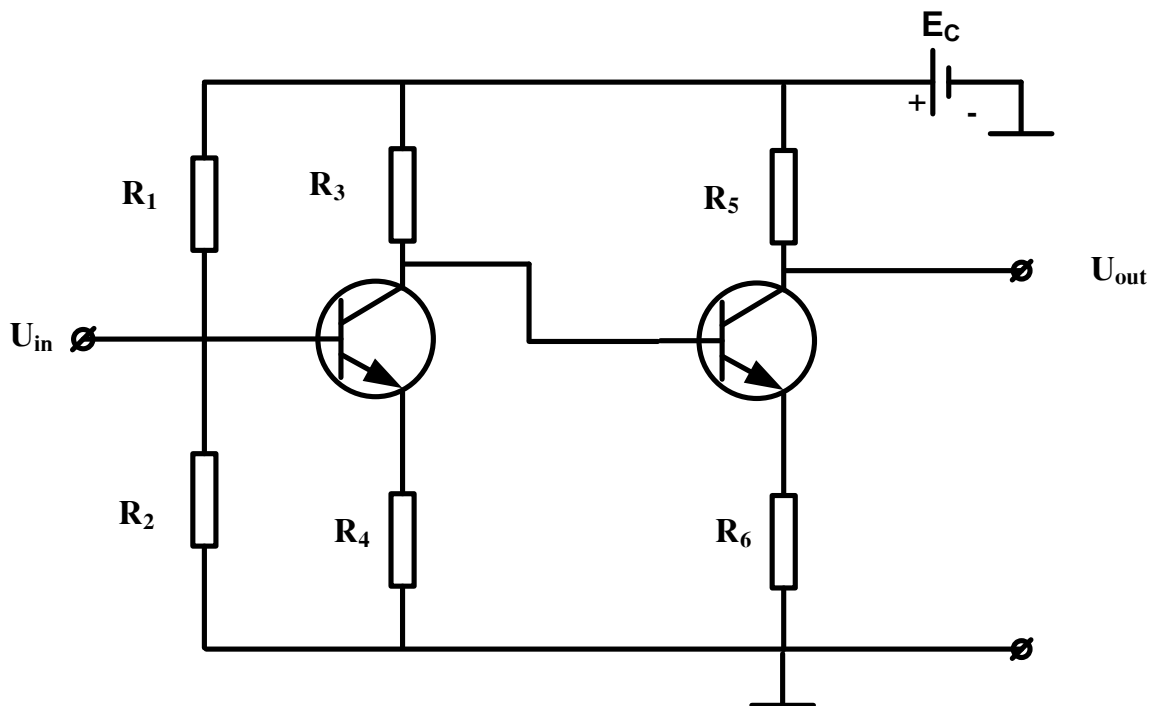2.2.6. Multistage amplifier

- Cascade arrangement for greater voltage gain
- Overall gain: $K_u = K_{u1} K_{u2} \dots K_{uN}$. In decibels: $K_{ui, (DB)} = 20 \log K_{ui}$
- Overall gain in DB: $K_{u, DB} = K_{u1, DB} + K_{u2, DB} + \dots K_{uN, DB}$
- Capacitively coupled amplifier



- Direct-coupled amplifier:
 - ✓ Better low-frequency response
 - ✓ If using C, very high R_{IN}
 - ✓ R_{in} high reduces gain

Chapter 2. Semiconductor Devices (Cont.)

2.1. PN Junction - Diode and application

2.2. Bipolar Junction Transistor (BJT) and applications

2.3. Operational amplifier (OPAM) and applications

2.4. Voltage regulation

Chapter 2. Semiconductor Devices (Cont.)

2.3.1. Differential amplifier

- 2 EC amplifiers with 2 bias sources
- Multistage differential amplifiers + push-pull \rightarrow OPAM: operational amplifier
- $\Delta U_{\text{out}} = U_{\text{out2}} - U_{\text{out1}} = K_{\text{diff}} \Delta I_{\text{in}}$
or $\Delta U_{\text{out}} = K_{\text{diff}} (U_{\text{in2}} - U_{\text{in1}})$



✓ If $U_{\text{in1}} = 0$ (grounded): $\Delta u_{\text{out}} = K_{\text{diff}} U_{\text{in2}}$.

If U_{out1} grounded $\rightarrow U_{\text{out2}} = K_{\text{diff}} U_{\text{in2}} \rightarrow U_{\text{in1}}$: Non-inverse input (P)

✓ If $U_{\text{in2}} = 0$ (grounded): $\Delta u_{\text{out}} = -K_{\text{diff}} U_{\text{in1}}$.

If U_{out1} grounded $\rightarrow U_{\text{out2}} = -K_{\text{diff}} U_{\text{in1}} \rightarrow U_{\text{in1}}$: Inverse input (N)

- Input resistance: very large; Output resistance: very small
- Amplifier gain: $K_{\text{OPAM}} = 10^4 - 10^6$ (ideal: infinity)

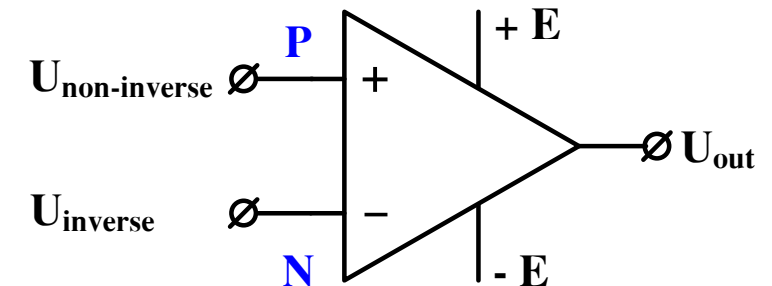
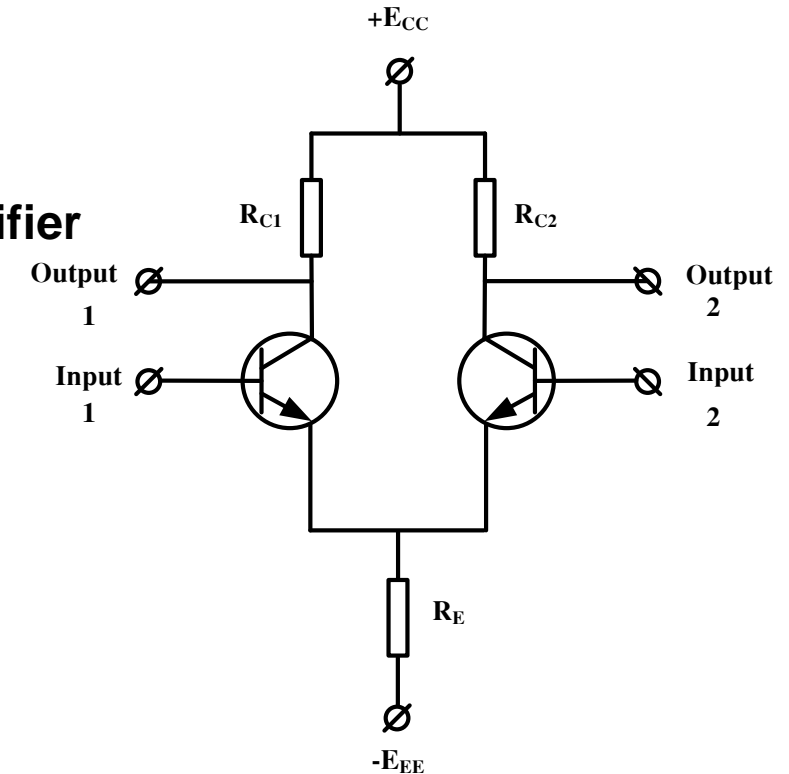


Chapter 2. Semiconductor Devices (Cont.)

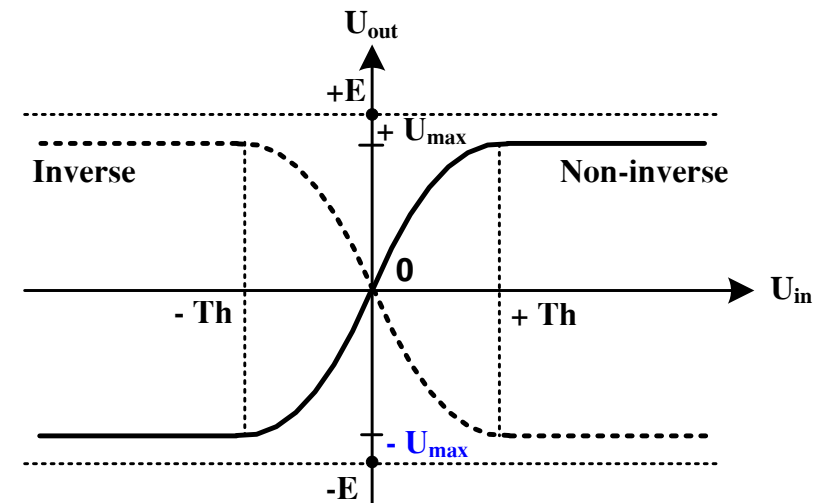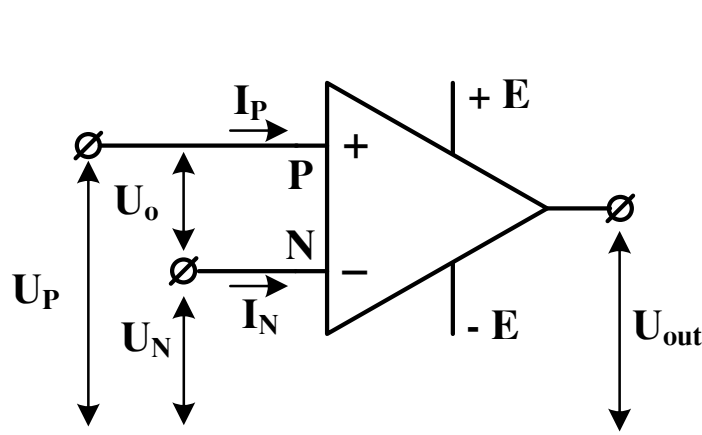2.3.2. OPAM

- **Ideal OPAM:**

- ✓ If $U_{in} = 0$, $U_{out} = K_{OPAM} U_{in} = 0$
- ✓ $R_{in} = \infty$ (open); $R_{out} = 0$ ()
- ✓ $K_{OPAM} = \infty$
- ✓ $U_P - U_N = U_{out}/K_{OPAM} = 0 \Rightarrow U_P = U_N$
- ✓ $I_P = I_N = 0$ (small base currents at inputs)



- **Practical OPAM**


- ✓ $U_{out} \neq 0$ when $U_{in} = 0 \Rightarrow$ Define Input offset voltage U_{os} (differential DC inputs) to force $U_{out} = 0$
- ✓ $I_{BIAS} = (I_P + I_N)/2 \Rightarrow$ DC current required by the inputs
- ✓ Input offset current I_{os} : base currents at input of OPAM are not always equal
- **Transfer characteristic: relation between input and output \Rightarrow inverse and non-inverse characteristic**
 - ✓ $+U_{max}/-U_{max}$: Max/min achievable output value (saturated output)
 - ✓ Linear amplification and saturation

Chapter 2. Semiconductor Devices (Cont.)

2.3.3. Applications of OPAM

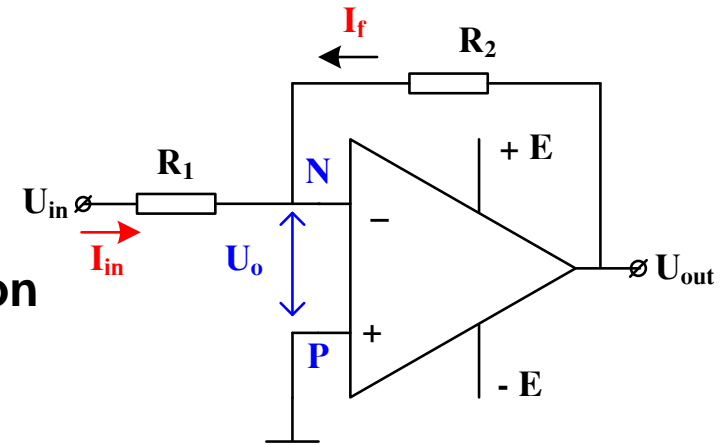
a) Inverting amplifier: Input resistor R_1 , feedback resistor R_2

- **Negative feedback:** Since KOPAM large \rightarrow NF to avoid saturation
- **Node N:** $I_{in} + I_f = 0$ (applying KCL, assuming $I_N = 0$)
- Ohm law: $I_{in} = (U_{in} - U_N)/R_1$; $I_f = (U_{out} - U_N)/R_2$. Since $U_N = U_P = 0$ (Ideal OPAM) $\rightarrow U_{out} = - (R_2/R_1)U_{in}$
- **Negative sign:** Input and output signals **out-of-phase**



b) Non-Inverting amplifier: Input resistor R_1 , feedback resistor R_2

- **Negative feedback**
 - **Node N:** $U_N = R_1/(R_1 + R_2)U_{out} = U_P = U_{in}$
- $\rightarrow U_{out} = + R_1/(R_1 + R_2)U_{in}$
- **Positive sign:** Input and output signals **in-phase**

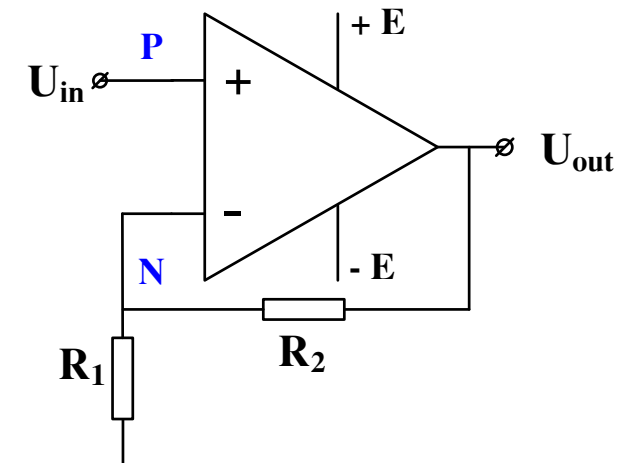


Chapter 2. Semiconductor Devices (Cont.)

Example 1

Add VR_2 – a potentiometer $120\text{ K}\Omega$ to inverting amplifier. $U_{\max} = \pm 12\text{ V}$ $R_1 = 1.5\text{ K}\Omega$, $R_2 = 3.3\text{ K}\Omega$

a) Derive equation for K_u

b) If $U_{\text{in}} = 200\text{mV}$, $V_R = ?$ for linear operation

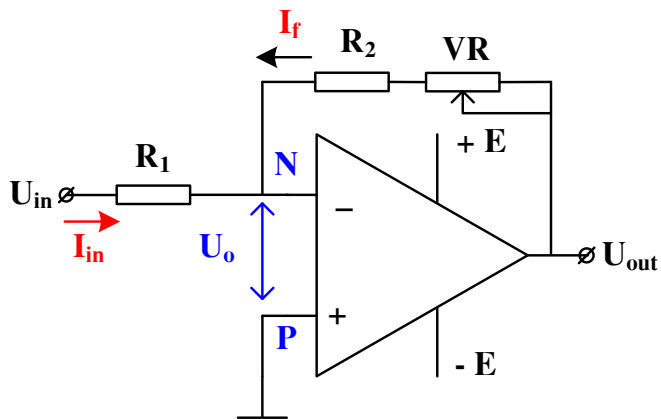


Example 2

Replace $R_2 = VR_2$ - potentiometer $120\text{ K}\Omega$. $U_{\max} = \pm 12\text{ V}$ $R_1 = 1.5\text{ K}\Omega$, $R_2 = 3.3\text{ K}\Omega$

a) Derive equation for K_u

b) If $U_{\text{in}} = 200\text{mV}$, $V_R = ?$ when saturation occurs

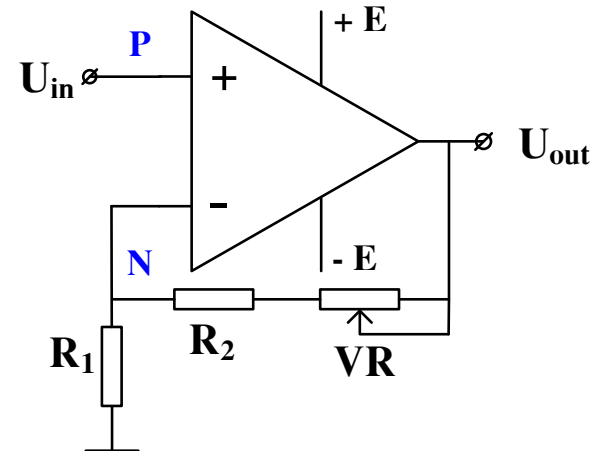


Chapter 2. Semiconductor Devices (Cont.)

c) Inverse summing amplifier

- **Negative feed back**
- **Node N:** $I_1 + I_2 = I_f$ (applying KCL, assuming $I_N = 0$)
- **Ohm Law:**

$$I_1 = (U_1 - U_N)/R_1; I_2 = (U_2 - U_N)/R_2; I_f = (U_{out} - U_N)/R_f$$
- Since $U_N = U_P = 0$ (ideal OPAM)
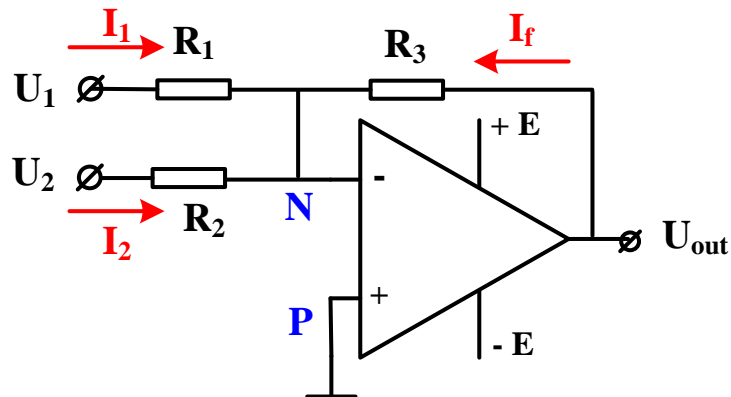
$$\Rightarrow U_{out} = - (R_f/R_1)U_1 - (R_f/R_2)U_2$$
- If $R_1 = R_2 = R_f \Rightarrow U_{out} = - (U_1 + U_2)$




d) Non-inverse summing amplifier

- **Negative feed back**
- **Node N:** $U_N = U_{out}R_1/(R_1 + R_2)$
- **Node P:** $I_1 = (U_1 - U_P)/R; I_2 = (U_2 - U_P)/R$ and $I_1 + I_2 = 0$

$$\Rightarrow U_P = 1/2(U_1 + U_2)$$
- **Since:** $U_N = U_P = U_{out}R_1/(R_1 + R_2)$
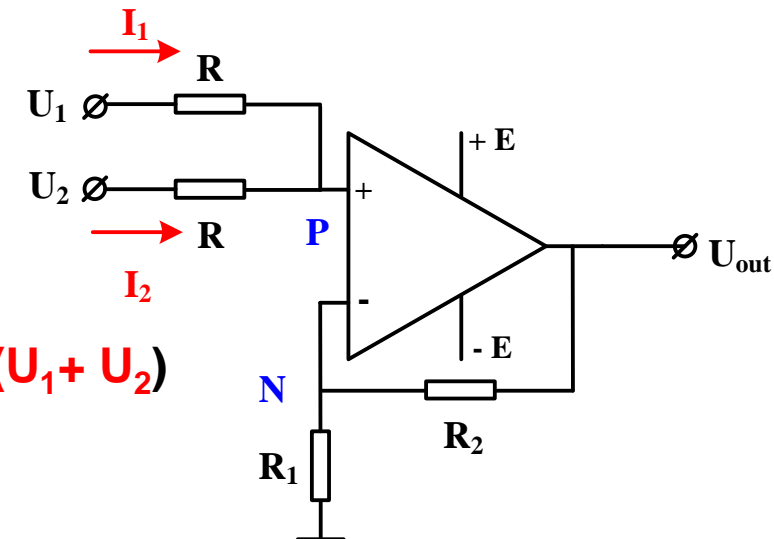
$$\Rightarrow U_{out} = [(R_1 + R_2)/(2R_1)](U_1 + U_2)$$




- If $R_1 = R_2 \Rightarrow U_{out} = (U_1 + U_2)$

Chapter 2. Semiconductor Devices (Cont.)

e) Subtracting amplifier:


- Negative feed back
- **Node N**: $I_1 = (U_1 - U_N)/(aR_a)$; $I_f = (U_N - U_{out})/R_a$, and $I_1 - I_f = 0$ or $I_1 = I_f$
 $\Rightarrow U_N = (aU_{out} + U_1)(a+1)$
- **Node P**: $U_P = U_2R_b/(R_b + bR_b) = U_2/(b+1)$
- Since $U_N = U_P$: $U_{out} = (a + 1)/[a(b + 1)]U_2 - U_1/a$
- If $(a = b)$: $U_{out} = 1/a(U_2 - U_1)$; and if $a = b = 1 \Rightarrow U_{out} = U_2 - U_1$

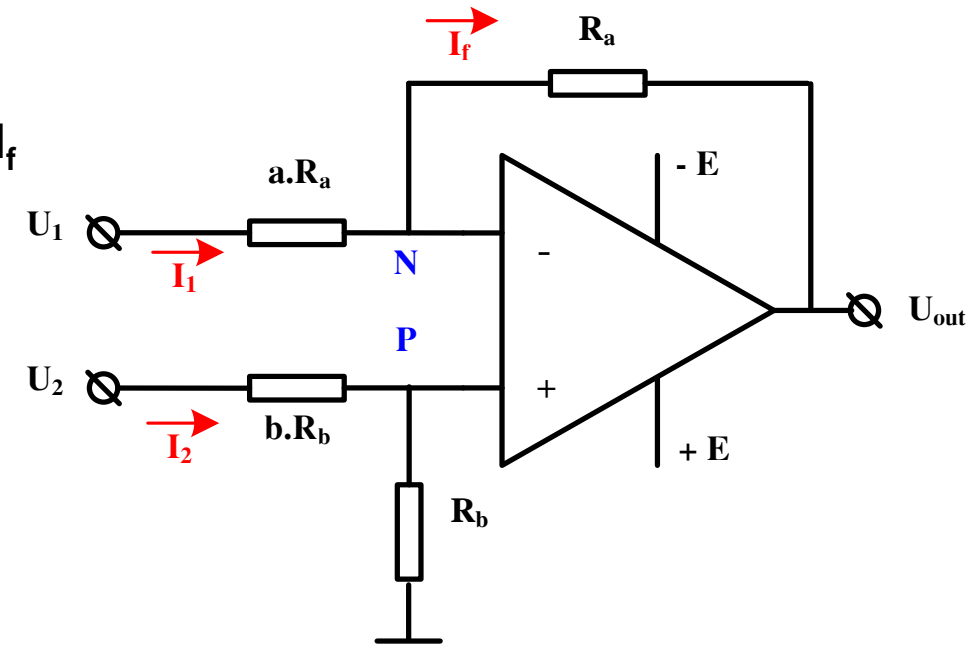


Chapter 2. Semiconductor Devices (Cont.)

Quick test 9

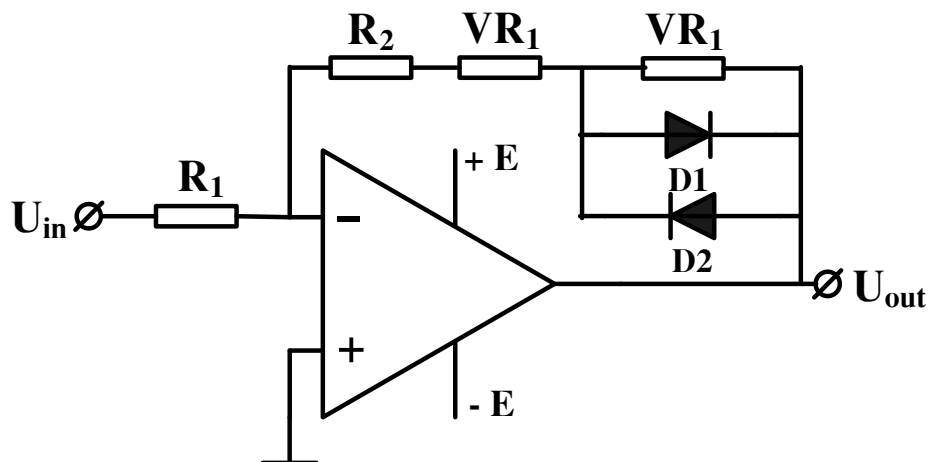Explain the effect of D1, D2 added to an inverting amplifier given below




Quick test 10: Demonstrate output DAC (Digital to Analog Converter) for 4-digit sequence given in waveforms of inputs D_0, D_1, D_2, D_3

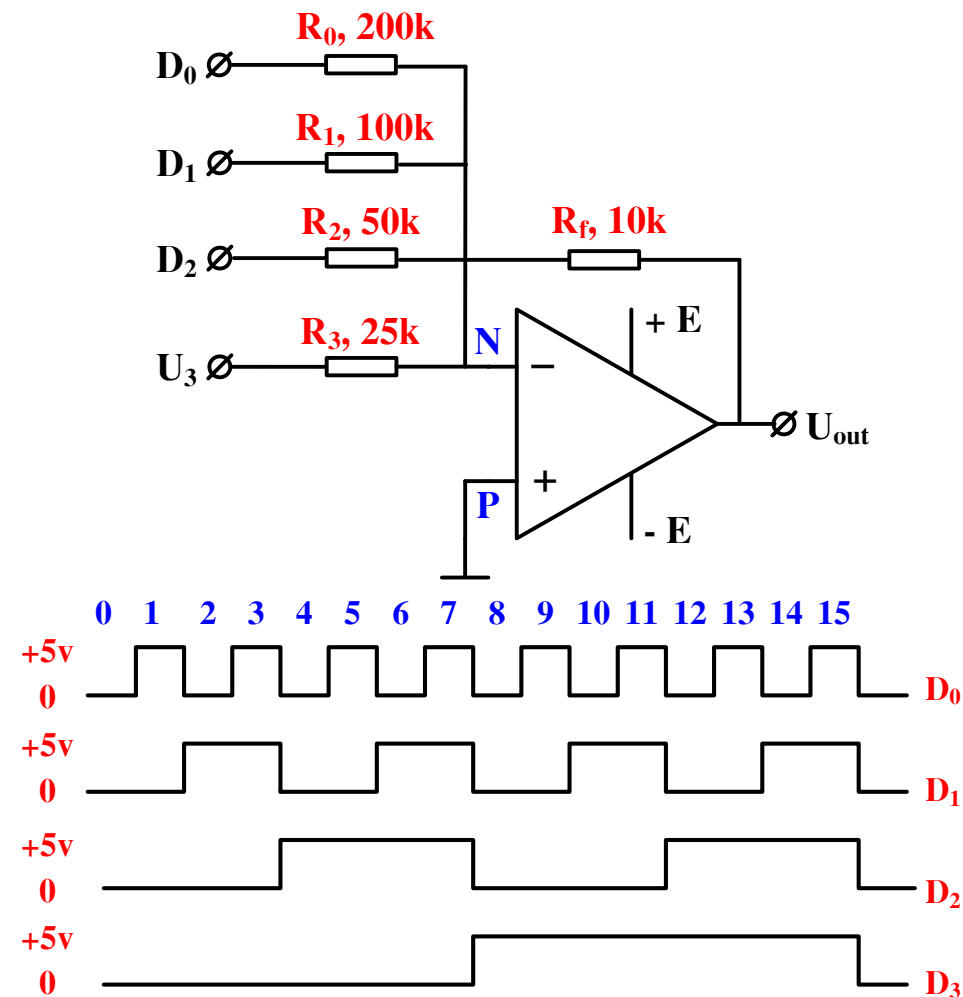

Chapter 2. Semiconductor Devices (Cont.)

Quick test 11

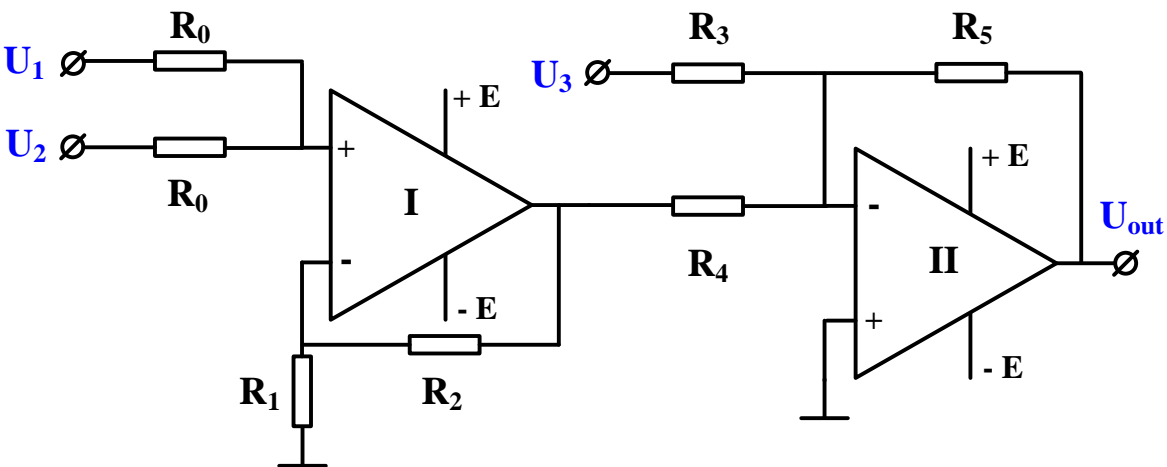
Establish relation between output U_{out} and inputs U_1 , U_2 , U_3 according to given circuit's elements



Quick test 12

- a) Establish relation between output U_{out} and inputs U_1 , U_2 , U_3 according to given circuit's elements
- b) Determine R_2 , R_4 , R_5 for getting this equation:


$$U_{out} = 2.5U_1 + 4.7U_2 - 4.1U_3$$

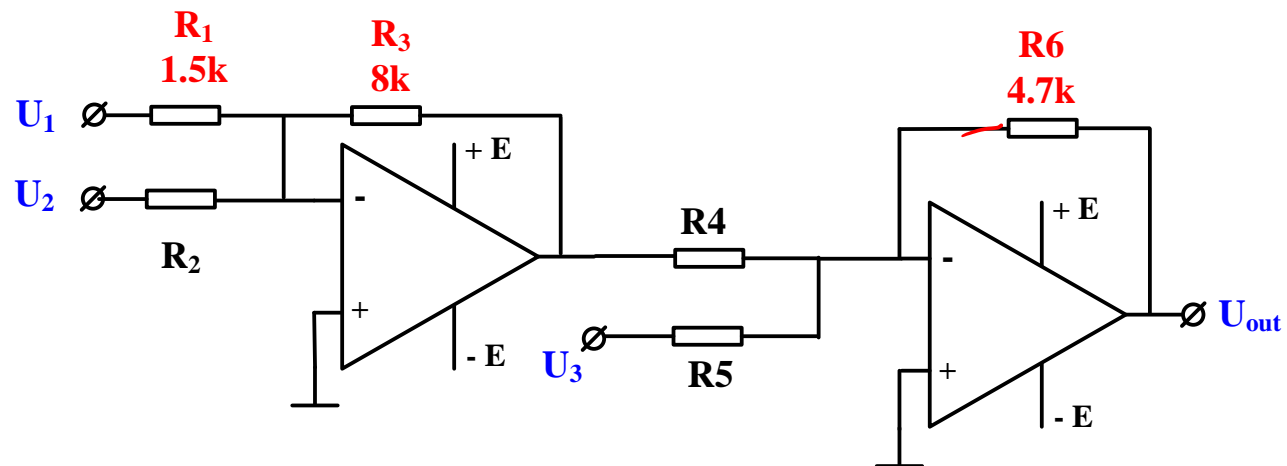

Chapter 2. Semiconductor Devices (Cont.)

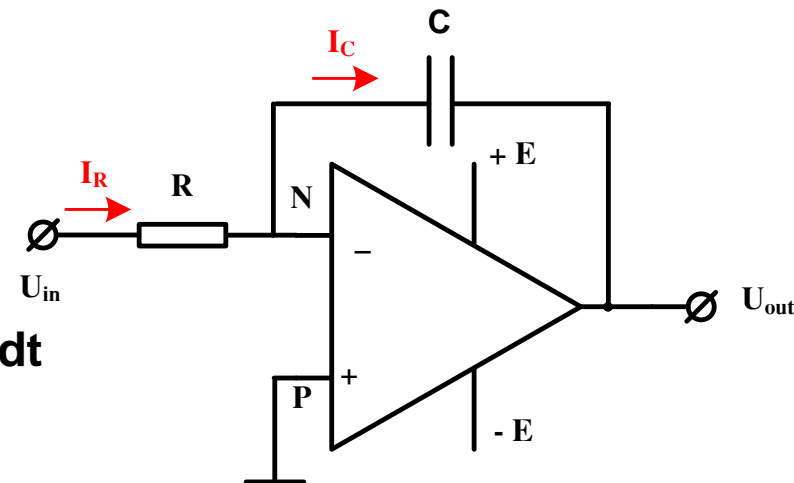f) Integrator:


- **Negative feed back**
- **Capacitor C:** feedback resistor replaced by C, which operates in charged and discharged period
- **Node N:** $I_R - I_C = 0$, where $I_R = (U_{in} - U_N)/R$ and $I_C = Cd(U_C/dt) = C(U_N - U_{out})/dt$
- **Since:** $U_N = U_P = 0 \rightarrow U_{out} = -1/(RC) \int U_{in} dt + U_0 \sim$ **Rate of input change**



where U_0 : initial potential on C before integration $\rightarrow U_0 = 0$?

Here: $T = RC$ – integral constant related to rate of change (RoC) at output according to the change of input


- **Example:** $R = 10 \text{ k}\Omega$, $C = 0.01 \text{ }\mu\text{F} \rightarrow T = RC = 0.1 \text{ ms}$
- ✓ RoC for negative ramp: $\Delta U_{out}/\Delta t = -U_{in}/(RC) = -5\text{V}/0.1 \text{ ms} = -50 \text{ mV}/\mu\text{s}$
- ✓ RoC for positive ramp: $\Delta U_{out}/\Delta t = +50 \text{ mV}/\mu\text{s}$, where $\Delta t = 100 \mu\text{s}$
- ✓ **Therefore:** $\Delta U_{out} = 5\text{V} \rightarrow$ When $U_{in} = +2.5\text{V}$, $U_{out} = 0 \rightarrow -5\text{V}$;
When $U_{in} = -2.5\text{V}$, $U_{out} = -5\text{V} \rightarrow 0\text{V}$
- ✓ **QUESTION:** If U_{out} changes $0 \rightarrow -5\text{V}$ with the same input in $50 \mu\text{s} \rightarrow$ **What modification in the circuit?**

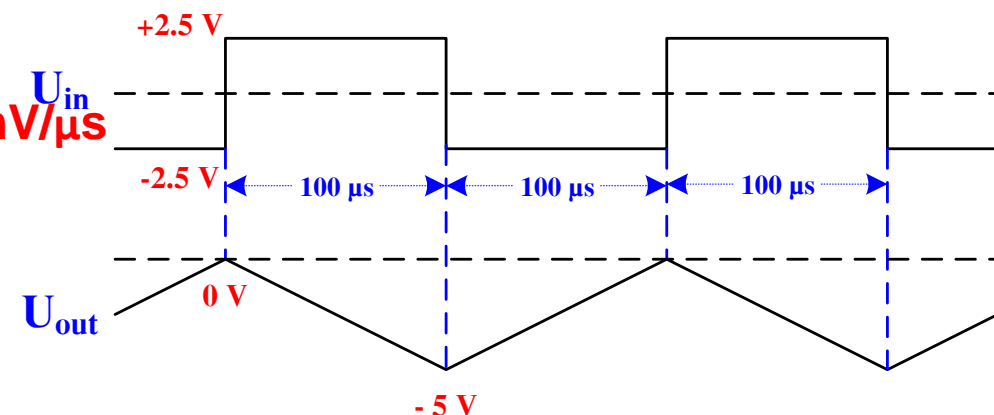

Chapter 2. Semiconductor Devices (Cont.)

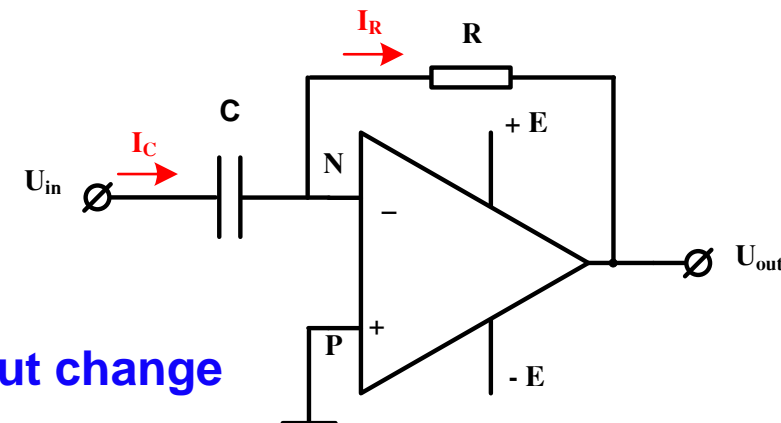
g) Differentiator:

- Negative feed back;
- Capacitor C: Input resistor is replaced by C interval
- Node N: $I_C - I_R = 0$, where $I_C = C d(U_{in} - U_N)/dt$ and $I_R = (U_N - U_{out})/R$
- Since $U_N = U_P = 0 \rightarrow C dU_{in}/dt = - U_{out}/R \rightarrow U_{out} = - (RC) dU_{in}/dt \sim \text{Rate of input change}$



Here: $T = RC$ – differential constant related to the achieved value of output according to RoC of input

- Example: $C = 0.001 \mu F$, $R = 2.2 k\Omega \rightarrow T = RC = 2.2 \mu s$
- ✓ RoC U_C/t : U_C changes from $-5 V$ to $+5 V$ in $5 \mu s$ and vice versa
 $\rightarrow U_C/t = 10V/5\mu s = 2V/\mu s$
- ✓ Therefore: $U_{out} = - (U_C/t) RC$
 - ✓ Positive ramp: $U_{out} = - 2V/\mu s \times 2.2 \mu s = - 4.4 V$
 - ✓ Negative ramp: $U_{out} = -(- 2V/\mu s) \times 2.2 \mu s = + 4.4 V$
- ✓ QUESTION: If $R = 3.3k\Omega \rightarrow$ What is the output changed?


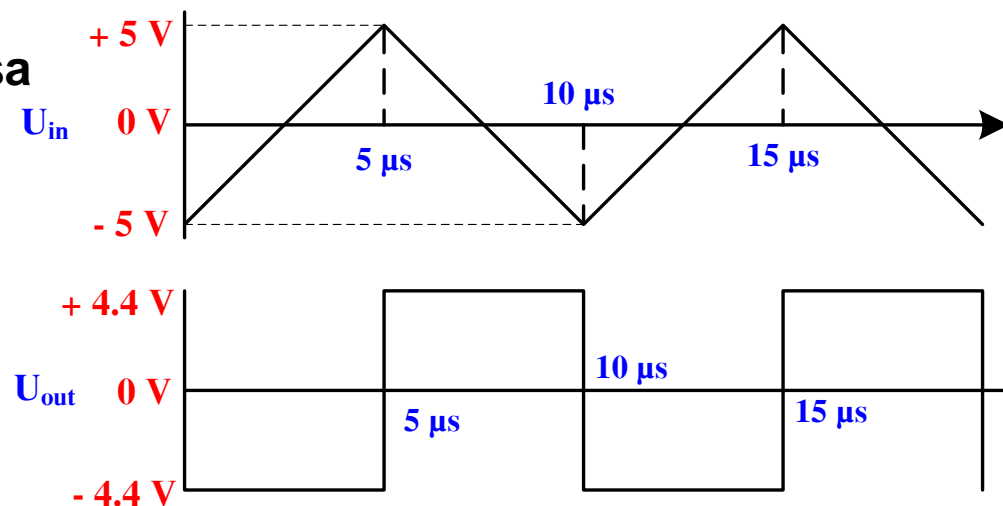


Chapter 2. Semiconductor Devices (Cont.)

2.3.4. Signal oscillators

a) Principle:

- **Positive feedback:** In-phase output is fed back to input with no phase shift
- **Close loop:** created by forward amplifier and feedback circuit
- **Desired output:** sinusoidal signal
- **Condition for oscillation:** 1) Phase shift around feedback = 0; 2) $K_u \cdot B = 1$
- **Start-up condition:** When DC supply is on, voltage gain should be > 1 at first to produce a desired output amplitude and oscillation is maintained

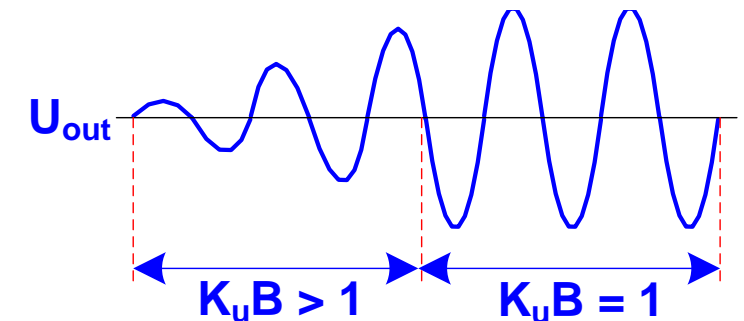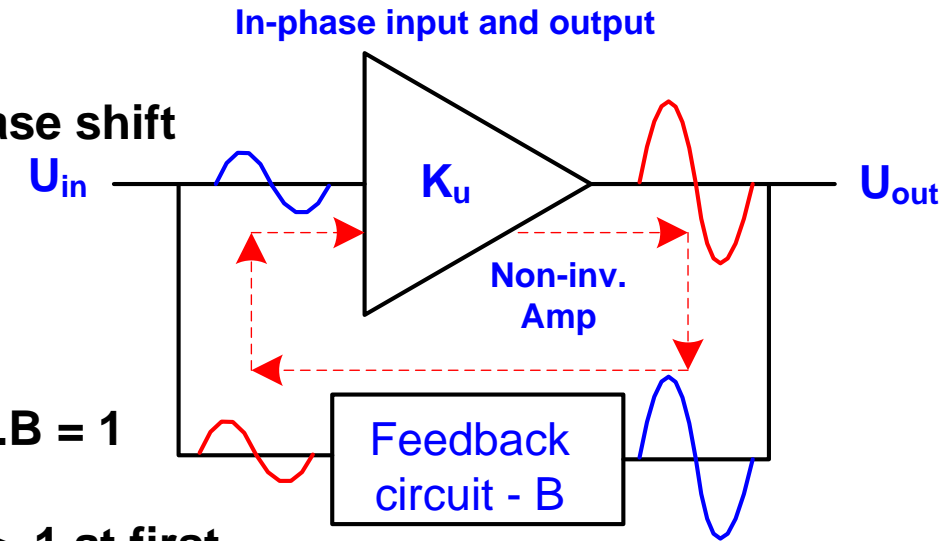


Chapter 2. Semiconductor Devices (Cont.)

b) Oscillator with RC feedback circuits

b1. Wien – Robinson bridge oscillator



- Lead-leg circuit: $Z_{(R1-C1)} = R_1 - jX_1$; $Z_{(R2-C2)} = R_2(-jX_2)/(R_2 - jX_2)$
- ✓ if $R_1 = R_2 = R$, $C_1 = C_2 = C \Rightarrow U_2 = U_1[X_{R1-C1}/(Z_{R1-C1} + Z_{R2-C2})]$
 $\Rightarrow U_2/U_1 = RX/[3RX + j(R - X)^2]$
- ✓ At resonance frequency f_c : $U_2/U_1 = 1/3$ or $U_2 = 1/3U_1$ since $R = X$ at f_c
- Wien – bridge oscillator: Utilization of lead-lag circuit $\Rightarrow U_{out} = U_1$, $U_p = U_2$
- ✓ Non-inverting amplifier gain: $K_u = 1 + R_f/R_0$, \Rightarrow input – output are in-phase
- ✓ Lead-leg feed back gain: $B = U_{out}/U_p = 1/3$
- ✓ Since $K_u B = 1 \Rightarrow K_u = 3 \Rightarrow R_f/R_0 = 2 \Rightarrow R_f = 2R_0$
- ✓ Start-up condition: $K_u > 3 \Rightarrow R_0$ replaced by a potentiometer, or back-to-back Zener diode
- Output signal frequency: resonance $f_c = 1/(2\pi RC)$

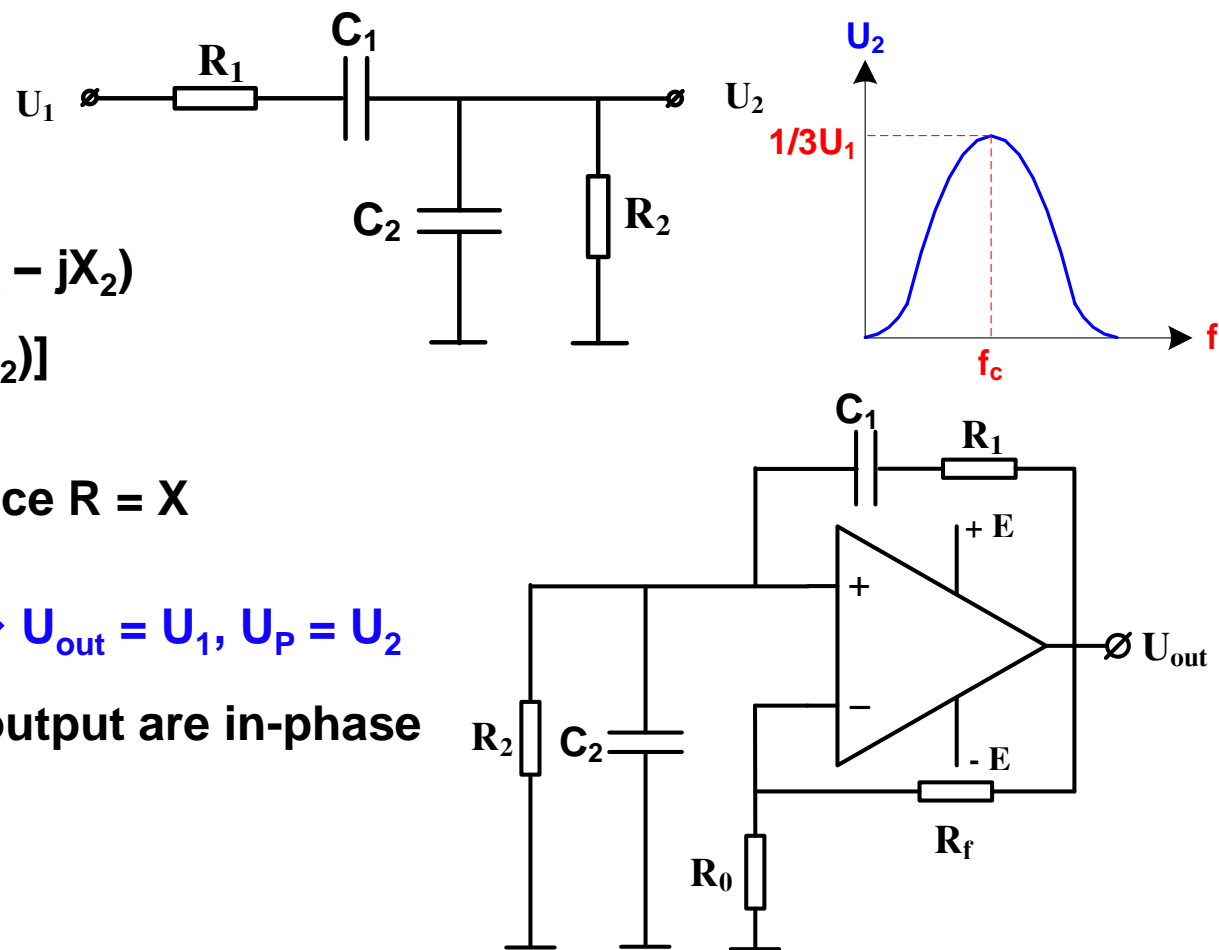

Chapter 2. Semiconductor Devices (Cont.)

b2. Phase-shift oscillator:


- **RC ladder:** Each RC shifts phase with max 90° . Oscillation occurs at frequency with total phase shift of 180° .
- If $R_1 = R_2 = R_3 = R$ and $C_1 = C_2 = C_3 = C$: $U_2/U_1 = 1/29$
- **RC phase shift oscillator:** based on inverting amplifier \rightarrow Input and output out-of-phase \rightarrow After RC ladder, total phase shift is 360° or 0°
- **Feedback RC ladder:** $B = U_2/U_1 = U_{out}/U_N = 1/29$
- ✓ Since $K_u B = 1$: $K_u = 1/29 \rightarrow R_f/R_0 = 29 \rightarrow R_f = 29R_0$
- **Output signal frequency:** resonance $f_c = 1/(2\pi\sqrt{6}RC)$

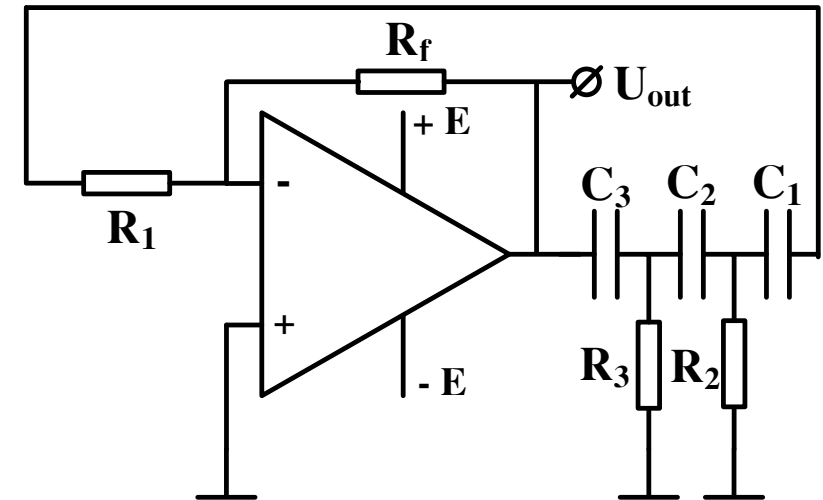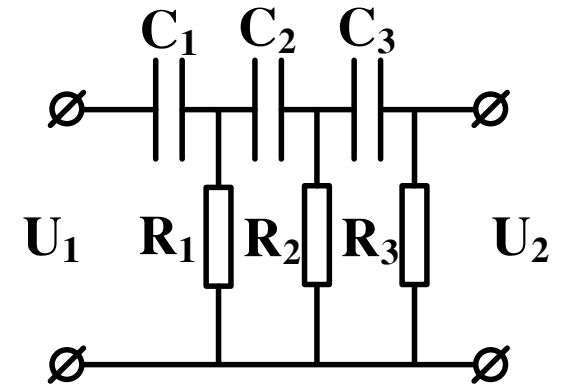

Chapter 2. Semiconductor Devices (Cont.)

b3. Colpitts oscillator


- **Feedback by C_1 , C_2 , L :** Used for necessary phase shift and plays role of resonant filter to pass signal of desired frequency at oscillation
- **Output signal frequency: resonance $f_r = 1/(2\pi\sqrt{LC_{equivalent}})$**
where $C_{equivalent} = C_1C_2/(C_1 + C_2)$
- $B = U_f/U_{out} = IX_{C1}/IX_{C2} = 1/(2\pi f_r C_1)/1/(2\pi f_r C_2) \Rightarrow B = C_2/C_1$
- Since $K_u B = 1 \Rightarrow K_u = C_1/C_2$
- Start-up condition: Initially $K_u B > 1$

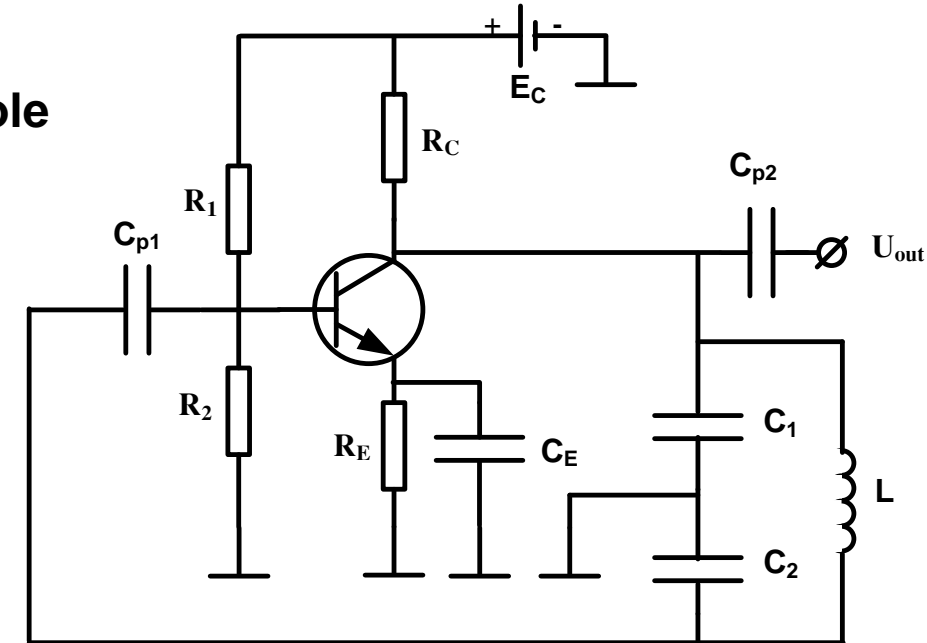

Chapter 2. Semiconductor Devices (Cont.)

b4. Maisne oscillator

- **Feedback by C_1 , C_2 , L :** Used for necessary phase shift and plays role of resonant filter to pass signal of desired frequency at oscillation
- **Output signal frequency: resonance $f_c = 1/(2\pi\sqrt{LC})$**
- Less commonly used, because of high cost of transformer and size

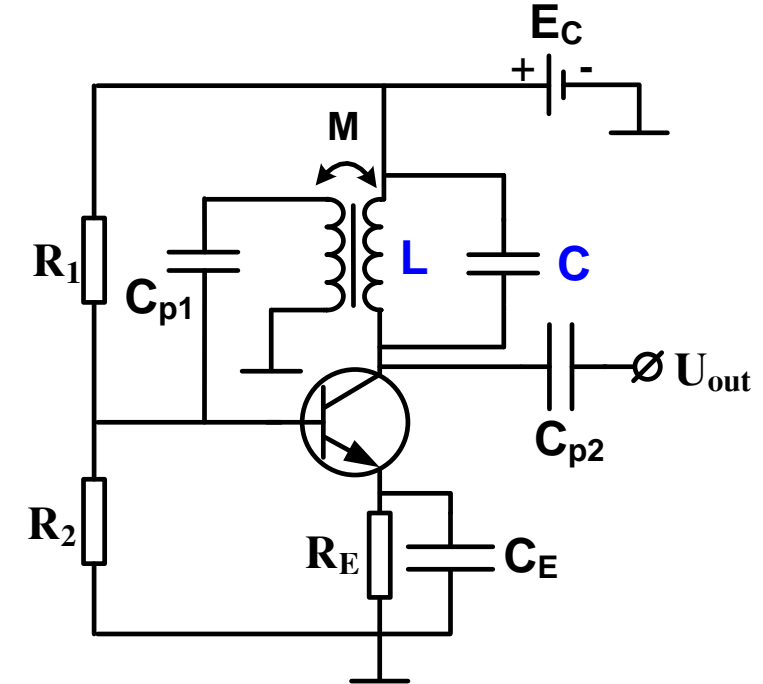

Chapter 2. Semiconductor Devices (Cont.)

2.1. PN Junction - Diode and application


2.2. Bipolar Junction Transistor (BJT) and applications

2.3. Operational amplifier (OPAM) and applications

2.4. Voltage regulation

Chapter 2. Semiconductor Devices (Cont.)

2.4.1. Basic concepts


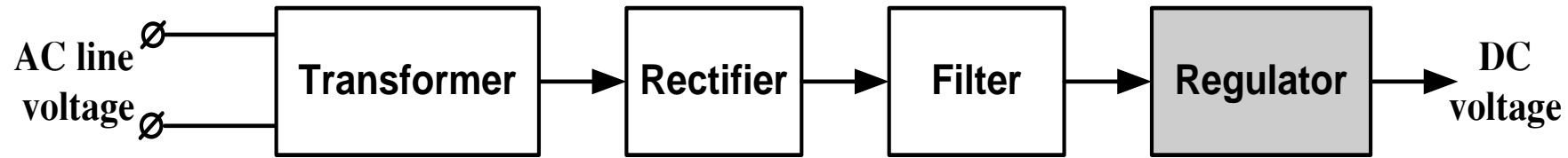


- **Definition:** Line regulation, Load regulation
- ✓ Line regulation: $(\Delta U_{\text{out}} - \Delta U_{\text{in}}) / \Delta U_{\text{in}} (100\%)$
- ✓ Load regulation: $(\Delta U_{\text{NL}} - \Delta U_{\text{FL}}) / \Delta U_{\text{FL}} (100\%)$, where NL = No load, FL = Full load
- **Classification:**
 - **Use of a control element:** Zener diode, series regulators, parallel regulators (shunt), switching regulators
 - **Linear output** (Zener diode, series regulators, parallel regulators (shunt)), **non-linear output** (switching regulators)
 - **Integrated circuit (IC)** regulators

Chapter 2. Semiconductor Devices (Cont.)

a) Zener diode

- **Key feature:** 1) designed to operate in breakdown region 3;
2) Ability to keep reserve voltage across its terminal constant;
- **If Zener diode forward biased:** Operate as a normal diode.
- **Zener breakdown characteristic:**
 - Breakdown effect begins at I_{ZK} , where I_Z start increasing rapidly, internal impedance begin decreasing
 - Down to bottom of knees, breakdown U_Z is almost a constant as I_Z increasing
- **Zener diode operating at breakdown acts as a voltage regulator:** because it maintains a nearly constant voltage over a specific range of reverse current
 - I_Z should be maintained at I_{ZK} (min value) to keep breakdown, o.w U_Z decreases
 - I_Z should be less than I_{ZM} (max value) to avoid damage
 - Therefore I_{ZK} : nominal value of I_Z typically specified on a dataset of Zener diode
 - Zener impedance: $Z_Z = \Delta U_Z / \Delta I_Z$

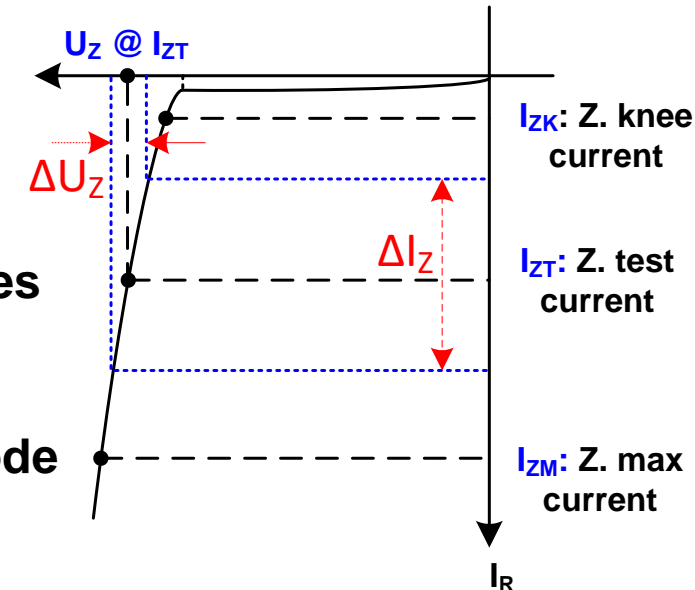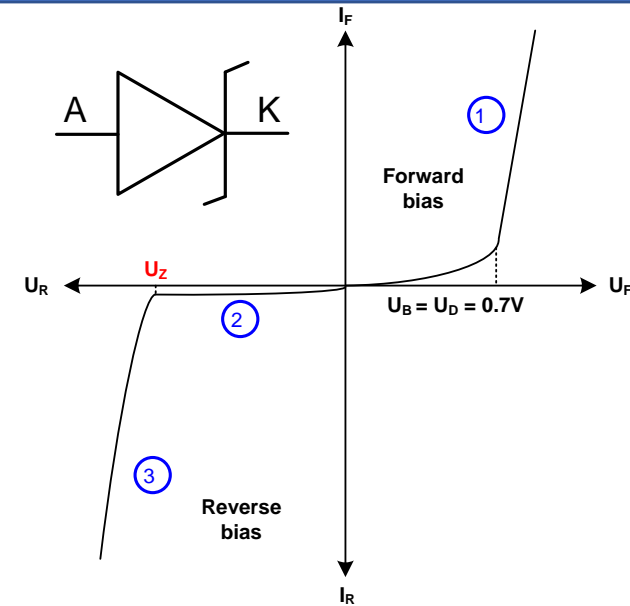

Chapter 2. Semiconductor Devices (Cont.)

Example: For a given Zener diode **IN4736**: $Z_T = 3.5\Omega$, $U_{ZT} = 6.8V$ at $I_{ZT} = 37mA$ and $I_{ZK} = 1mA$.

What is U_Z when $I_Z = 50mA$? When $I_Z = 25mA$?

- $I_Z = 50mA$: $\Delta I_Z = 50 - 37 = 13mA \rightarrow \Delta U_Z = \Delta I_Z R_Z = 13mA \times 3.5\Omega = +45.5mV \rightarrow U_Z = U_{ZT} + \Delta U_Z \sim 6.85V$
- $I_Z = 25mA$: $\Delta I_Z = 25 - 37 = -12mA \rightarrow \Delta U_Z = \Delta I_Z R_Z = -12mA \times 3.5\Omega = -42mV \rightarrow U_Z = U_{ZT} + \Delta U_Z \sim 6.76V$

Example: For a voltage regulator using Zener diode: $U_Z = 12.7V$, $R_1 = 390\Omega$, $R_E = 12k\Omega$, $R_L = 240\Omega$, $\beta = 50$, $U_{BW} = 0.7V$. Rectified output a) $U_{in} = 21V$ when $I_L = 0$ (no load) and b) $U_{in} = 20V$ when $I_L = 50mA$ (with load).


What is currents at E, B, C and I_Z without and with load?

• **Without load:**

- $U_{out} = U_{RE} = U_Z - U_{BE} = 12.7V - 0.7V = 12V \rightarrow I_E = U_{RE}/R_E = 12V/12k\Omega = 1mA \rightarrow I_B = I_E/(1 + \beta) \sim 20\mu A$; $I_C = \beta I_B \sim I_E$
- $U_{R1} = U_{in} - U_Z = 21V - 12.7V = 8.3V \rightarrow I_1 = U_{R1}/R_1 = 8.3V/390\Omega \sim 21.3mA$
 $\rightarrow I_Z = I_1 - I_B = 21.3mA - 20\mu A \sim 21.3mA$

• **With load:** $I_E = U_{out}/(R_E // R_L) \sim 20V/235\Omega = 51.1mA$

➤ In similar manner: $I_B = 1mA$; $I_C \sim I_E = 51.1mA$; $I_1 = 18.7mA$, $I_Z = 17.7mA$

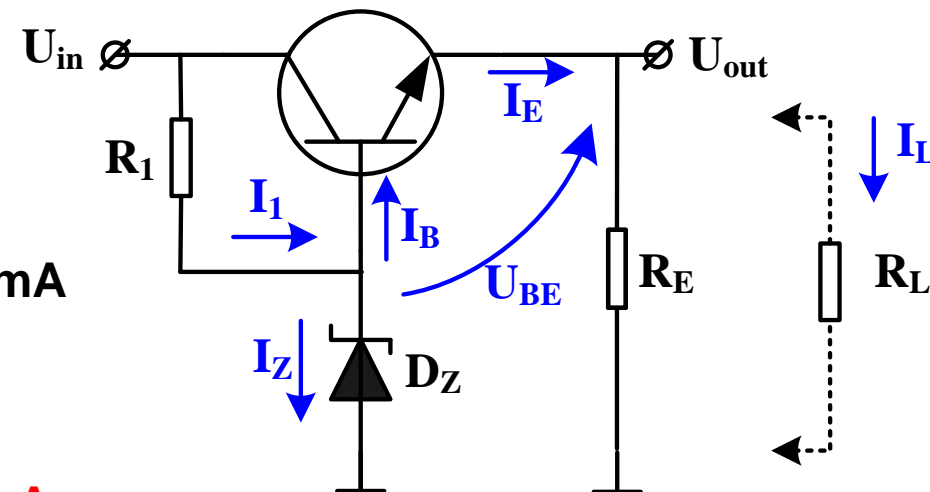

Chapter 2. Semiconductor Devices (Cont.)

b) Series regulator: based on OPAM


- **Comparator:** Inverse and non-inverse; operating in saturation mode, $U_{out} = \pm U_{max}$

➤ **Inverse:** (-) input compared with U_{ref} in (+) input

✓ If $U_0 = U_{ref} - U_{in} > 0 \rightarrow U_{in} < U_{ref} \rightarrow U_{out}$ from $+U_{max} \rightarrow -U_{max}$

✓ If $U_0 = U_{ref} - U_{in} < 0 \rightarrow U_{in} > U_{ref} \rightarrow U_{out}$ from $-U_{max} \rightarrow +U_{max}$

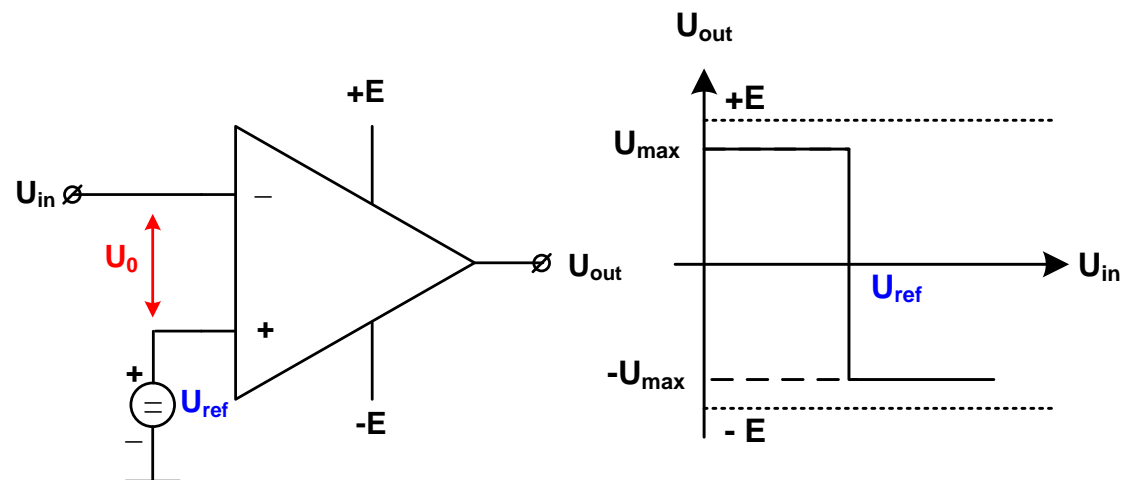✓ Transfer characteristic: based on inverse amplifier




➤ **Non-Inverse:** Non-Inverse (+) input compared with U_{ref} in (-) input

✓ If $U_0 = U_{in} - U_{ref} > 0 \rightarrow U_{in} > U_{ref} \rightarrow U_{out}$ from $-U_{max} \rightarrow +U_{max}$

✓ If $U_0 = U_{in} - U_{ref} < 0 \rightarrow U_{in} < U_{ref} \rightarrow U_{out}$ from $+U_{max} \rightarrow -U_{max}$

✓ Transfer characteristic: based on non-inverse amplifier

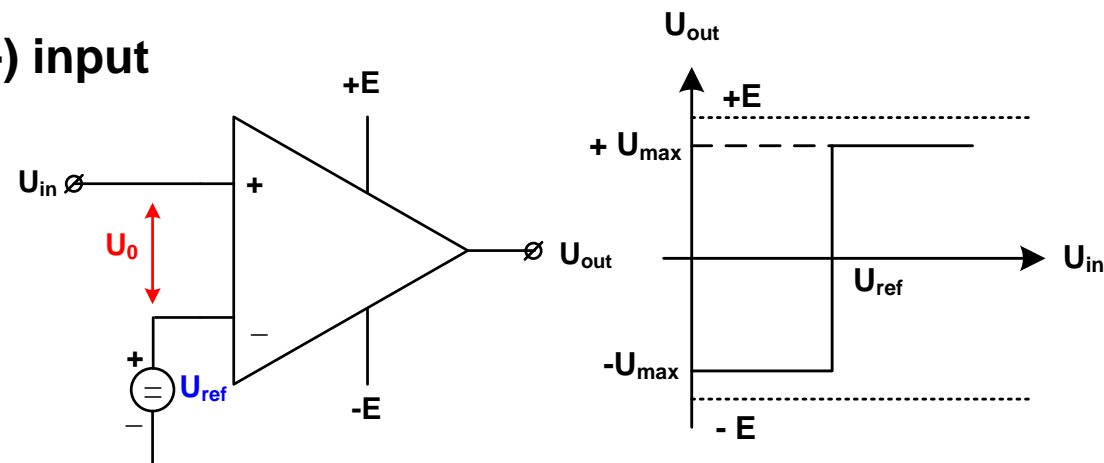


Chapter 2. Semiconductor Devices (Cont.)

- **Schematic circuit:** Based on **non-inverse comparator**
- Transistor as a **control element** switch connected in series with LOAD
- **Principle:** Compared $U_{ref} = U_Z$ and $U_{R3} = U_{out} R_3 / (R_2 + R_3)$ fed back to N-input $\rightarrow U_{out} = U_{ref} (1 + R_2 / R_3)$ (neglect U_{BE})
- If $U_0 = U_{ref} - U_{R3}$ zero-crossed, OPAM output U_B opens transistor $\rightarrow U_{out}$ is adjusted accordingly to be const


Example:

- $U_{ref} = U_Z = 5V \rightarrow U_{out} = U_Z (1 + R_2 / R_3) = 5V (1 + 10k / 10k) = 10V$


Quick test 13:

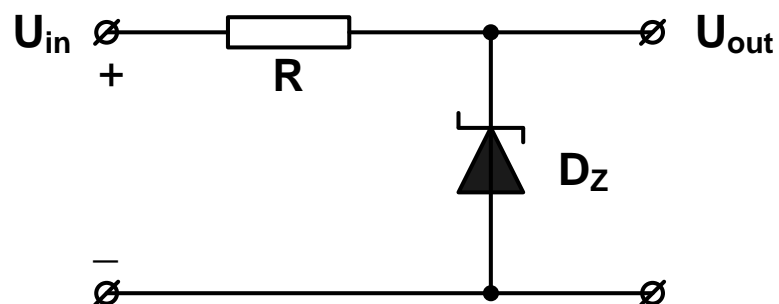

- $U_{out} = U_Z$

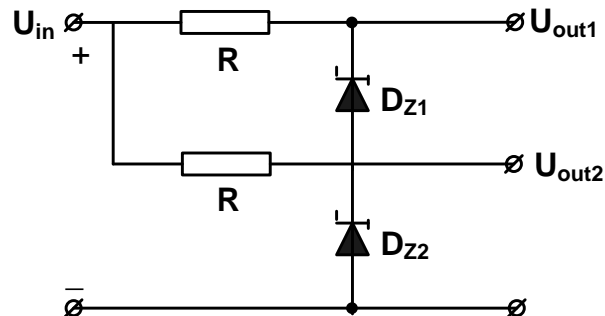

- $U_{out2} = U_{Z2}; U_{out1} = U_{Z1} + U_{Z1}$

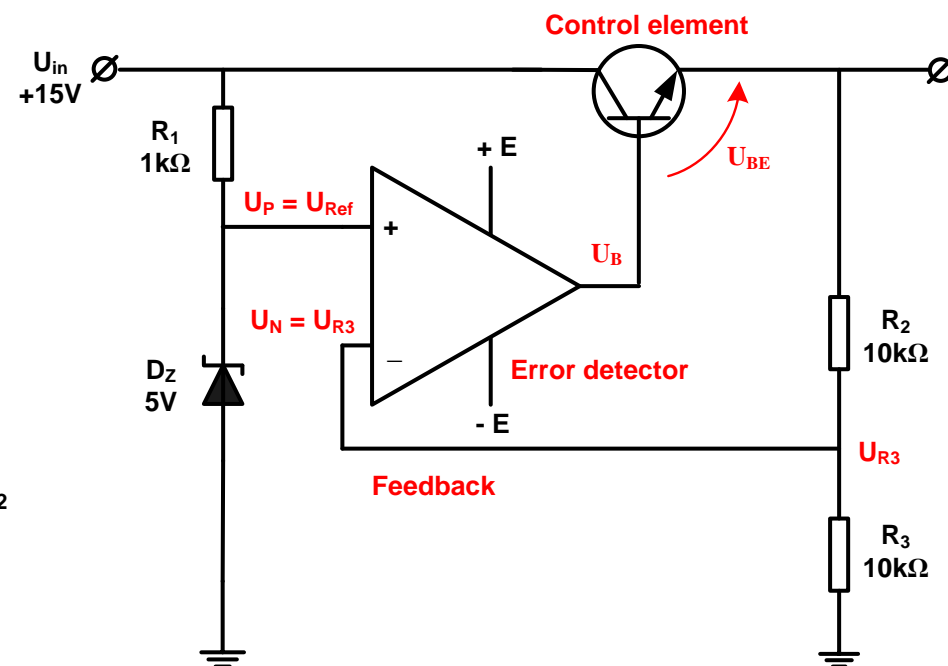

Chapter 2. Semiconductor Devices (Cont.)

c) Parallel regulator: based on OPAM (common name: **SHUNT regulator**)

- Transistor as a **control element** connected in parallel to the LOAD, and R_1 is series with LOAD

- **Principle:** Inverse comparator


- r_{CE} and R_1 are voltage divider used to maintain U_{out} constant

- If U_{out} decreases/increases, sensed by R_3 - $R_4 \rightarrow U_0 = U_{ref} - U_{R4}$ zero-crossed and U_B decreased/increased $\rightarrow I_B$ and then I_C decreased/increased $\rightarrow r_{CE}$ increased/decreased \rightarrow Maintain U_{out} as a constant, with a voltage divider of R_1 and r_{CE}

Example: If max input $U_{in} = 12.5$, what power rating for R_1 ?

- $U_{out} = 0 \rightarrow U_Z(1+R_3/R_4) = 0 \rightarrow 10V$, and in worse case R_1 is dissipated when short output or $U_{out} = 0 \rightarrow U_{R1} = U_{in} - U_{out} = 12.5V$

- Power rating: $P = UI = U_{R1}^2/R_1 = (12.5V)^2/22\Omega = 7.1 W \rightarrow$ Select R_1 with power rating about $> 10W$ for use

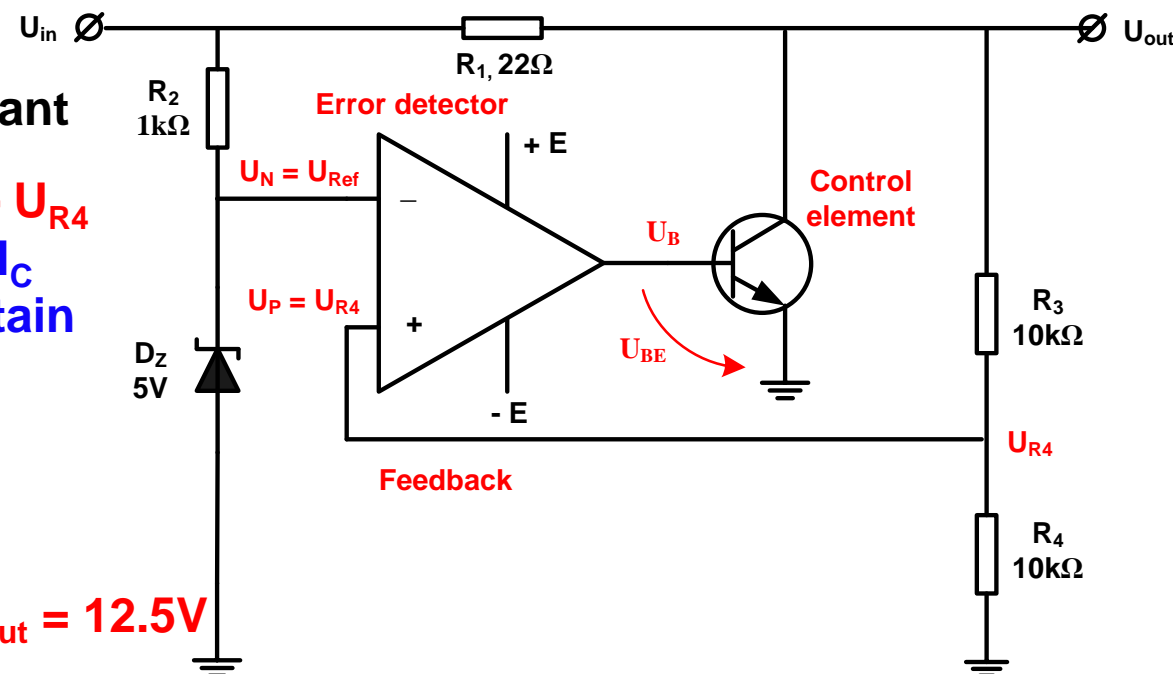

Chapter 2. Semiconductor Devices (Cont.)



d) Switching regulator: **based on OPAM**

- **Principle:**
 - **More efficiency than linear types, because Transistor not always conducted**
 - **More load current at low voltage than linear regulators, since the control transistor doesn't dissipate**
- **Type:** step-down, step-up, inverter

Chapter 2. Semiconductor Devices (Cont.)

1. Step-down regulator

- ✓ Charge and discharge of C
- ✓ $U_{out} = (t_{on}/T)U_{in}$, where $T = t_{on} + t_{off}$
- ✓ t_{on}/T : duty cycle
- ✓ If $U_{out} \downarrow \rightarrow t_{on} \uparrow \rightarrow$ **C is charged more** additionally to compensate the decrease $\rightarrow U_{out} \downarrow$
- ✓ If $U_{out} \uparrow \rightarrow t_{on} \downarrow \rightarrow$ **C is discharged** enough inversely to the increase $\rightarrow U_{out} \uparrow$

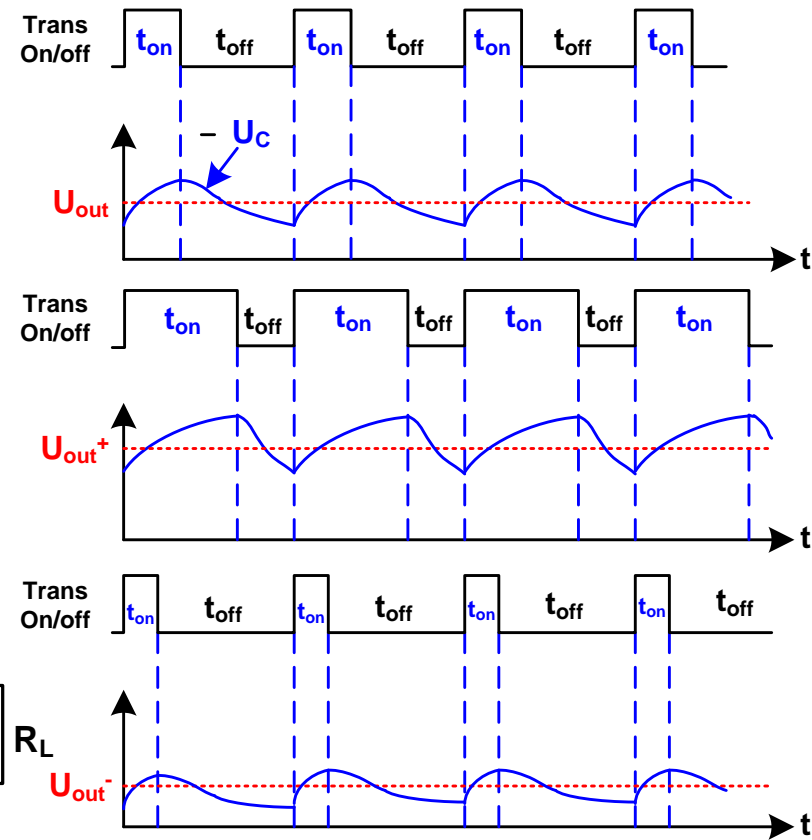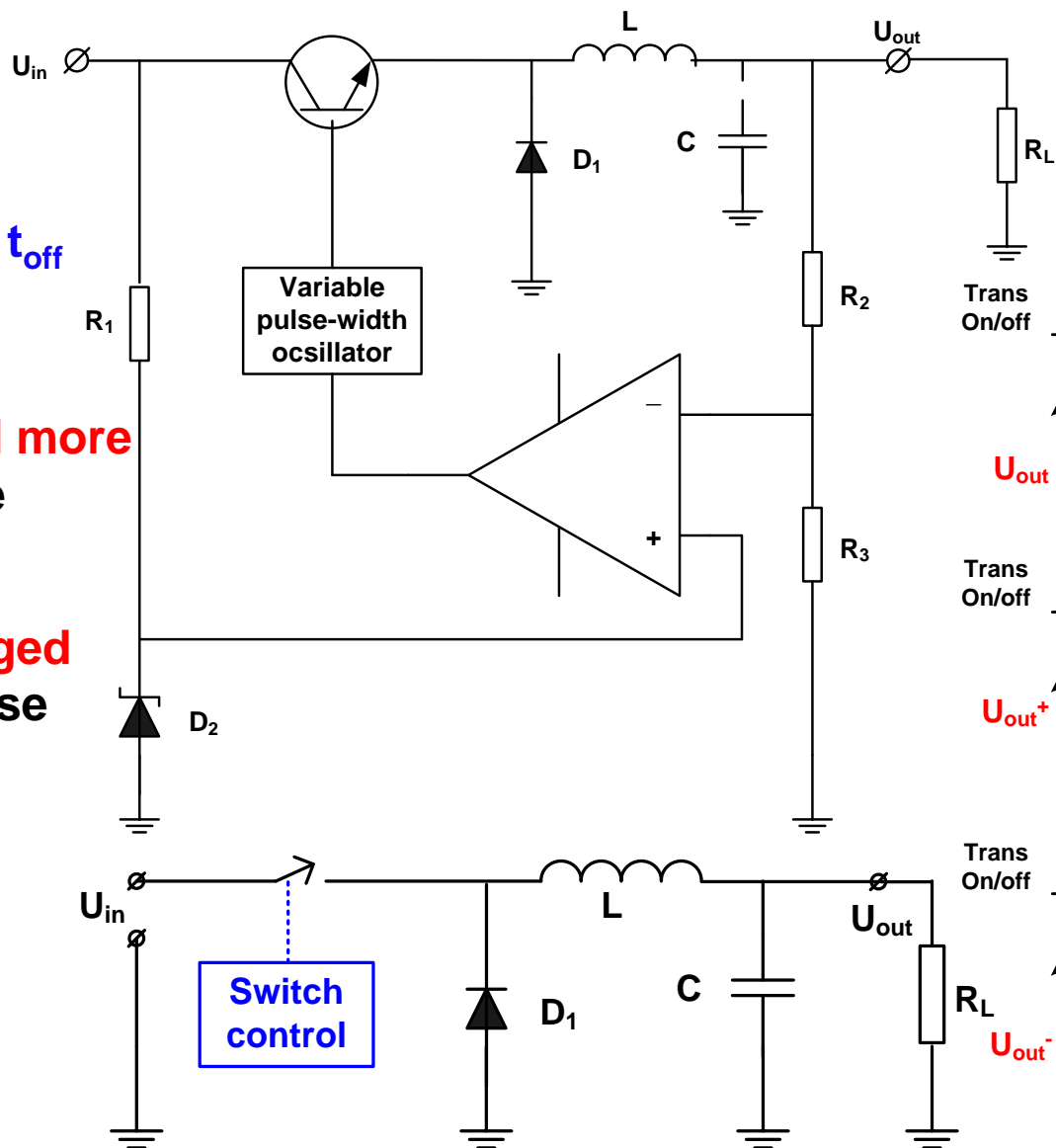


Chapter 2. Semiconductor Devices (Cont.)

2. Step-up regulator

- ✓ When Transistor is **on**, U_L jumps to U_{in} ($+ \rightarrow -$). During t_{on} , the induced voltage U_L starts decreasing, D_1 is reverse biased, C discharged small amount to the load (**C is not charged**)
- ✓ When Transistor is **off**, U_L changes polarity ($- \rightarrow +$), D_1 is forward biased, and **C is charged to U_{in}** . During t_{off} : $U_{out} = U_{in} + U_L$
- ✓ If $U_{out} \uparrow \rightarrow t_{on} \downarrow \rightarrow$ decrease in the amount that C will charge
- ✓ If $U_{out} \downarrow \rightarrow t_{on} \uparrow \rightarrow$ increase in the amount that C will discharge
- ✓ As the result: U_{out} maintains constant value


3. Voltage-inverter regulator: self-reading

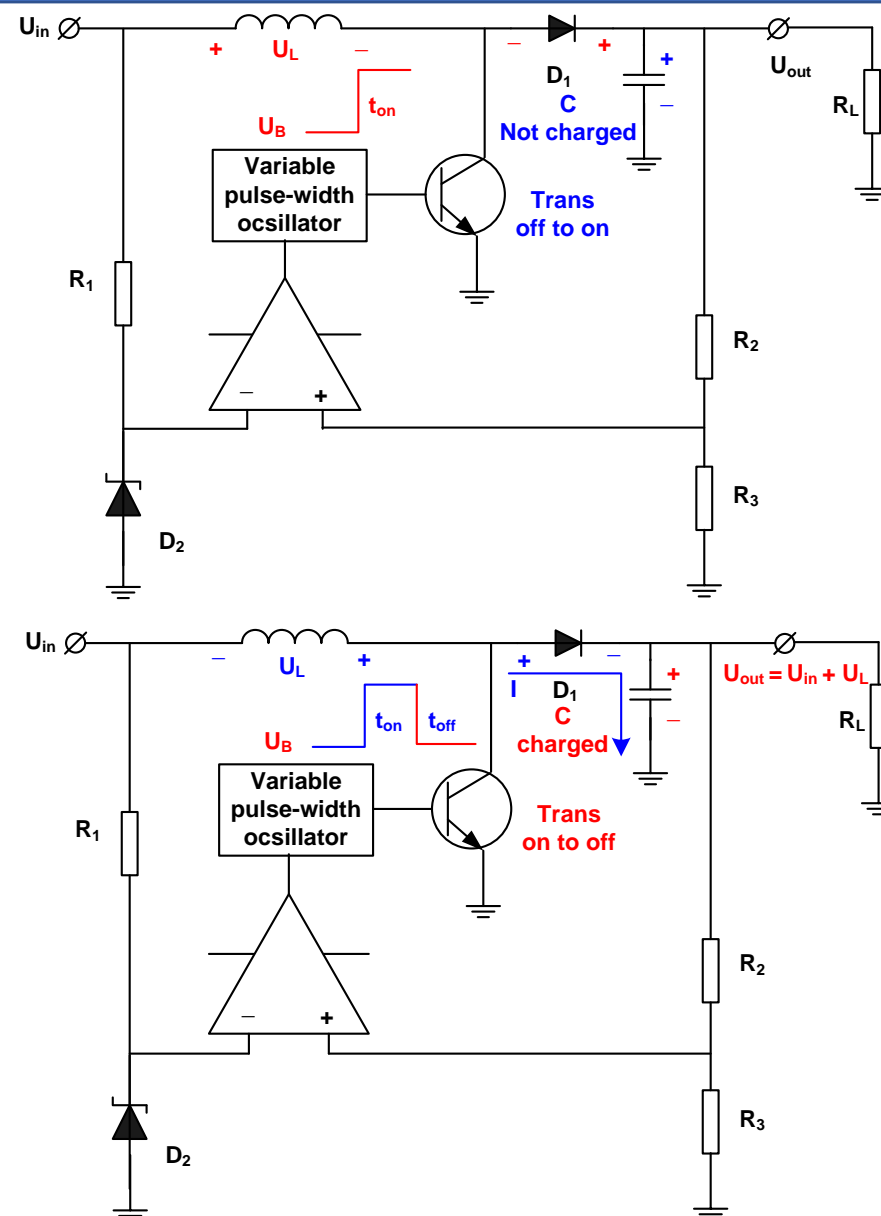

Chapter 2. Semiconductor Devices (Cont.)

e) Integrated circuit (IC) regulators

- **78XX**: XX = positive regulated voltage (+05, +06, +08, +09, +12, +15, +18, +24 V)
- **79XX**: XX = negative regulated voltage (-05, -06, -08, -09, -12, -15, -18, -24 V)
- **LM317**: precise $U_{out} = 1.25 \text{ V}$. R1-R2 voltage divider used for various U_{out}
→ $U_{out} = 1.25 \text{ V}(1 + R_2/R_1)$
- **μA78G**: provide positive voltage output from +5 to +30 V
- **μA79G**: provide negative voltage output from -2.5 to -30 V
- **QUESTION**: Investigate applications of IC regulators (increase power dissipation, current limiting,)
- **Current regulators**: self-reading

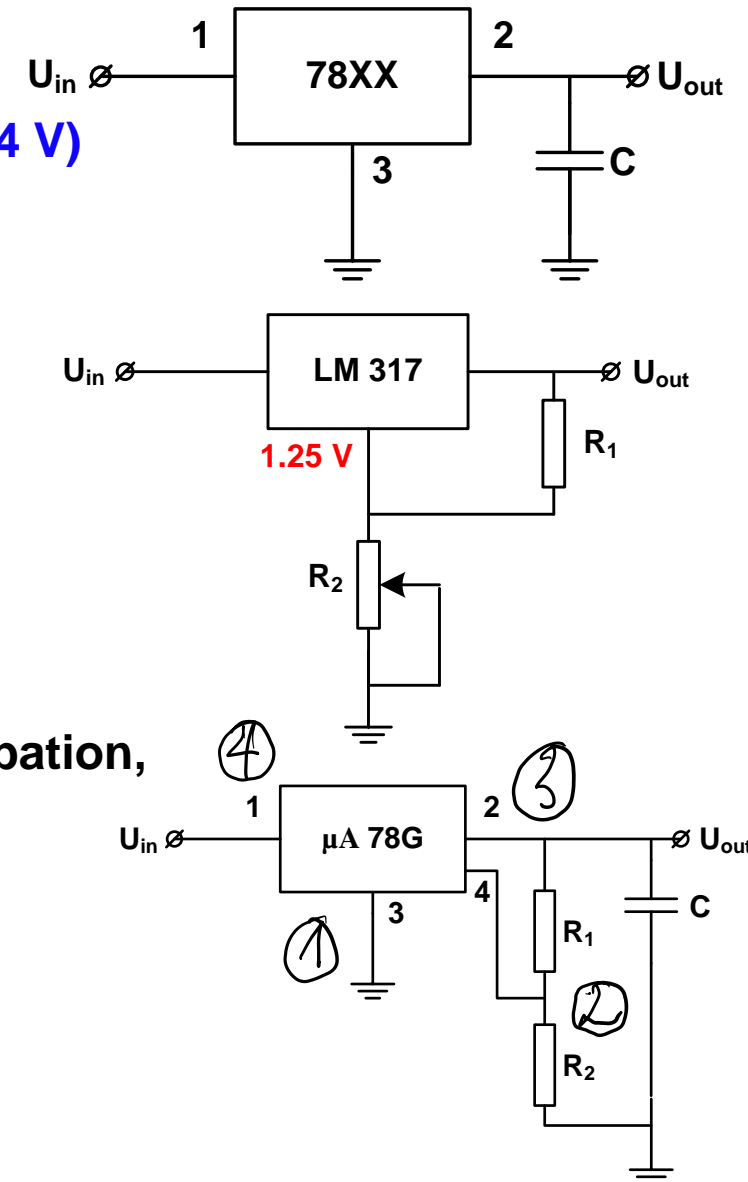

Chapter 2. Semiconductor Devices (Cont.)

CHAPTER 2: SUMMARY

1. DIODE and applications

a. Forward bias, reverse bias, break down

b. Applications:

- Rectifiers: Half-wave, Full-wave, bridges, doubler
- Limiters: serial (upper, lower), parallel (upper, lower)

2. Transistors and applications

a. Basic equations, amplification mode, saturation mode, cut-off mode, basic amplifier schemes (EC, CC)

b. DC analysis: Q-point, DC load line, DC load

c. DC bias methods: based current, feedback current, emitter currents, DC equivalent (Thevenin's)

d. AC analysis: EC and CC

- AC equivalent model of transistor and amplifier
- Derivation of K_u , K_i , $K_p = K_u K_i$, take note of operation frequency range

d. Multistage amplifier: independent DC mode for a stage, $K_u = K_1 \dots K_N$, C-coupled and direct coupled

3. OPAM and applications

- a. Linear and saturation mode of OPAM**
- b. Basic features: Transfer characteristic according to inverse and non-inverse inputs, $U_P = U_N$, $I_P = I_N = 0$**
- c. Applications: inverse and non-inverse amplifiers, summing and subtracting amplifiers, integrator and differentiators, function generators**

4. Oscillators

- e. Signal oscillators**
 - Oscillation conditions**
 - Based on RC feedback**
 - Based on use of OPAM and Transistors**
 - Signal frequency: resonance frequency**

Chapter 2. Semiconductor Devices (Cont.)


5. Voltage regulators

- **Zener diode: based on Zener effect**
- **Series: Control element in series with LOAD, based on non-inverse mechanism**
- **Parallel: Control element in parallel to LOAD, based on inverse mechanism**
- **Switching: non-linear compensation of output voltage, based on charge/discharge of C**
- **Integrated circuits (IC): 78XX, 79XX, LM317, uA78G, uA79G**

Quick test Chapter 2


Prob 1. Given a circuit assuming that: $R = 0\Omega$ and $U_D = 0,7V$.

- State the function of the circuit and illustrate the output signal $U_{out}(t)$ and input signal $U_{in}(t)$ on the same coordinate system.
- If the order of branches D_1 -E and D_2 -E are exchanged, is there any significant change in its function, and explain the reason?

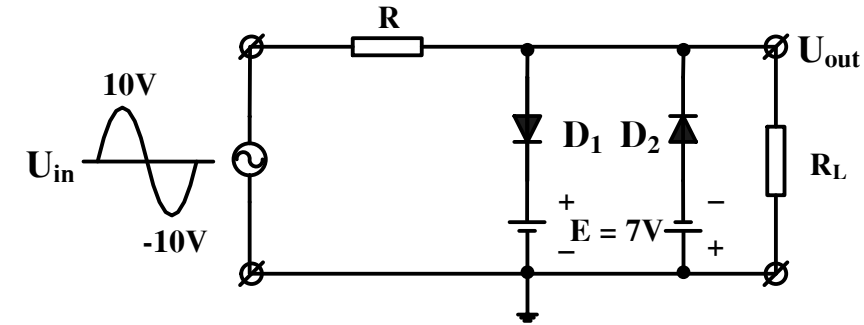

Prob 2. Given a circuit, with saturated voltages of OPAM $\pm U_{max} = \pm 10V$.

- State the function of the circuit and derive the equation for U_{out} according to its parameters, assuming $R_1 = R_2$.
- When $R_1 = R_2 = 10K\Omega$, $U_1 = U_2 = 1V$. Determine the max value of R_4/R_3 so that the circuit keeps operating in a linear amplification.

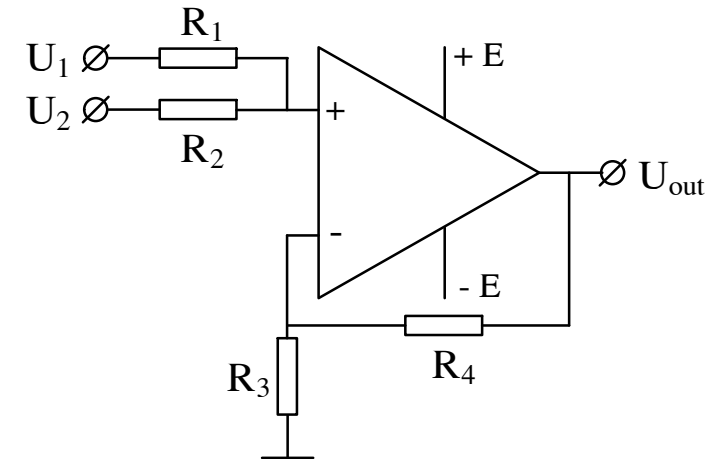

Prob 3. Given a regulator circuit using Zener diode.

- With $U_{in} = 12V$, $U_{out} = 9V$, test Zener current $I_{ZT} = 25\text{ mA}$. Determine compensate resistor R .
- With $U_{in} = 20V$, $U_{out} = U_Z = 6V$, max Zener current $I_{ZM} = 30mA$, knees current $I_{ZK} = 0V$, $R=400\Omega$. Determine R_t to work in regulation band.
- If $U_{inNL} = 12V$ without LOAD, and $U_{inL} = 10V$ with LOAD. Determine the voltage stability coefficient in %

