



25 YEARS ANNIVERSARY  
SOICT

ĐẠI HỌC BÁCH KHOA HÀ NỘI  
VIỆN CÔNG NGHỆ THÔNG TIN VÀ TRUYỀN THÔNG



ĐẠI HỌC BÁCH KHOA HÀ NỘI  
VIỆN CÔNG NGHỆ THÔNG TIN VÀ TRUYỀN THÔNG

# Electronics for Information Technology

(Điện tử cho Công nghệ Thông tin)

IT3420E

**Đỗ Công Thuần**

Department of Computer Engineering

Email: [thuandc@soict.hust.edu.vn](mailto:thuandc@soict.hust.edu.vn)

# General Information

- Course: **Electronics for Information Technology**
- ID Number: IT3420
- Credits: 2 (2-1-0-4)
- Lecture/Exercise: 32/16 hours (48 hours, 16 weeks)
- Evaluation:
  - Midterm examination and weekly assignment: **50%**
  - Final examination: **50%**
- Learning Materials:
  - Lecture slides
  - Textbooks
    - *Introductory Circuit Analysis* (2015), 10<sup>th</sup> – 13<sup>th</sup> ed., Robert L. Boylestad
    - *Electronic Device and Circuit Theory* (2013), 11<sup>th</sup> ed., Robert L. Boylestad, Louis Nashelsky
    - *Microelectronics Circuit Analysis and Design* (2006), 4<sup>th</sup> ed., Donald A. Neamen
    - *Digital Electronics: Principles, Devices and Applications* (2007), Anil K. Maini

# Contact Your Instructor

- You can reach me through office in **Room 802, B1 Building**, HUST.
  - You should make an appointment by email before coming.
  - If you have urgent things, just come and meet me!
- You can also reach me at the following **email** any time. This is the best way to reach me!
  - [thuandc@soict.hust.edu.vn](mailto:thuandc@soict.hust.edu.vn)

# Course Contents

- The Concepts of Electronics for IT
- **Chapter 1: Passive Electronic Components and Applications**
- **Chapter 2: Semiconductor Components and Applications**
- **Chapter 3: Operational Amplifiers**
- **Chapter 4: Fundamentals of Digital Circuits**
- **Chapter 5: Logic Gates**
- **Chapter 6: Combinational Logic**
- **Chapter 7: Sequential Logic**

# Chapter 3:

## Operational Amplifiers


- Operational Amplifier
- Ideal Parameters
- Operational Amplifier Circuits
- Applications

# Operational Amplifier

- An **operational amplifier** (op-amp) is an integrated circuit that **amplifies the difference** between two input voltages and produces a single output.
- The op-amp is prevalent in analog electronics.
- The op-amp can be thought of as another electronic device (in much the same way as the bipolar or field-effect transistor).
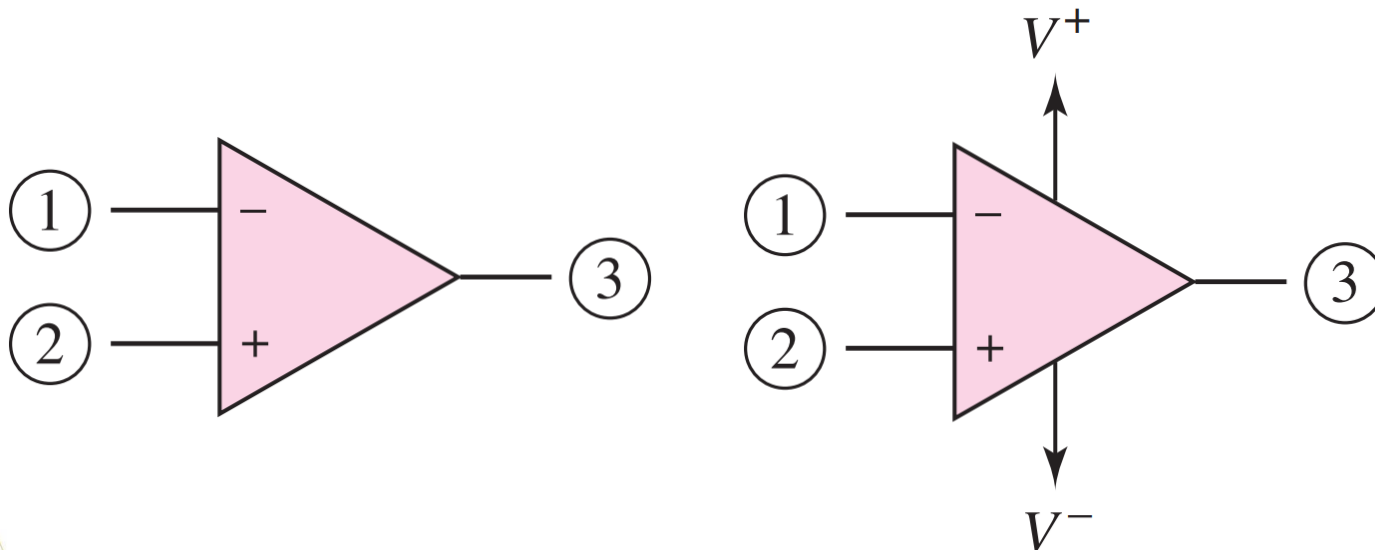
# Operational Amplifier


- 2 input terminals: ①-② and 1 output terminal: ③
- There are normally tens of transistors that make up an op-amp circuit → it requires dc power so that the transistors are biased in the active region.
- Most op-amps are biased with both a positive and a negative voltage supply,  $V^+$  and  $V^-$ .





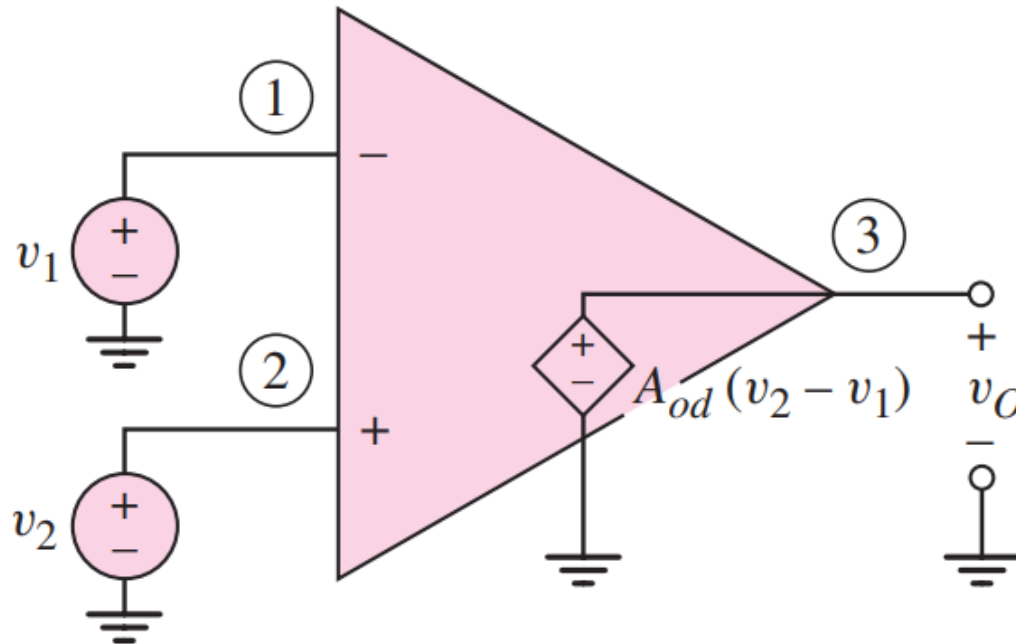
# Ideal Parameters

- The ideal op-amp **senses the difference** between two input signals and **amplifies this difference** to produce an output signal.
- The terminal voltage is the voltage at a terminal **measured with respect to ground**.



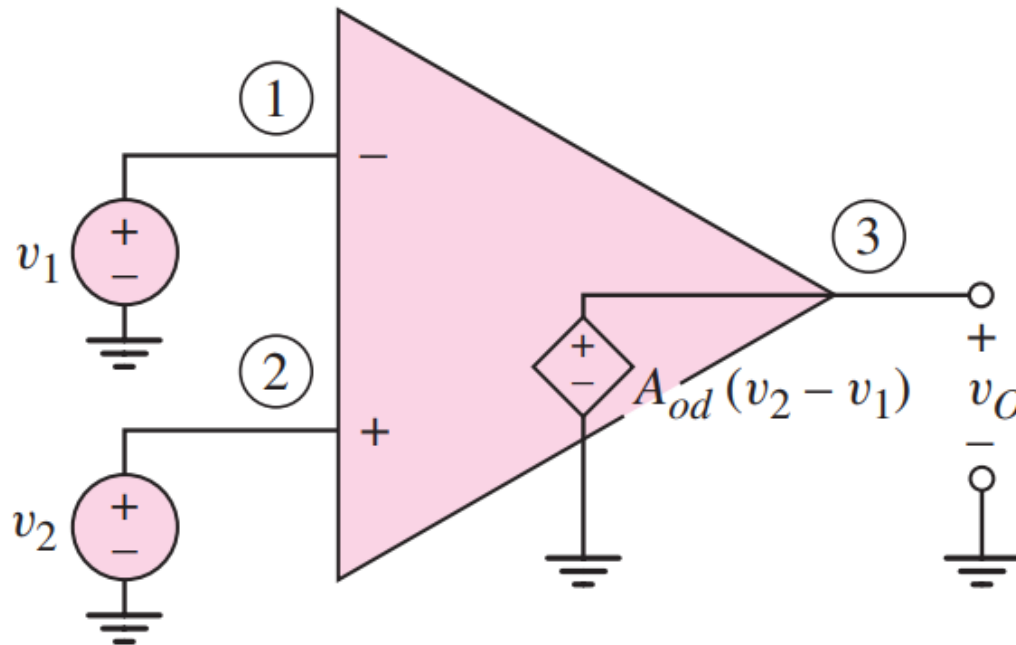
# Ideal Parameters

- The **input resistance** between ① and ② is **infinite**,  $R_i = \infty$   
→ the **input current** at each terminal is **zero**.
- The **output terminal** ③ of an ideal op-amp acts as the output of an **ideal voltage source** →  $R_o = 0$ .



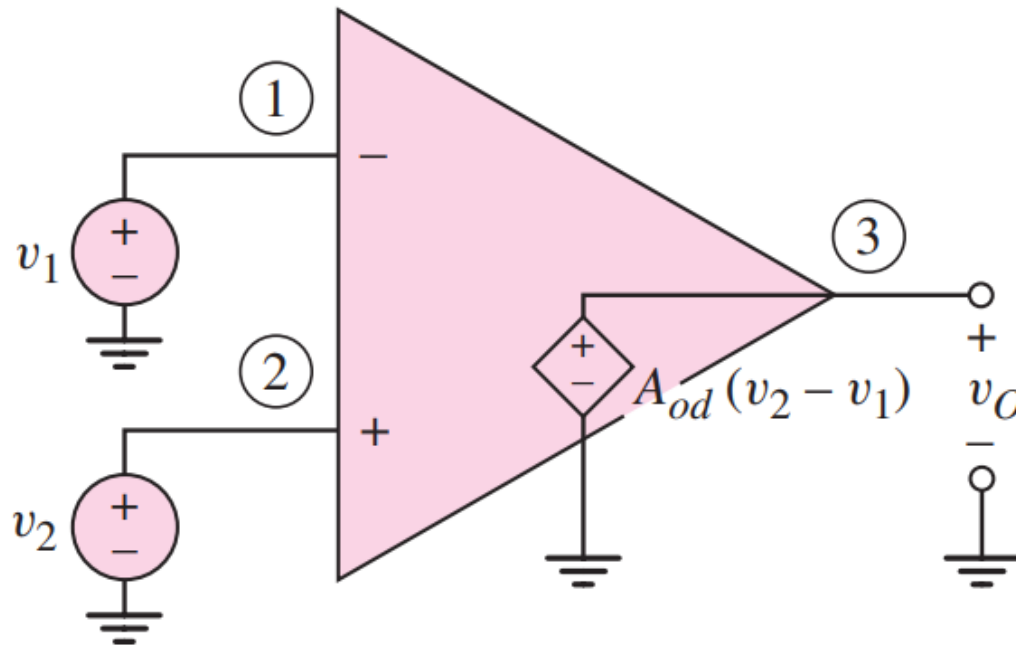
# Ideal Parameters

- $A_{od}$  the **open-loop differential voltage gain** of the op-amp.
- $A_{od}$  is very large and approaches to infinity.



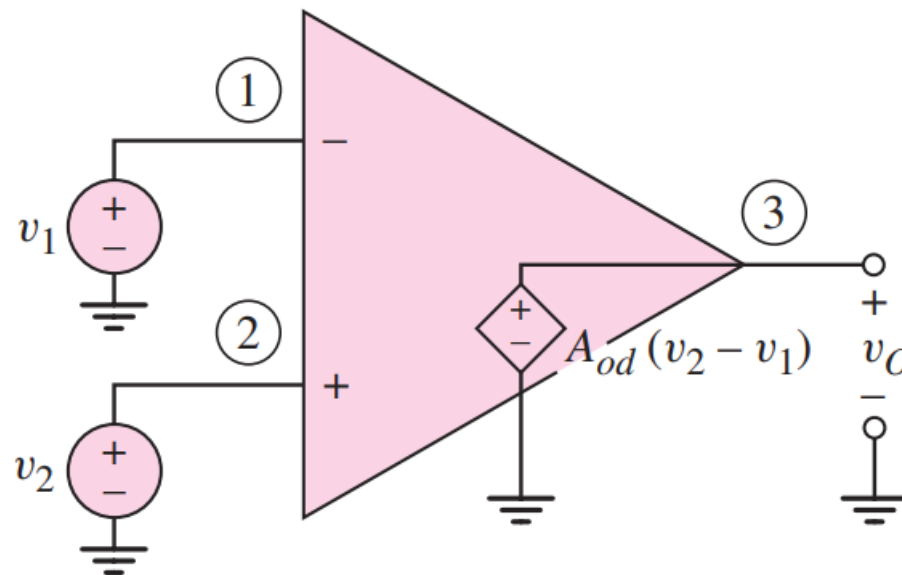
# Ideal Parameters

- The output is **out of phase** with respect to  $v_1$  and **in phase** with respect to  $v_2$
- $v_1$ : the **inverting input terminal**, designated by the “-” notation
- $v_2$ : the **noninverting input terminal**, designated by the “+” notation



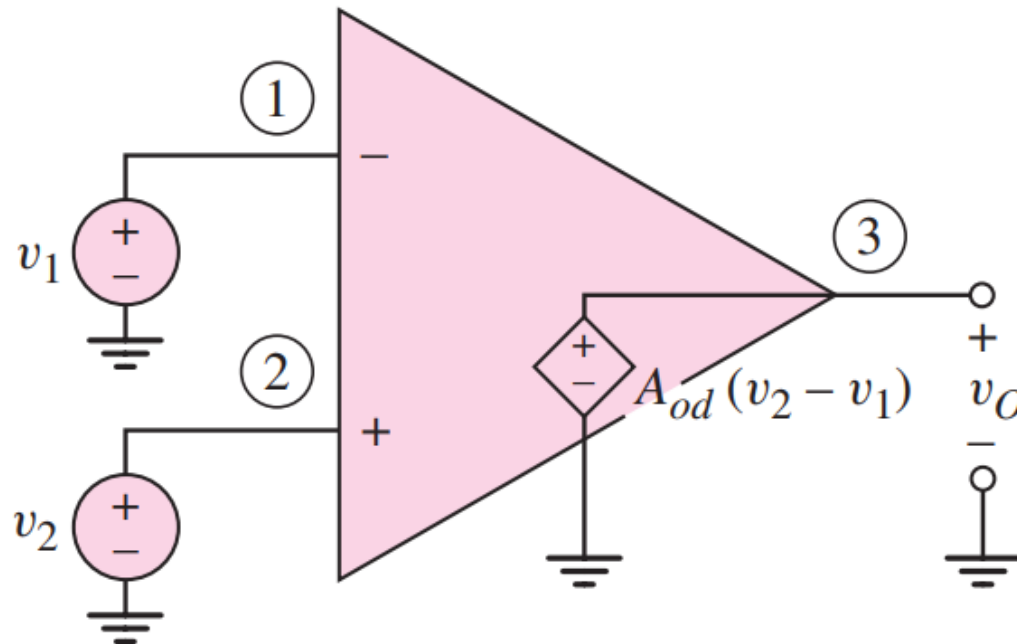
# Ideal Parameters

- The ideal op-amp responds only to the difference between the two input signals  $v_1$  and  $v_2$ .
- For  $v_1=v_2$ , the ideal op-amp maintains a **zero output** ( $v_O = 0$ ).



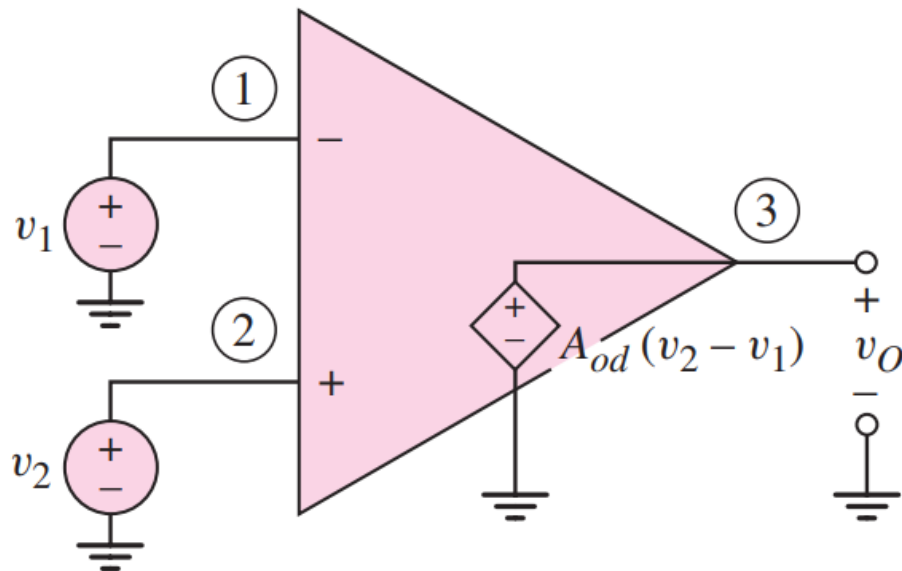
# Ideal Parameters

- When  $v_1 = v_2 \neq 0$ , there is a common-mode input signal.
- For the ideal op-amp, the common-mode output signal is zero.
- This characteristic is referred to as common-mode rejection.



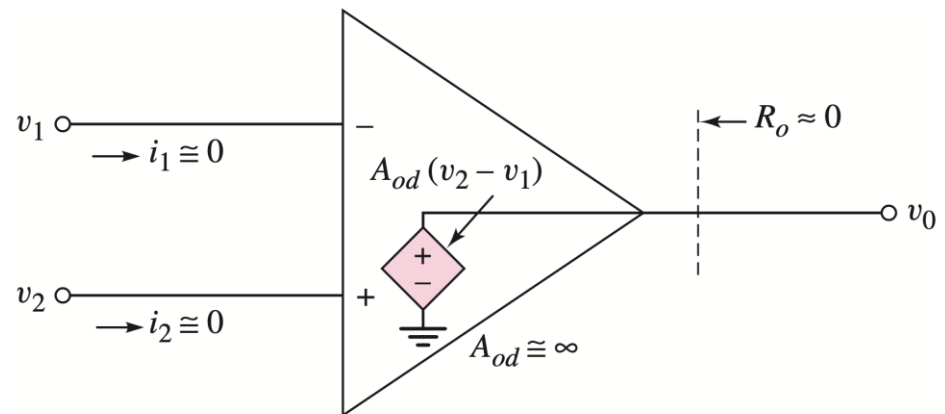
# Ideal Parameters

- For an ideal op-amp:  $A_{od} \cong \infty$
- If  $A_{od}$  is very large and  $v_o$  is finite:  $(v_2 - v_1) \cong 0$
- The effective input resistance to the op-amp is assumed to be infinite:  $i_1 \cong 0$   $i_2 \cong 0$
- The output resistance  $R_o \approx 0$  (ideal case)  $\rightarrow$  the output voltage is connected directly to the dependent voltage source, and it is independent of any load connected to the output.


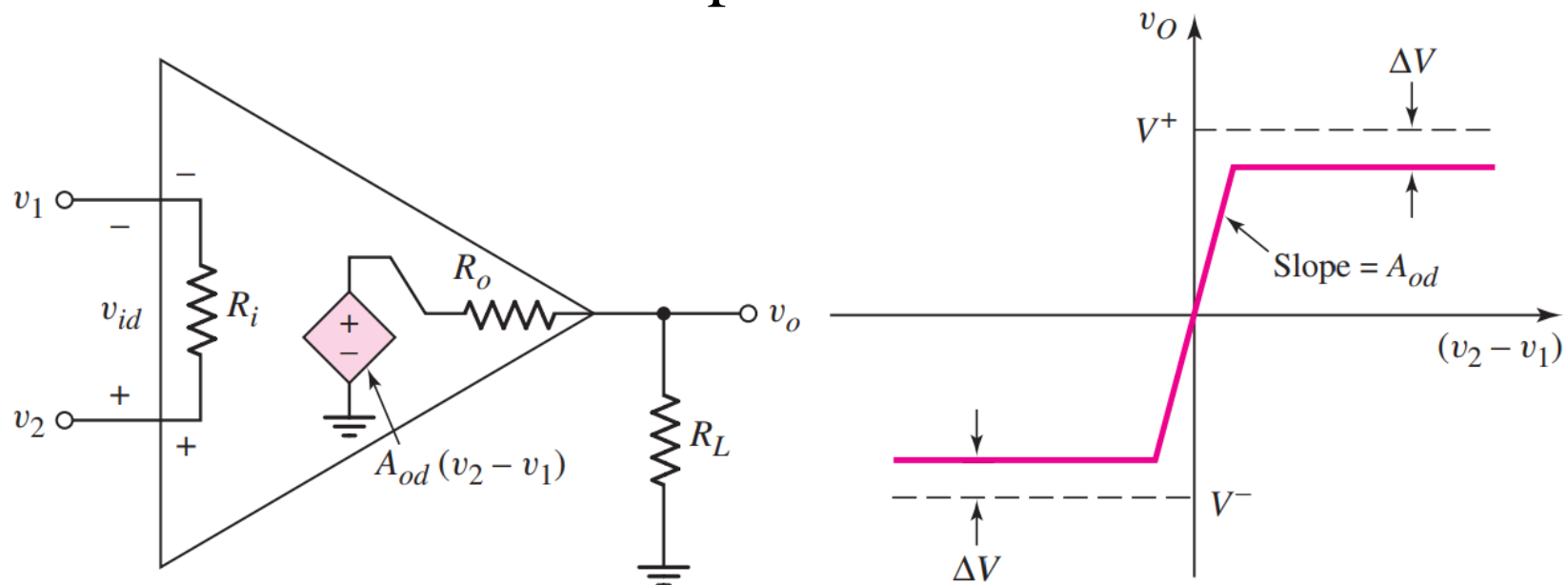
# Practical Op-amps


- The properties of a practical op-amp approach those of an ideal op-amp.
- If  $R_i$  is very large and  $R_o$  is very small, we can consider a practical op-amp as an ideal op-amp, and then can use it as a simple device.





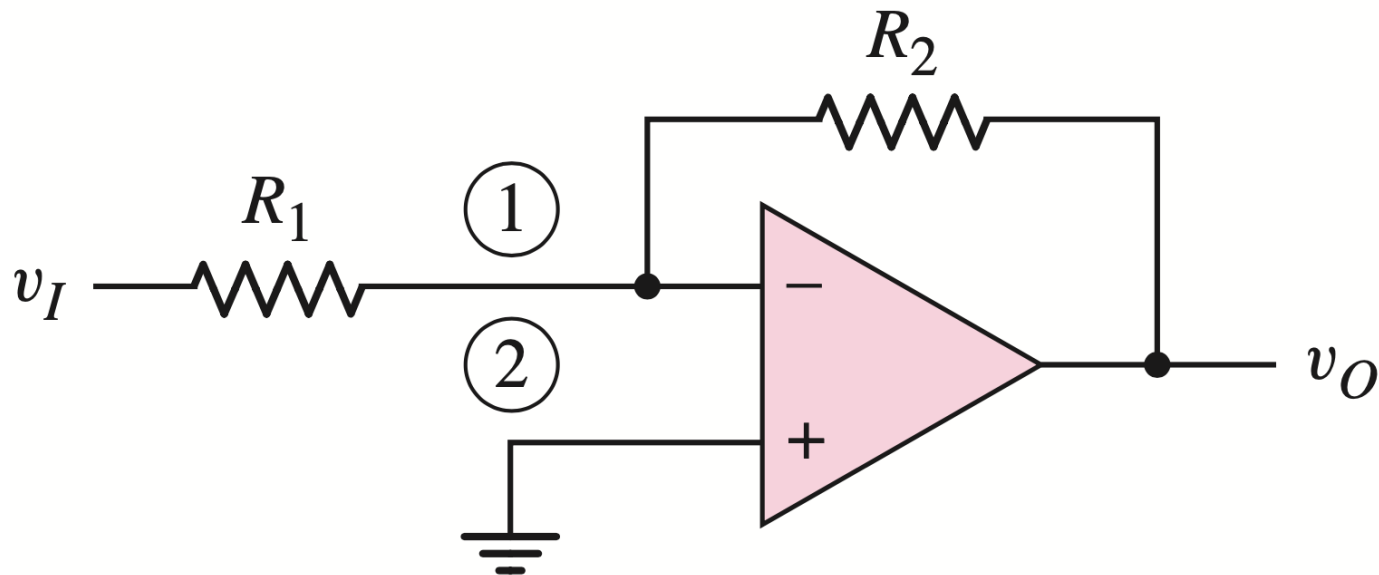
# Inverting Amplifier

- One of the most widely used op-amp circuits.
- Applying the **closed-loop configuration** for stability.
- The op-amp is biased with dc voltages (not shown in the figure).




# Inverting Amplifier

- Inverting op-amp equivalent circuit:

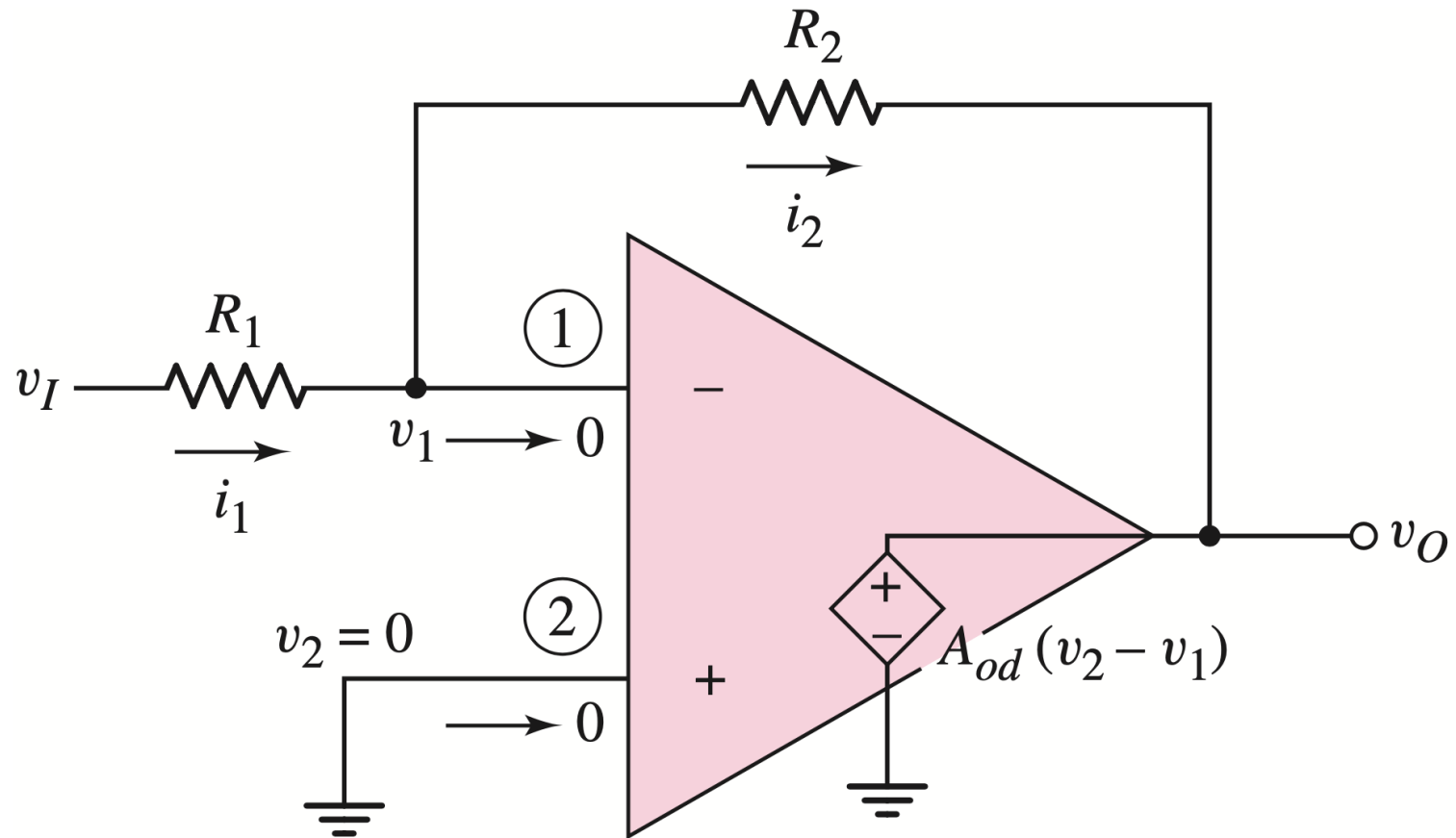

# Inverting Amplifier

Virtual ground,  $v_I = 0$

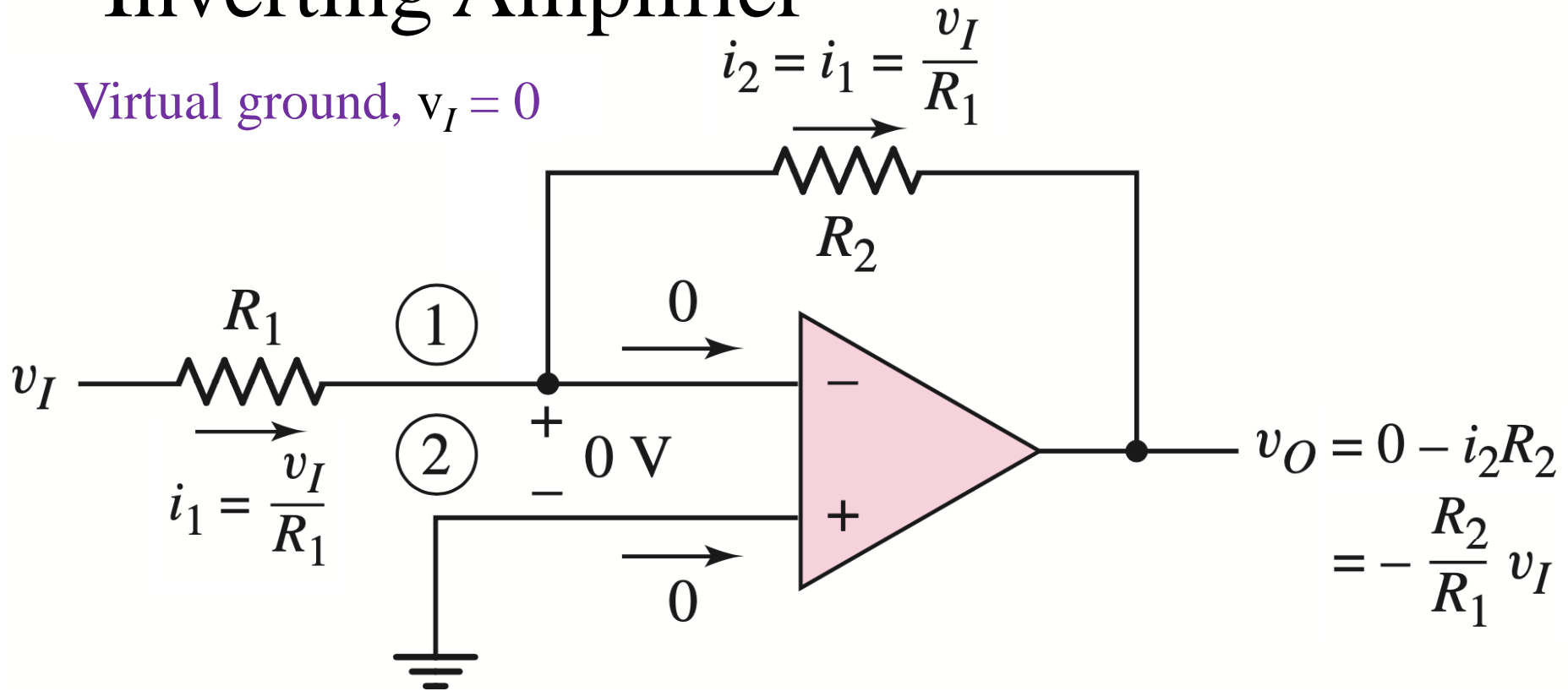


- Closed-loop voltage gain:
- Input resistance

$$A_v = \frac{v_O}{v_I} = -\frac{R_2}{R_1}$$

$$R_i = \frac{v_I}{i_1} = R_1$$
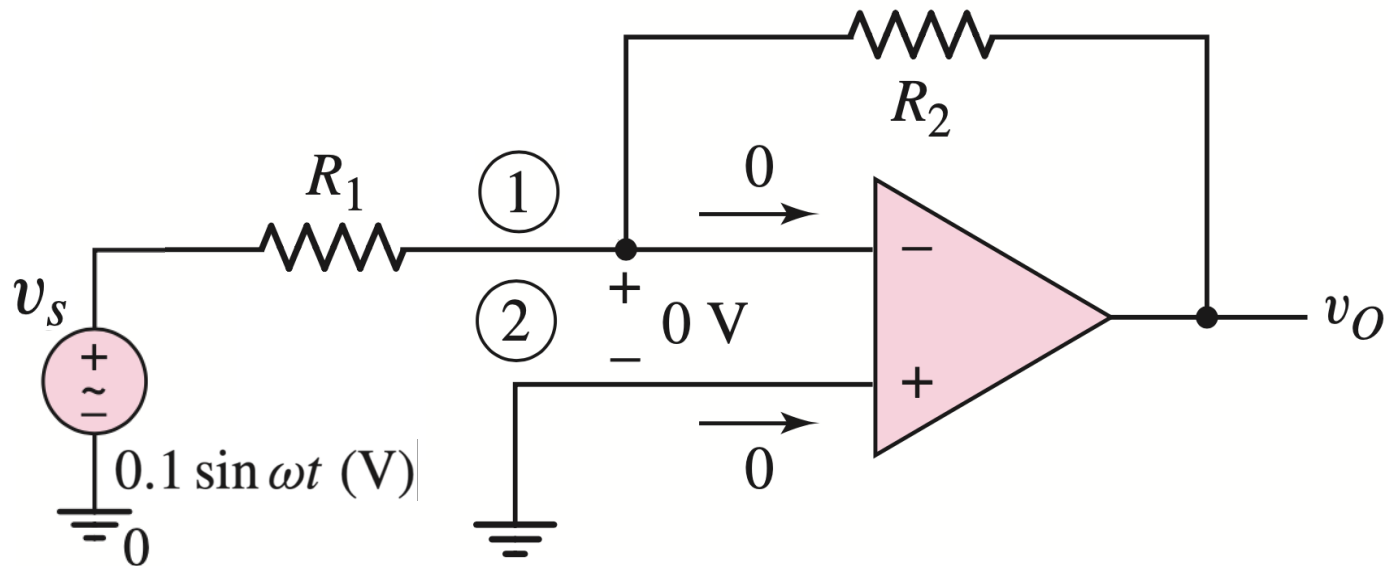
# Example 3.1

- Design an inverting amplifier with a specified voltage gain:  $v_s = 0.1 \sin \omega t$  (V) so that the voltage gain:  $A_v = -5$
- Assume that the source can supply a maximum current of  $5 \mu\text{A}$ .



# Example 3.1


$$R_1 = \frac{v_s(\max)}{i_1(\max)}$$

$$= \frac{0.1}{5 \times 10^{-6}}$$

$$\Rightarrow 20 \text{ k}\Omega$$


$$A_v = \frac{-R_2}{R_1} = -5$$
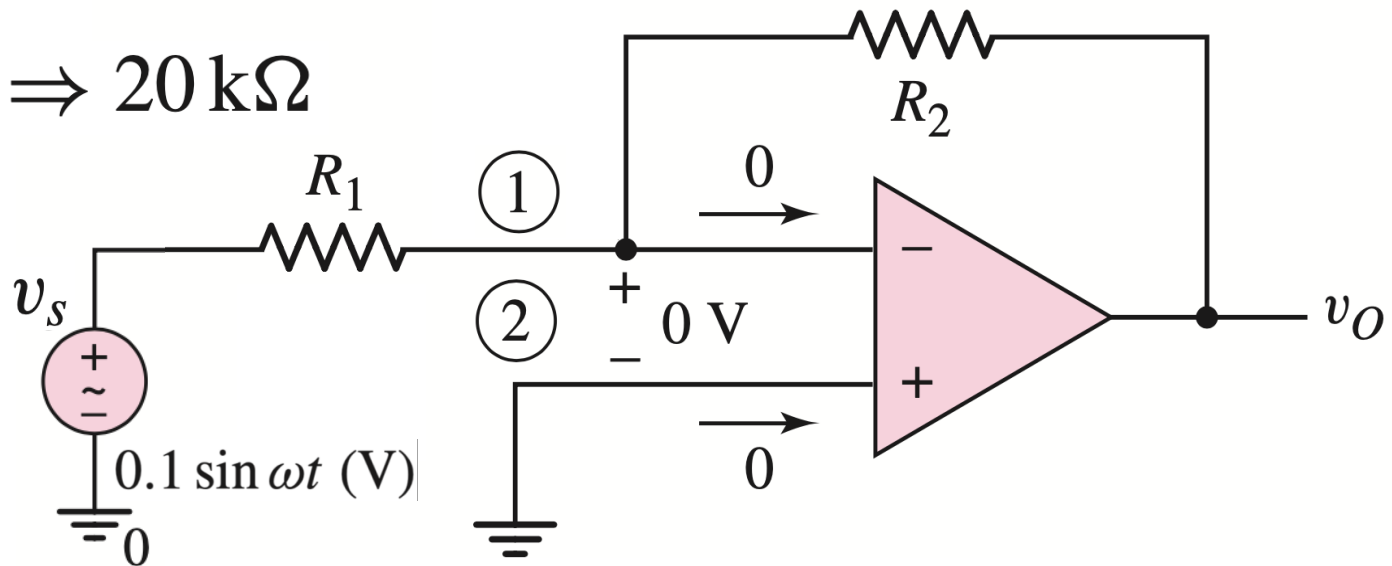
$$R_2 = 5R_1 = 5(20) = 100 \text{ k}\Omega$$


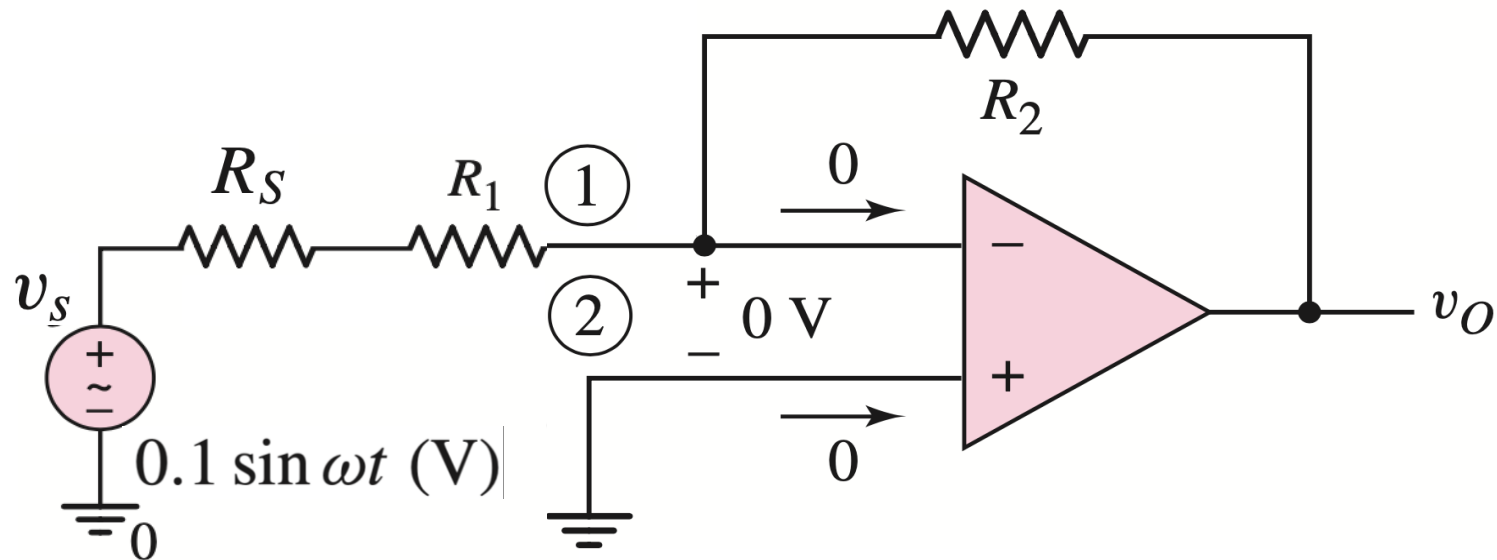
## Example 3.2

- Similar to Example 3.1, except that  $R_S = 1 \text{ k}\Omega$




## Example 3.2

$$R_1 + R_S = \frac{v_s(\max)}{i_1(\max)} = \frac{0.1}{5 \times 10^{-6}} \Rightarrow 20 \text{ k}\Omega$$

$$R_S = 1 \text{ k}\Omega$$

$$\Rightarrow R_1 = 19 \text{ k}\Omega$$
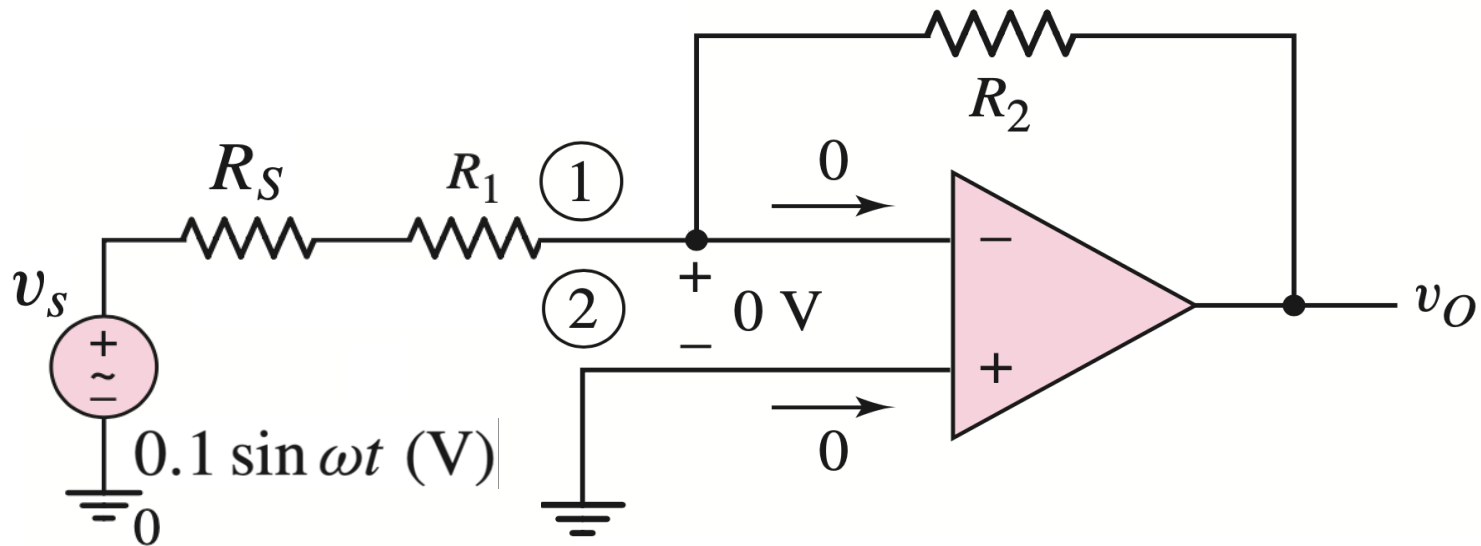
$$R_2 = 5(R_1 + R_S) = 5(19 + 1) = 100 \text{ k}\Omega$$



# Problem-Solving Technique: Ideal Op-Amp Circuits


1. If the (+) terminal of the op-amp is **at ground potential**, then the (-) terminal is at virtual ground. Sum currents at this node, assuming zero current enters the op-amp itself.
2. If the (+) terminal of the op-amp is **not at ground potential**, then the (-) terminal is equal to that at the (+) terminal. Sum currents at the (-) terminal node, assuming zero current enters the op-amp itself.
3. For the ideal op-amp circuit, the output voltage is determined from either Step 1 or Step 2 above and is independent of any load connected to the output terminal.



# Noninverting Amplifier

- The input voltage  $v_I$  is applied directly to the (+) terminal, while one side of  $R_1$  is connected to the (-) terminal and the other side is at ground.
- Due to the negative feedback connection,  $v_1$  and  $v_2$  are essentially equal (i.e. **virtual short**).


$$\Rightarrow v_1 = v_2$$

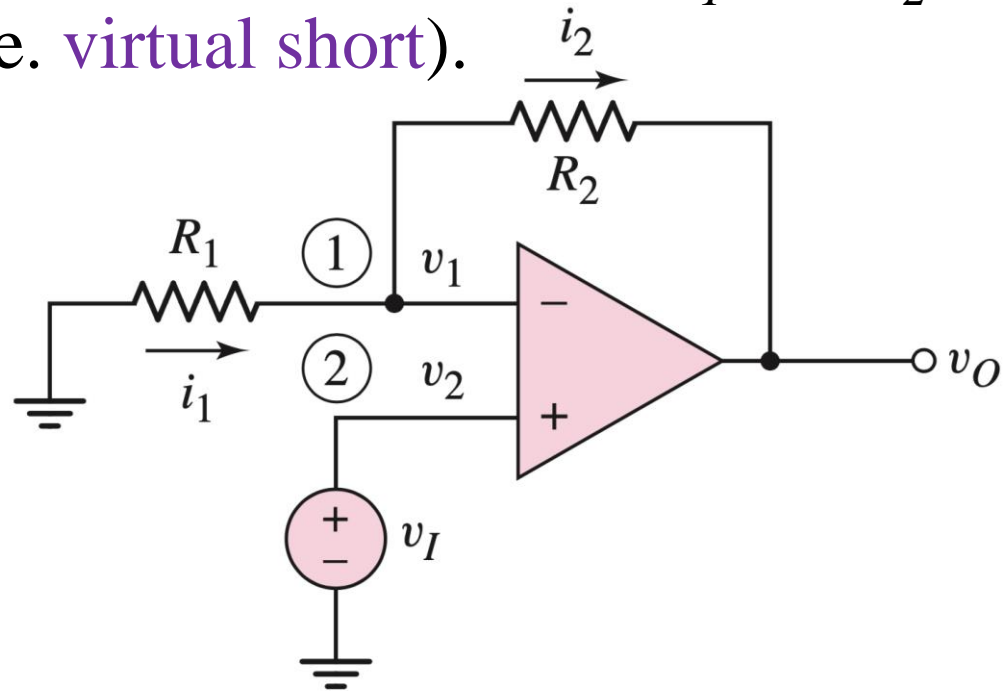
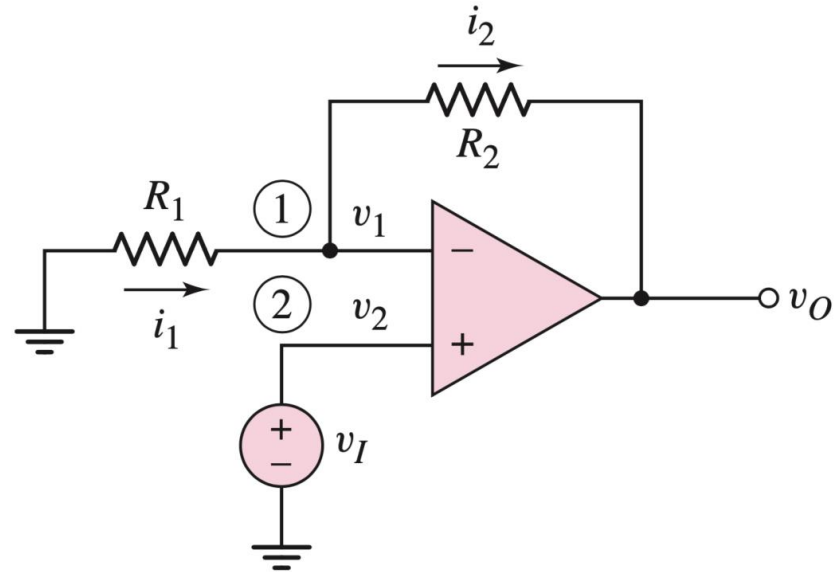
# Noninverting Amplifier

$$i_1 = -\frac{v_1}{R_1} = -\frac{v_I}{R_1}$$

$$i_2 = \frac{v_1 - v_O}{R_2} = \frac{v_I - v_O}{R_2}$$




$$\Rightarrow A_v = \frac{v_O}{v_I} = 1 + \frac{R_2}{R_1}$$

- As before:

$$i_1 = i_2 \Rightarrow -\frac{v_I}{R_1} = \frac{v_I - v_O}{R_2}$$
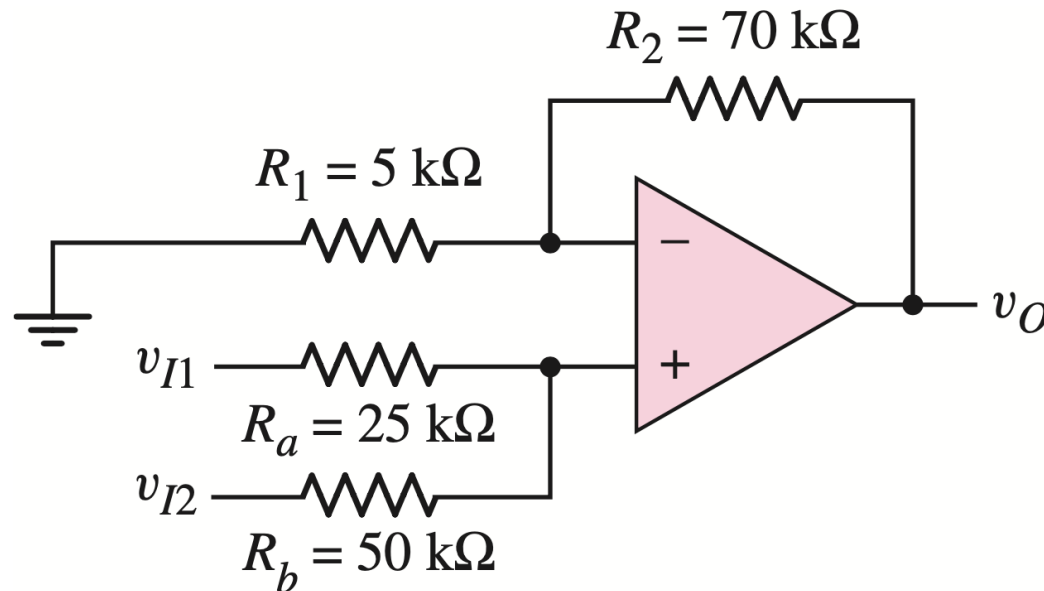
## Example 3.3

- Use superposition to determine the output voltage  $v_O$  in the ideal op-amp circuit in the following figure:





- Answer:  $v_O = 10v_{I1} + 5v_{I2}$

# Comparator

- A **comparator** is a circuit that can determine if an input voltage exceeds a certain level.
- When an op-amp is used as a comparator, there is **no negative feedback**.
- The op-amp output will be saturated in one of two states (usually a positive or negative voltage).
- **Zero-Level Detection**
- **Nonzero-Level Detection**

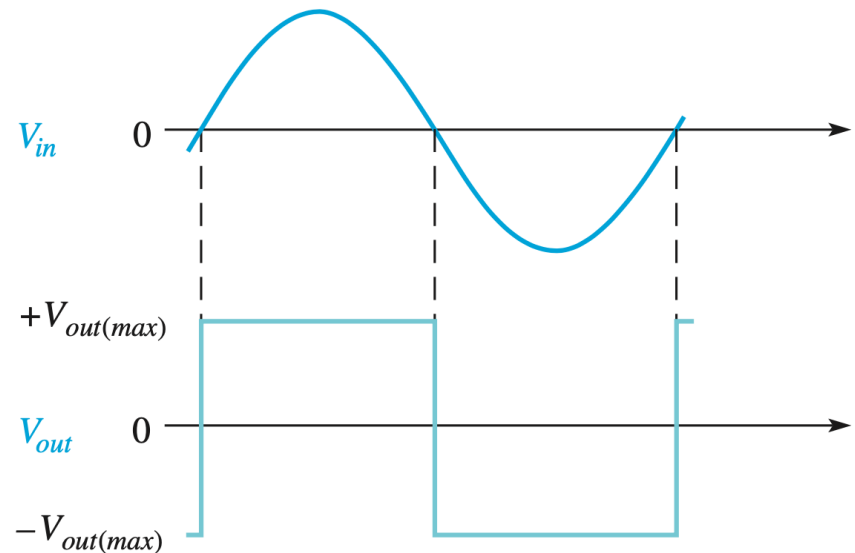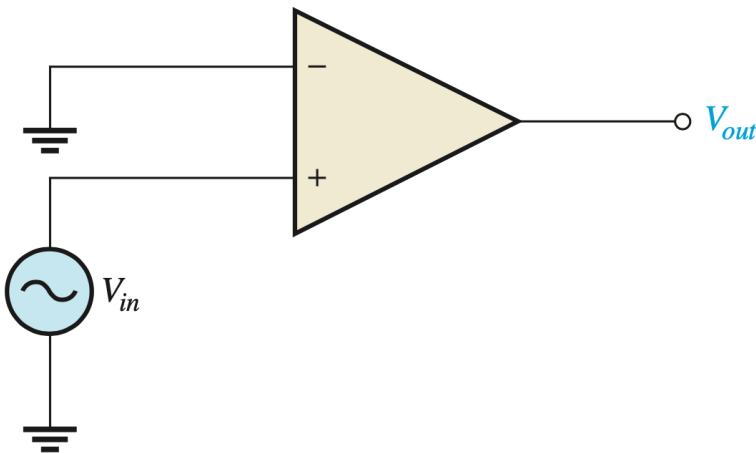
# Zero-Level Detection

- The inverting input is grounded and will serve as a **0V reference**.
- The signal is applied to the noninverting input.
- As the input signal crosses the 0V reference point, the output suddenly switches from one saturated state to the other.




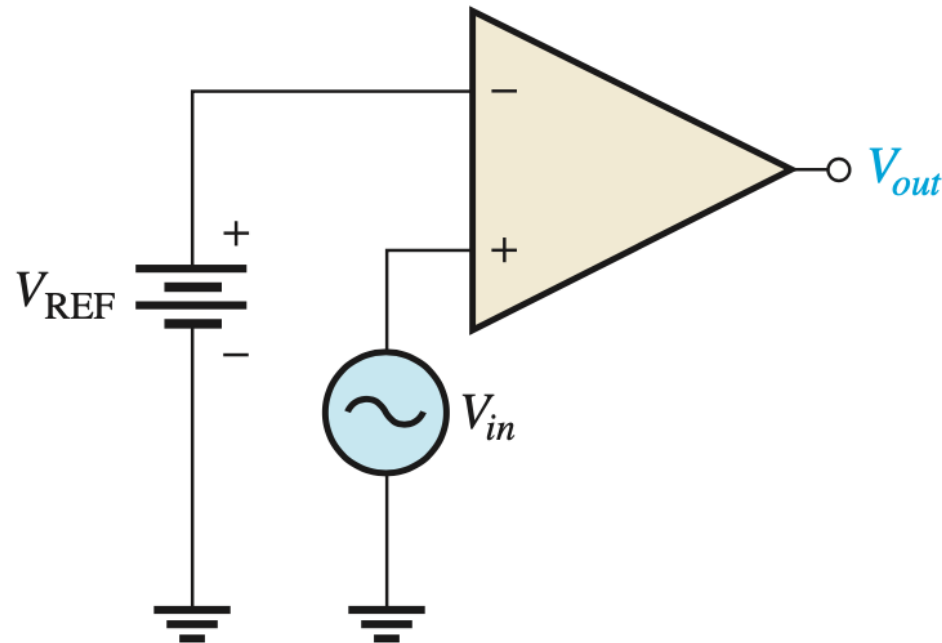
# Nonzero-Level Detection

- Connecting a **fixed reference** to the (-) input of the op-amp (instead of the 0V reference).



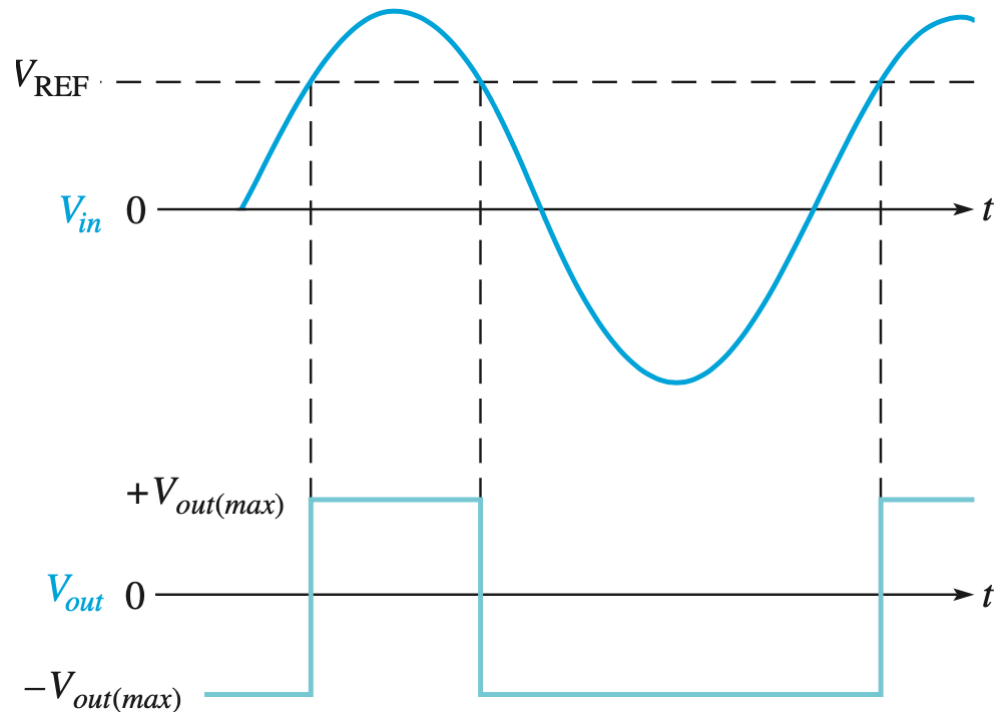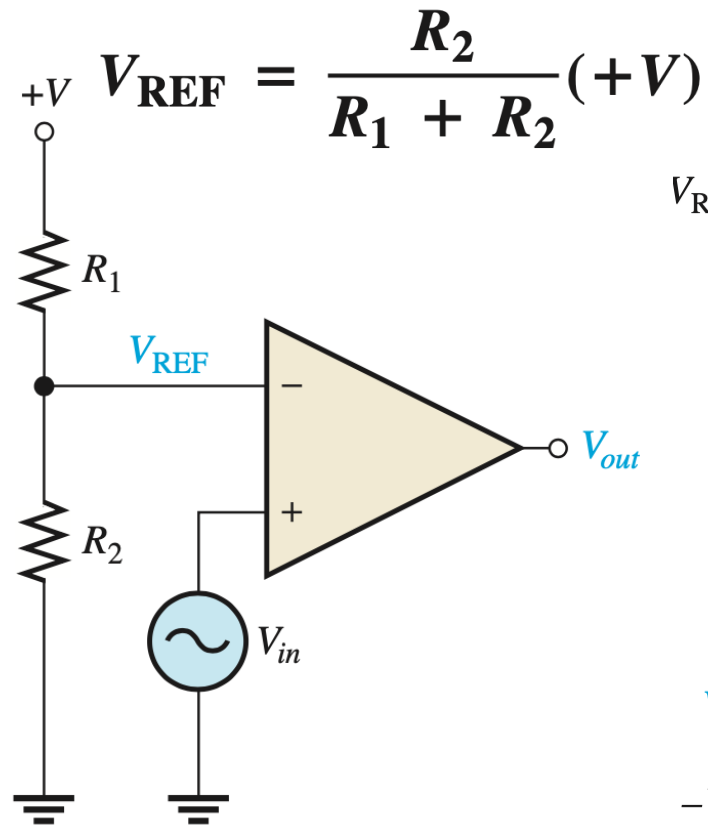
# Nonzero-Level Detection

- A practical arrangement is to use a voltage divider to set the reference voltage:


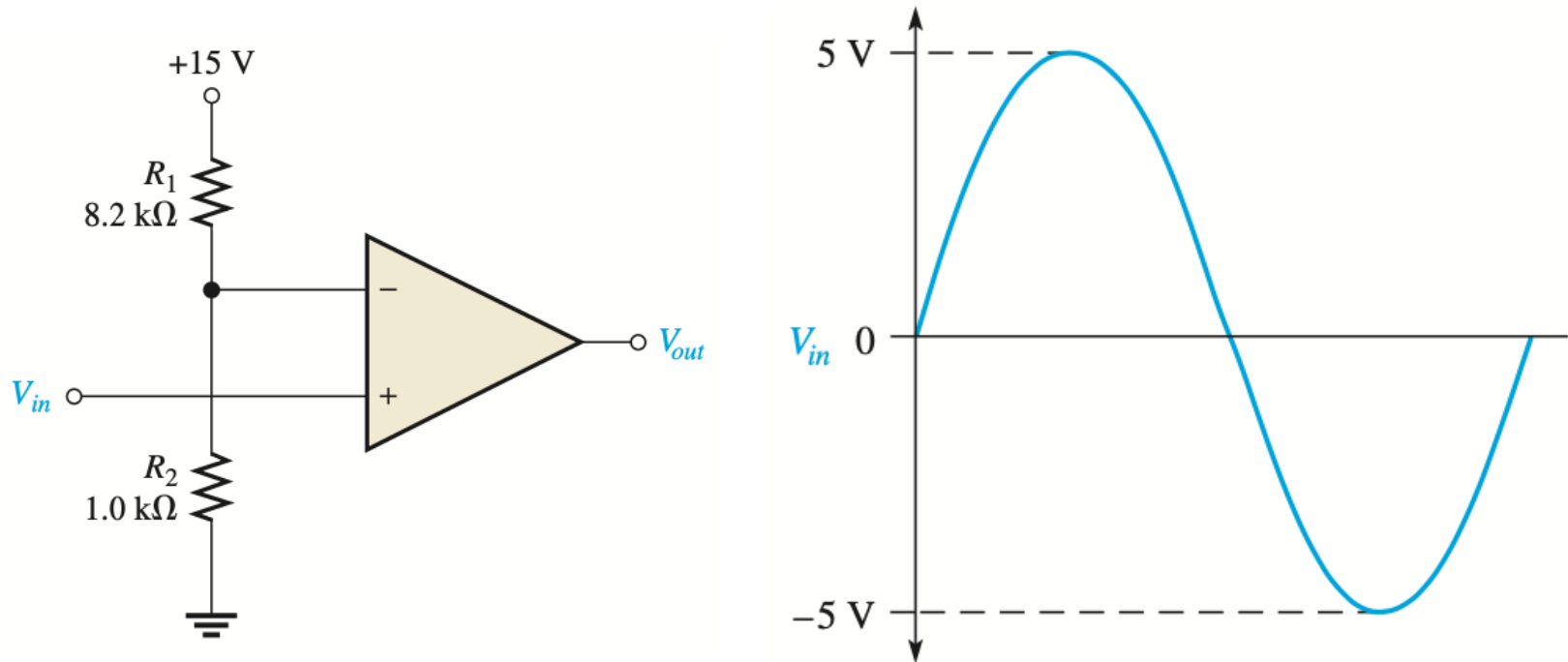
# Example 3.4



- The input signal is applied to the comparator circuit. Draw the output showing its proper relationship to the input signal. Assume that the maximum output levels of the op-amp are 12V.





# Example 3.4


- Reference voltage:

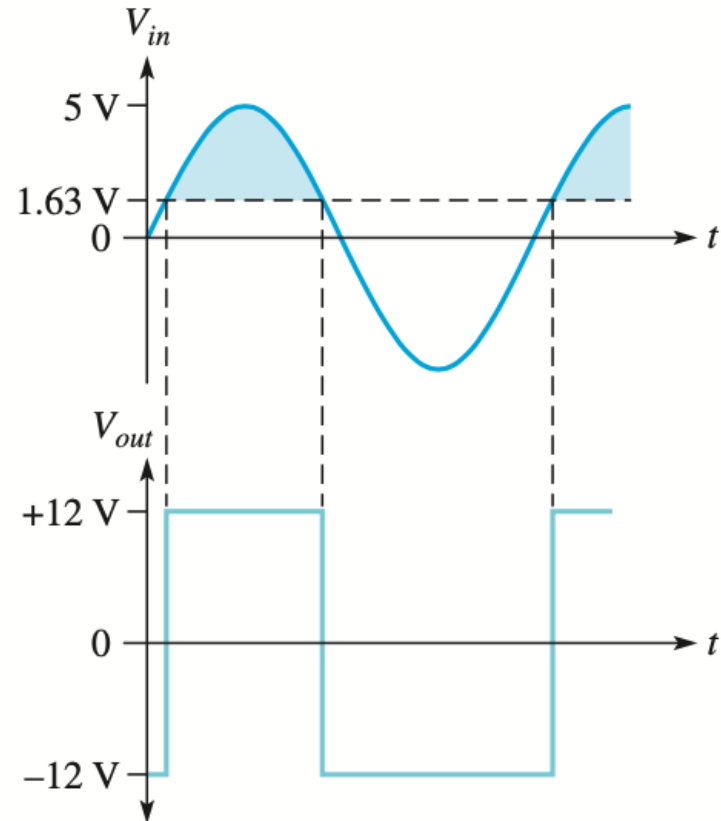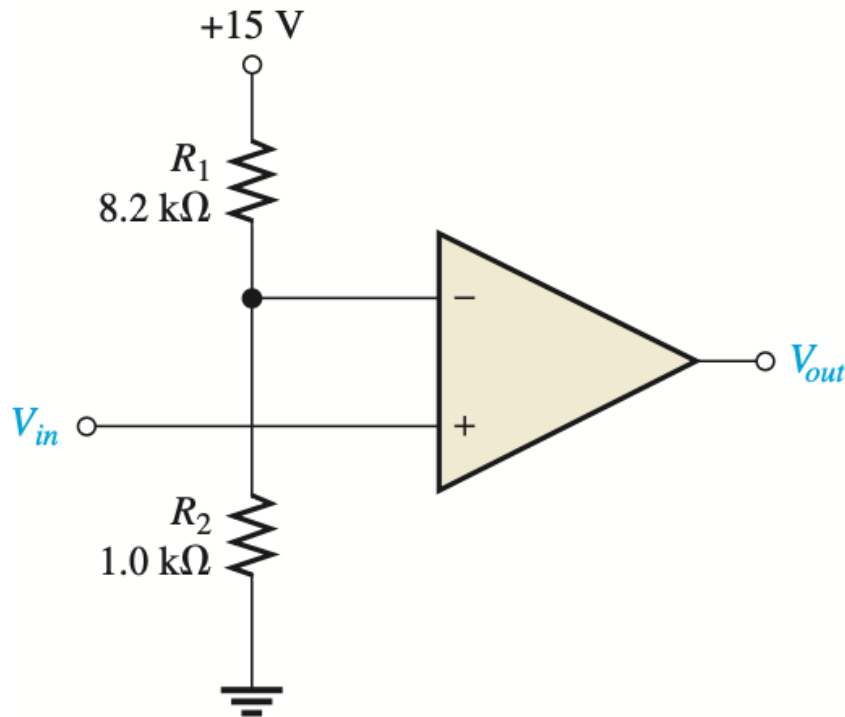



$$V_{\text{ref}} = \frac{R_2}{R_1 + R_2} (+V) = \frac{1.0}{8.2 + 1.0} \times 15 = 1.63\text{ V}$$
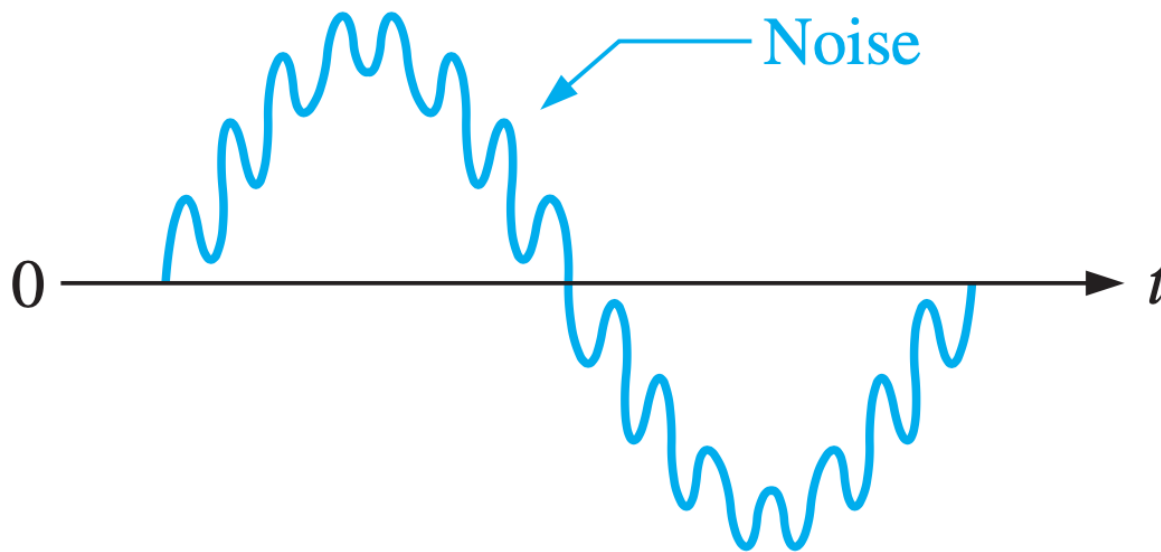
# Effects of Input Noise on Comparator


- Consider the sine wave with superimposed noise:



# Effects of Input Noise on Comparator

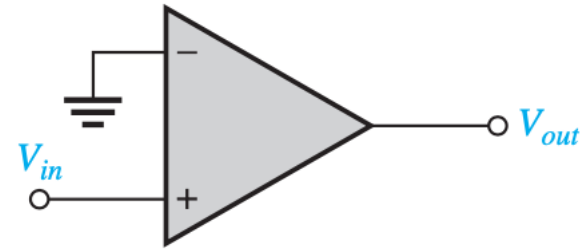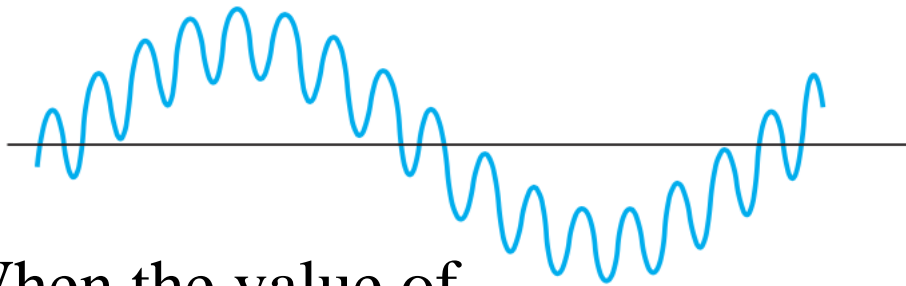

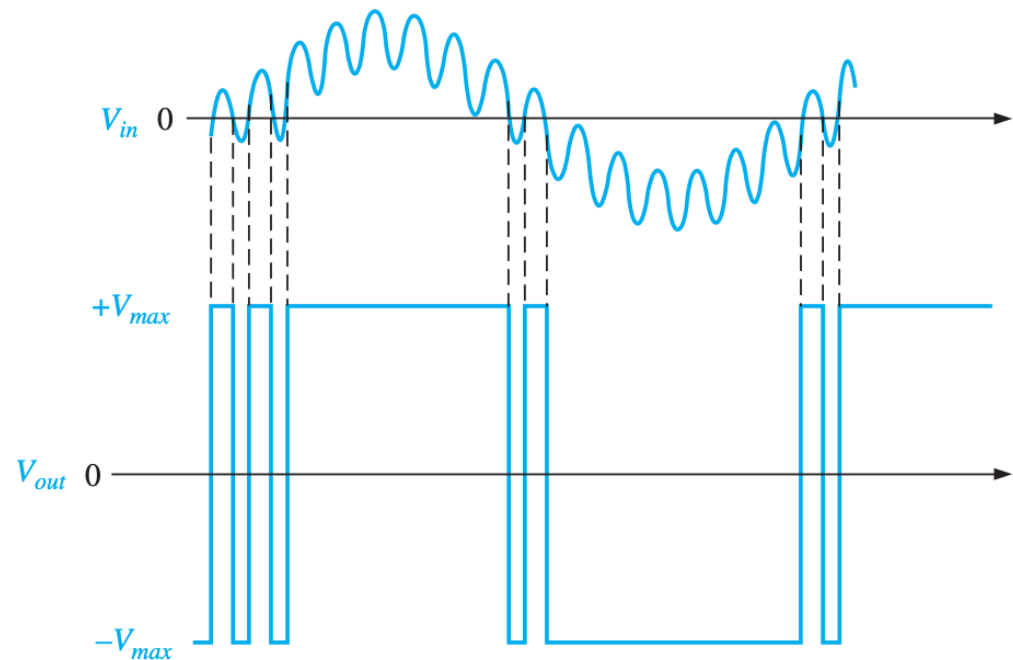
When the value of sine wave goes to the zero the variation caused by the noise can cause the **net input fluctuate over zero value** certain time.



Faulty output voltage

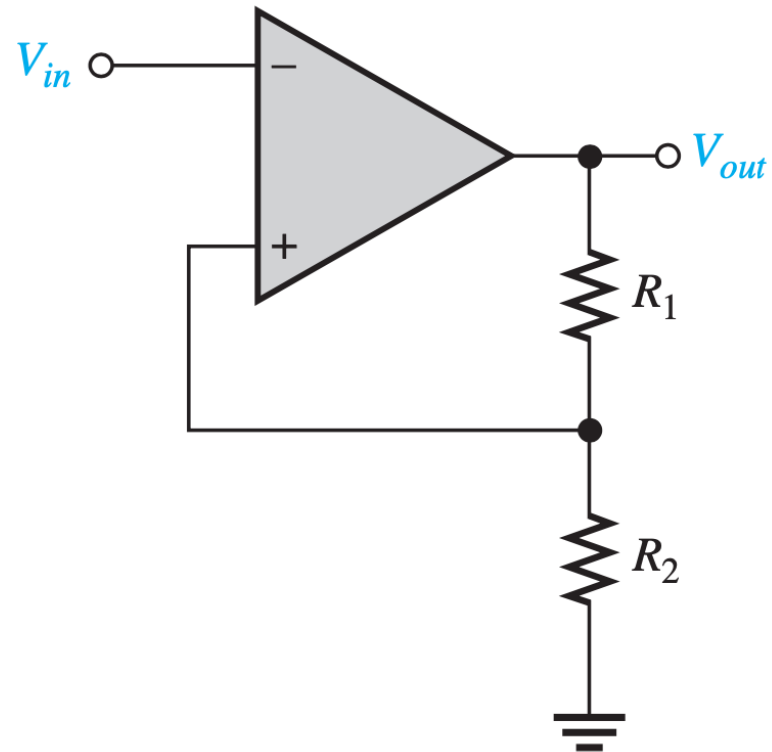
# Effects of Input Noise on Comparator

- To decrease the response of comparator towards the noise the method incorporating **positive feedback** (aka **hysteresis**) is used.
- 2 reference points:
  - $V_{LTP}$ : **lower trigger point**
  - $V_{UTP}$ : **upper trigger point**



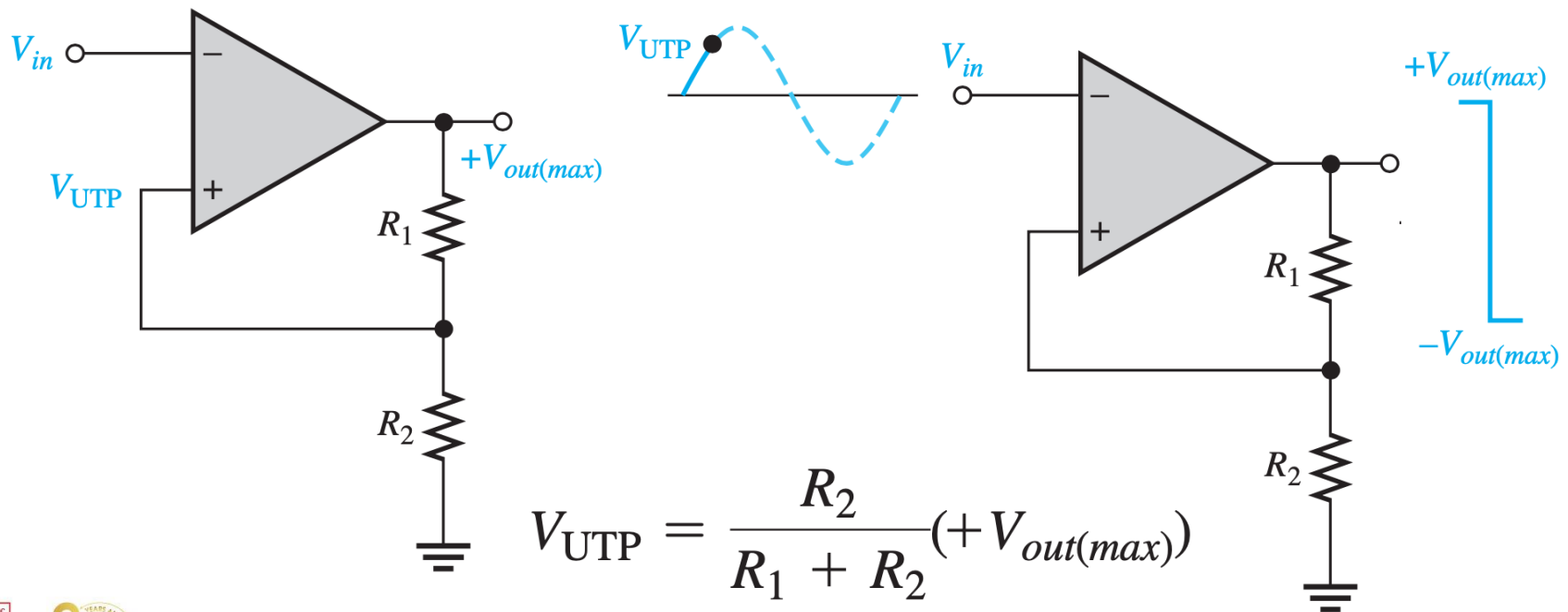
# Effects of Input Noise on Comparator

- For  $V_{in} < V_{UTP}$ ,  $V_{out}$  is locked at  $+V_{out(max)}$  (extreme positive value)
- For  $V_{in} > V_{UTP}$ ,  $V_{out}$  is locked at  $-V_{out(max)}$  (extreme negative value)


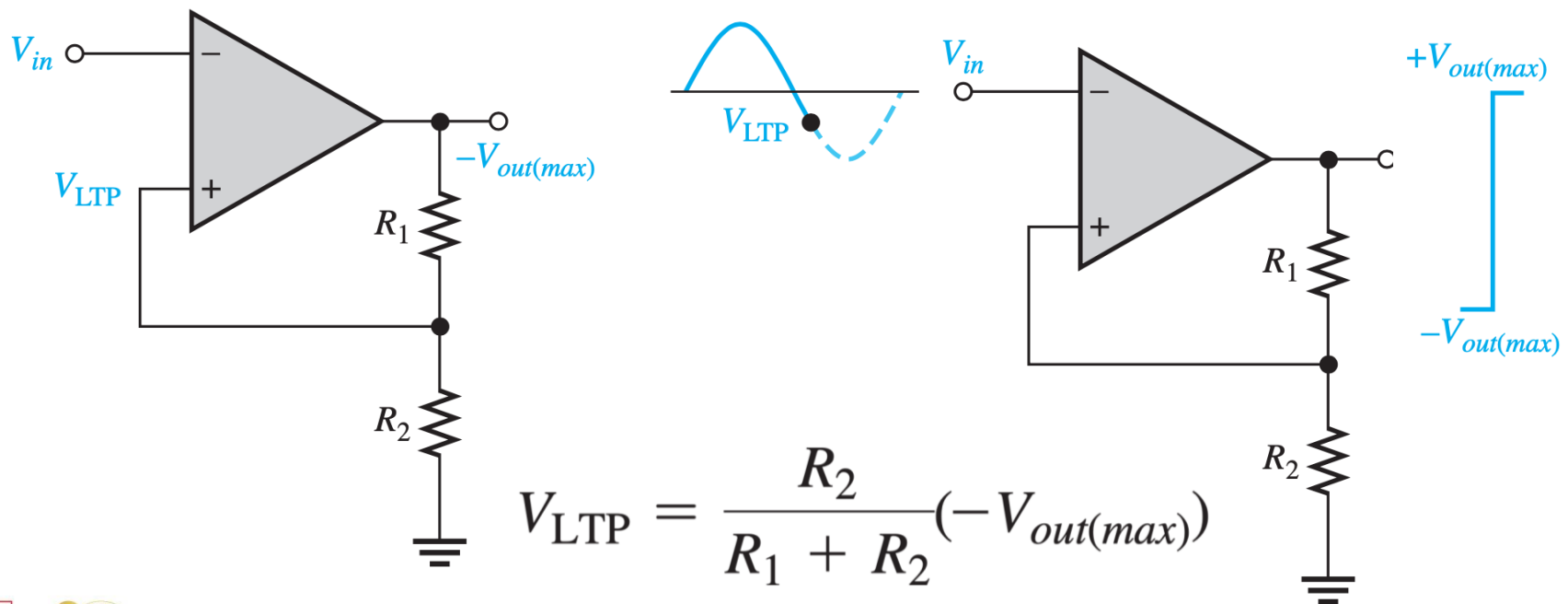
# Effects of Input Noise on Comparator


- For  $V_{in} > V_{LTP}$ ,  $V_{out}$  is locked at  $-V_{out(max)}$  (extreme negative value)
- For  $V_{in} < V_{LTP}$ ,  $V_{out}$  is locked at  $+V_{out(max)}$  (extreme positive value)


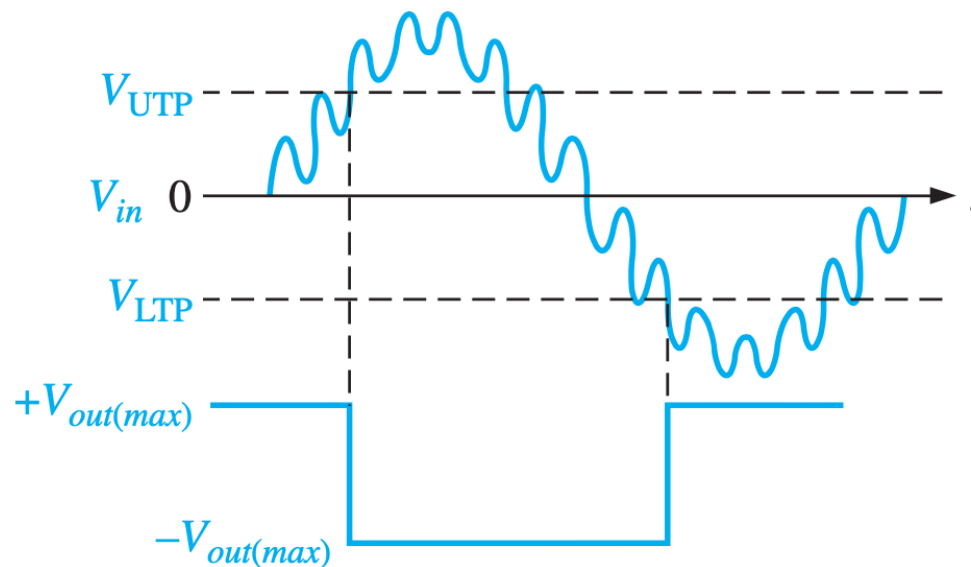
# Effects of Input Noise on Comparator

- The comparator created with the hysteresis is called a **Schmitt trigger**.
  - Less quantity of noise voltage provides no influence at the output.

$$V_{\text{HYS}} = V_{\text{UTP}} - V_{\text{LTP}}$$




# Example 3.5

- Consider the following circuit.
- Assume:  $+V_{out(max)} = +5\text{ V}$  and  $-V_{out(max)} = -5\text{ V}$
- Find:  $V_{UTP}$   $V_{LTP}$   $V_{HYS}$

$$\begin{aligned} V_{UTP} &= \frac{R_2}{R_1 + R_2} (+V_{out(max)}) \\ &= 0.5(5\text{ V}) = \mathbf{+2.5\text{ V}} \end{aligned}$$

$$\begin{aligned} V_{LTP} &= \frac{R_2}{R_1 + R_2} (-V_{out(max)}) \\ &= 0.5(-5\text{ V}) = \mathbf{-2.5\text{ V}} \end{aligned}$$
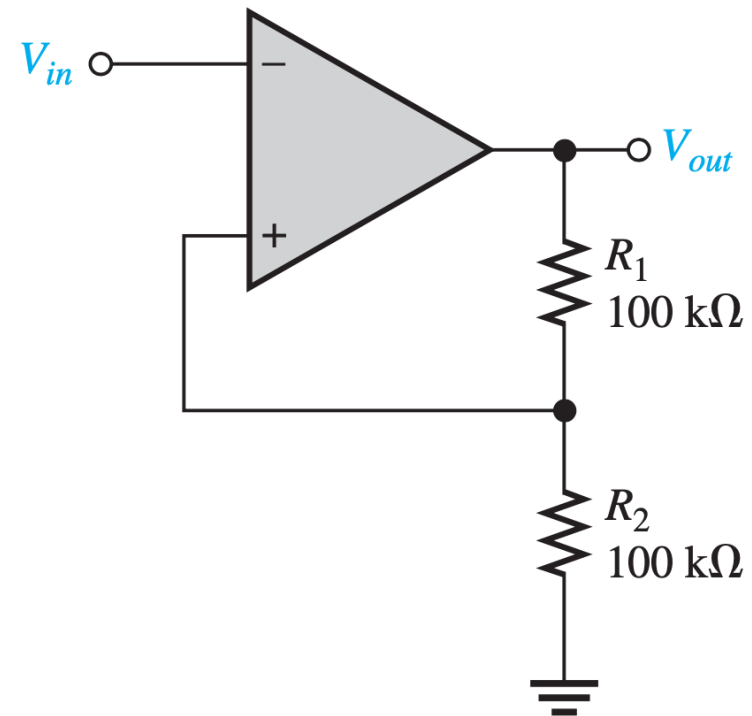
$$\begin{aligned} V_{HYS} &= V_{UTP} - V_{LTP} \\ &= 2.5\text{ V} - (-2.5\text{ V}) = \mathbf{5\text{ V}} \end{aligned}$$






# Summing Amplifier

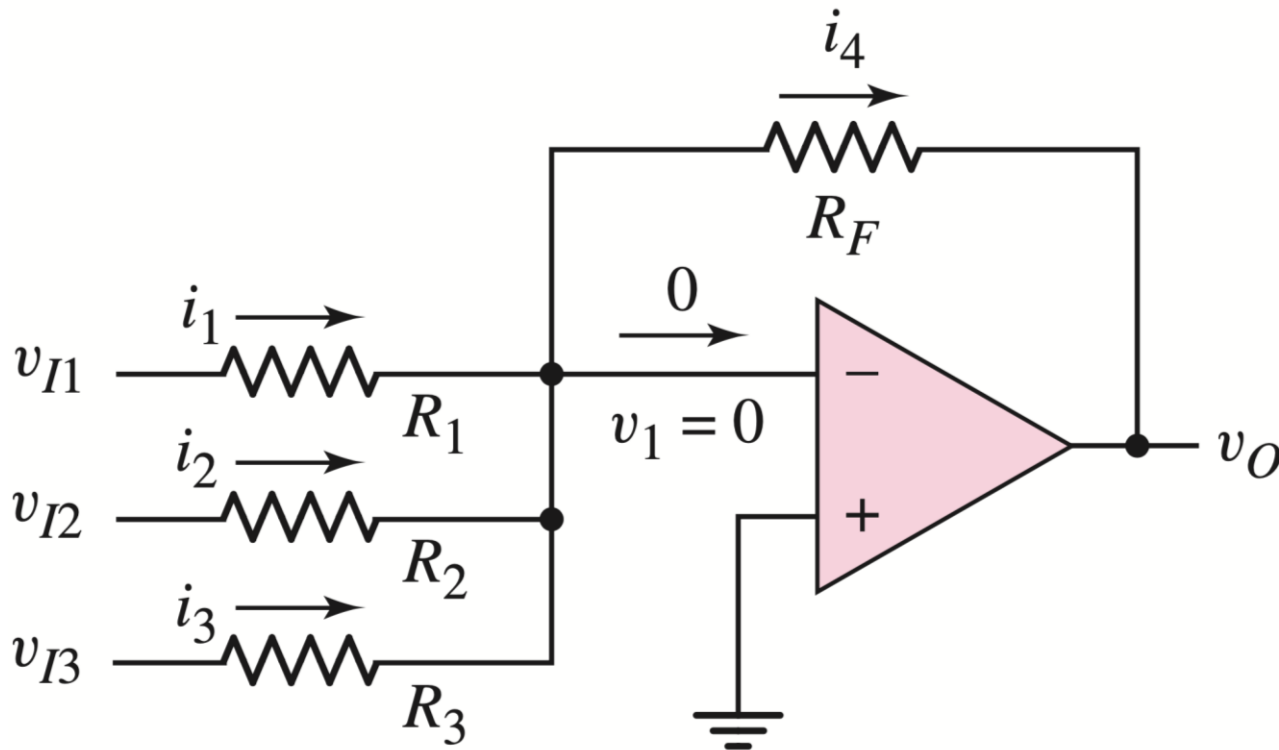
## Objective:

- Analyze and understand the characteristics of the summing operational amplifier.


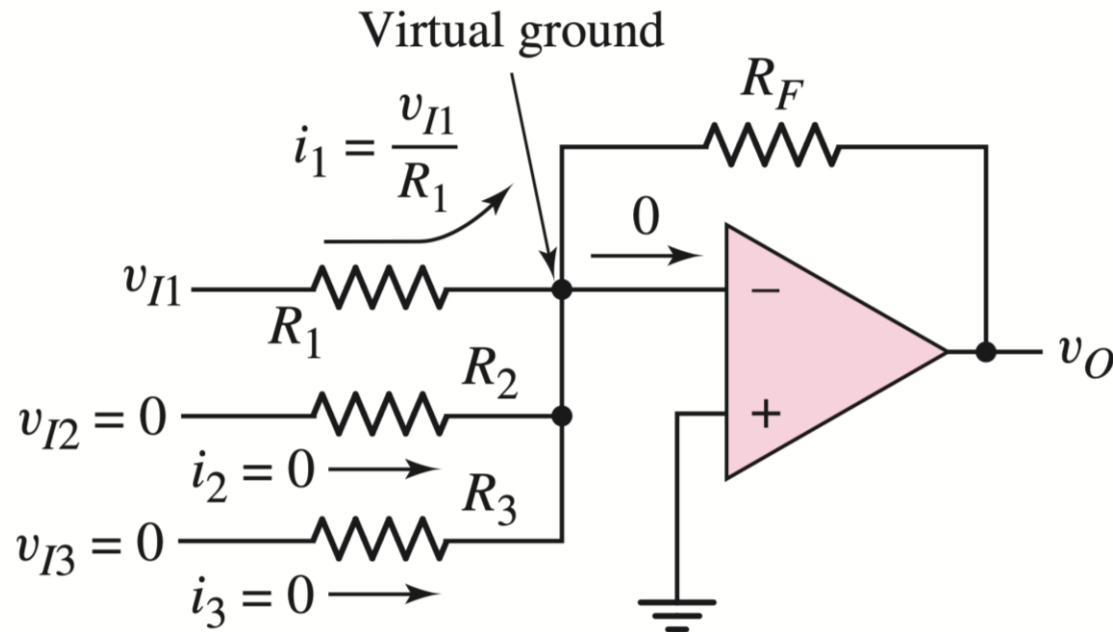
# Summing Amplifier

- To analyze the op-amp circuit, use the **superposition theorem** and the **concept of virtual ground**.
- Algebraically sum these terms to determine the total output.



# Summing Amplifier

- If we set:

$$v_{I2} = v_{I3} = 0 \Rightarrow i_1 = \frac{v_{I1}}{R_1}$$

- We have:

$$\begin{aligned} v_O(v_{I1}) &= -i_1 R_F \\ &= -\left(\frac{R_F}{R_1}\right) v_{I1} \end{aligned}$$


- Similarly, we have:

$$\begin{cases} v_O(v_{I2}) = -i_2 R_F = -\left(\frac{R_F}{R_2}\right) v_{I2} \\ v_O(v_{I3}) = -i_3 R_F = -\left(\frac{R_F}{R_3}\right) v_{I3} \end{cases}$$

- The total voltage:


$$v_O = v_O(v_{I1}) + v_O(v_{I2}) + v_O(v_{I3})$$
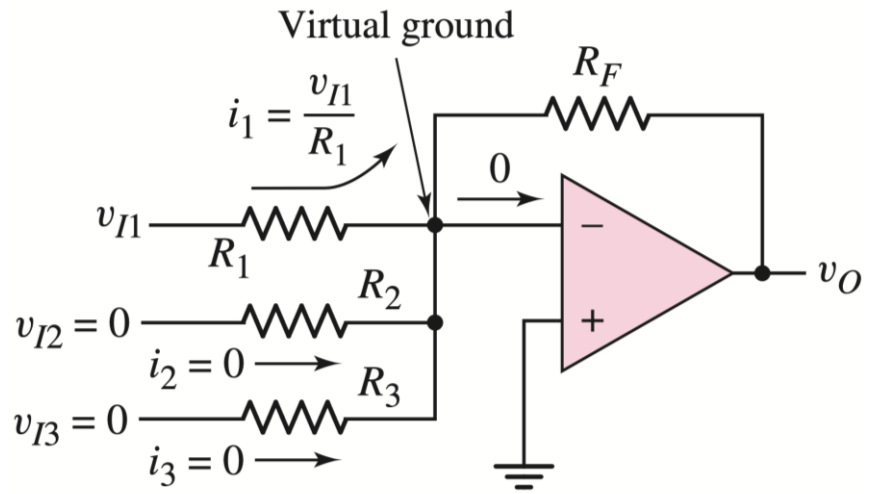
$$\Rightarrow v_O = -\left(\frac{R_F}{R_1} v_{I1} + \frac{R_F}{R_2} v_{I2} + \frac{R_F}{R_3} v_{I3}\right)$$


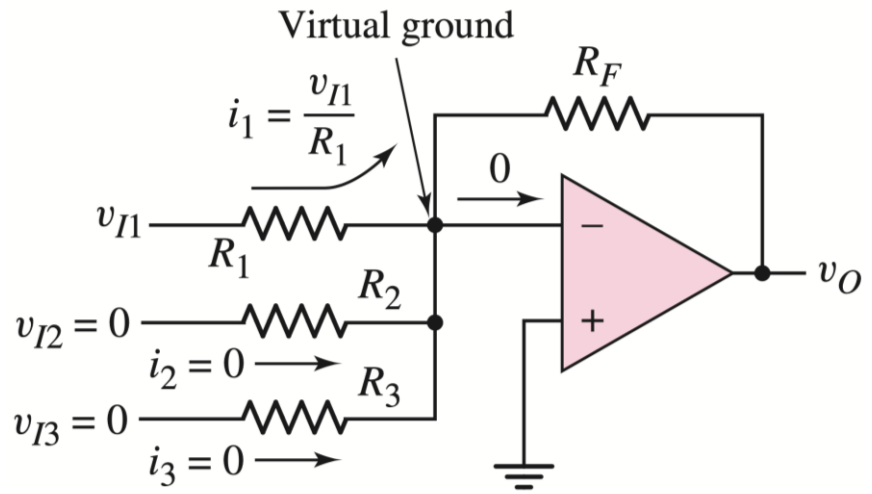
# Summing Amplifier

- The output voltage is the **sum of the three input voltages**, with different weighting factors.
- This circuit is called the **inverting summing amplifier**.



- When:

$$R_1 = R_2 = R_3 \equiv R$$

$$\Rightarrow v_O = -\frac{R_F}{R_1}(v_{I1} + v_{I2} + v_{I3})$$

# Example 3.6

(a) Design an inverting amplifier with the output voltage:  $v_O = -3(v_{I1} + 2v_{I2} + 0.3v_{I3} + 4v_{I4})$ .

Max input resistance is  $400\text{k}\Omega$ .

(b) Using (a), find  $v_O$  for:

- (i)  $v_{I1} = 0.1\text{V}$ ,  $v_{I2} = -0.2\text{V}$ ,  $v_{I3} = -1\text{V}$ ,  $v_{I4} = 0.05\text{V}$ ;
- (ii)  $v_{I1} = -0.2\text{V}$ ,  $v_{I2} = 0.3\text{V}$ ,  $v_{I3} = 1.5\text{V}$ ,  $v_{I4} = -0.1\text{V}$ .

# Example 3.6

- Answer:

(a)  $R_3 = 400\text{k}\Omega$ ,  $R_F = 360\text{k}\Omega$ ,  
 $R_1 = 120\text{k}\Omega$ ,  $R_2 = 60\text{k}\Omega$ ,  $R_4 = 30\text{k}\Omega$ ;

(b)


- (i)  $v_O = +1.2\text{V}$ ,
- (ii)  $v_O = -1.35\text{V}$

# Cascaded Op-Amp Circuits

- A cascade connection is a head-to-tail arrangement of two or more op amp circuits such that the output of one is the input of the next.
- Each circuit in the string is called a *stage*.
- The original input signal is increased by the gain of the individual stage.
- **Advantage:** Opamp circuits can be cascaded **without changing their input-output relationships** (due to the infinite input resistance and zero output resistance).

# Cascaded Op-Amp Circuits

- A three-stage cascaded connection:

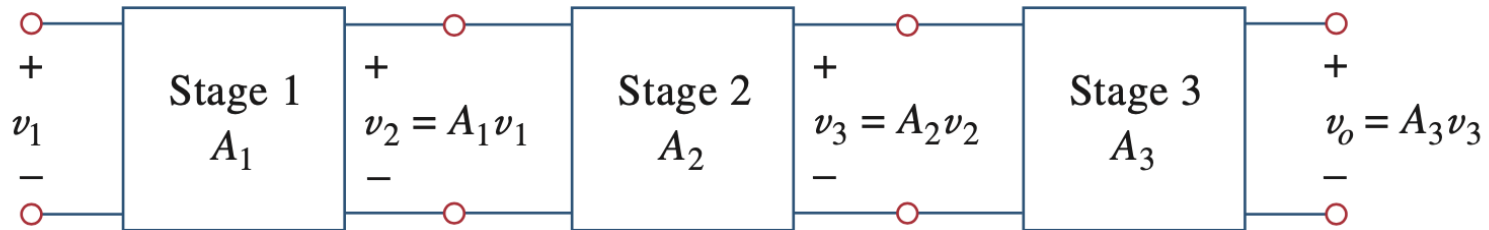

- The overall gain of the cascade connection is the product of the gains of the individual op amp circuits:


$$A = A_1 A_2 A_3$$

- The cascade connection does not affect the op amp input-output relationships.
- But, the design of an actual op-amp circuit must ensure that the load due to the next stage in the cascade does not saturate the op-amp.


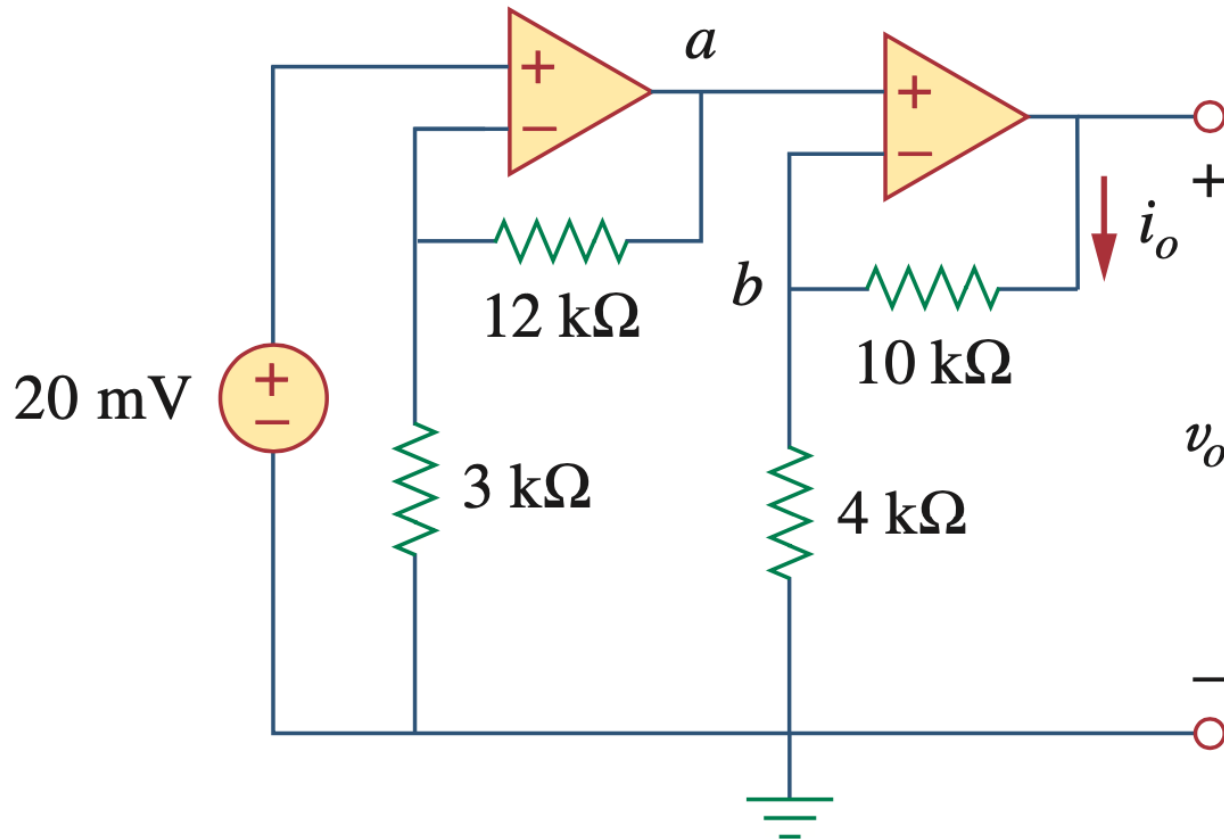
# Example 3.7

- Find  $v_o$  and  $i_o$  in the circuit:



## Example 3.7

- This circuit consists of two noninverting amplifiers cascaded.
- At the output of the first op amp:

$$v_a = \left(1 + \frac{12}{3}\right)(20) = 100 \text{ mV}$$

- At the output of the second op amp:

$$v_o = \left(1 + \frac{10}{4}\right)v_a = (1 + 2.5)100 = 350 \text{ mV}$$

## Example 3.7

- The required current  $i_o$  is the current through the 10-k $\Omega$  resistor:


$$i_o = \frac{v_o - v_b}{10} \text{ mA}$$

- But:  $v_b = v_a = 100 \text{ mV}$

- Hence:  $i_o = \frac{(350 - 100) \times 10^{-3}}{10 \times 10^3} = 25 \mu\text{A}$
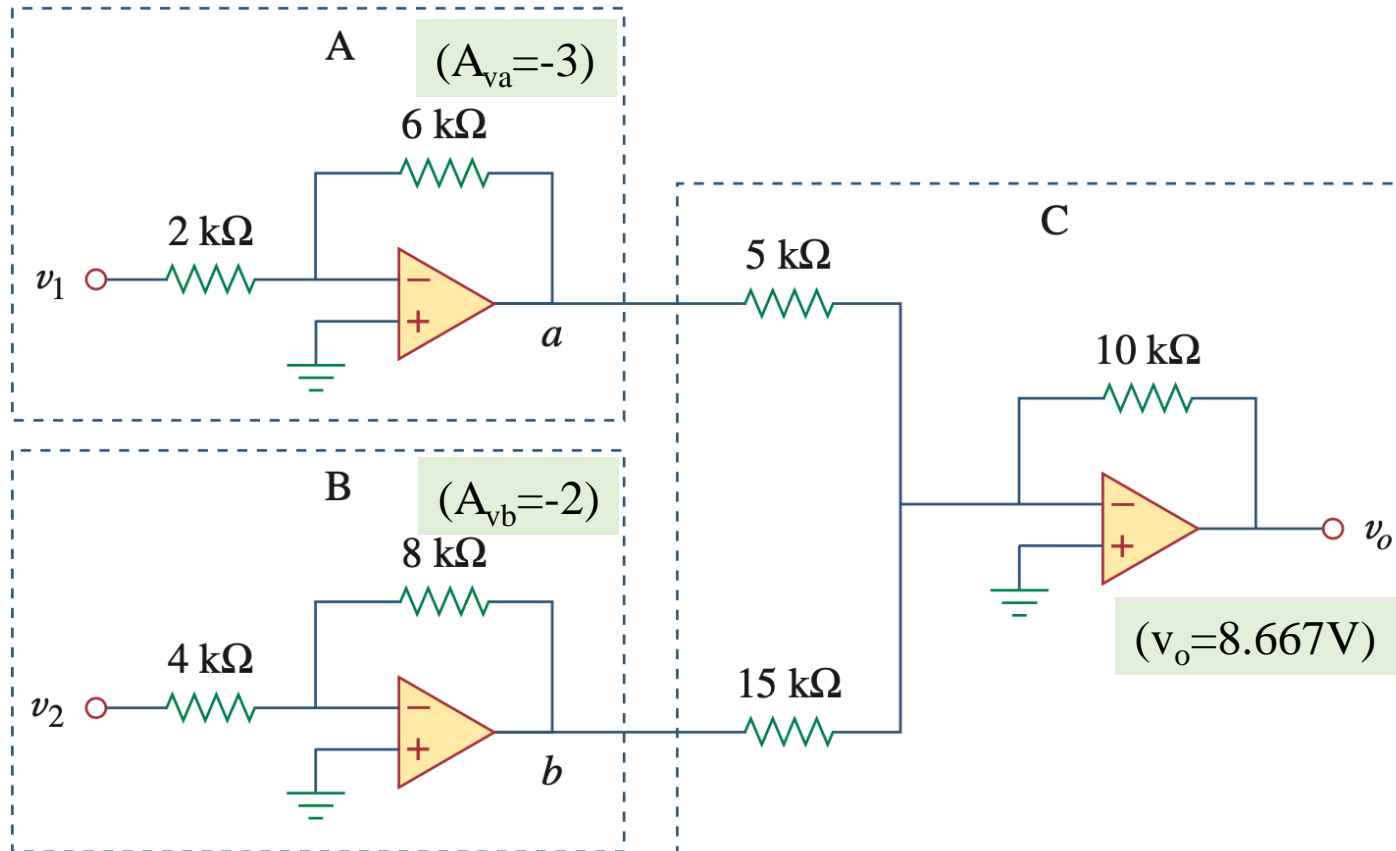
# Example 3.8

- If  $v_1 = 1\text{V}$  and  $v_2 = 2\text{V}$ , find  $v_o$  in the op-amp of the circuit.



# Example 3.8

- Gain of the first op-amp (A) = -3
- Gain of the second op-amp (B) = -2
- The output of the first (A) and second (B) op-amps:


$$v_{11} = -3v_1 = -3 \times 1 = -3 \text{ V}$$

$$v_{22} = -2v_2 = -2 \times 2 = -4 \text{ V}$$

- The output of the third op-amp (C):


$$\begin{aligned} v_o &= -(10 \text{ k}\Omega / 5 \text{ k}\Omega) v_{11} + [-(10 \text{ k}\Omega / 15 \text{ k}\Omega) v_{22}] \\ &= -2(-3) - (2/3)(-4) \\ &= 6 + 2.667 = \mathbf{8.667 \text{ V}} \end{aligned}$$

# Summary of Basic Op-amp Circuits

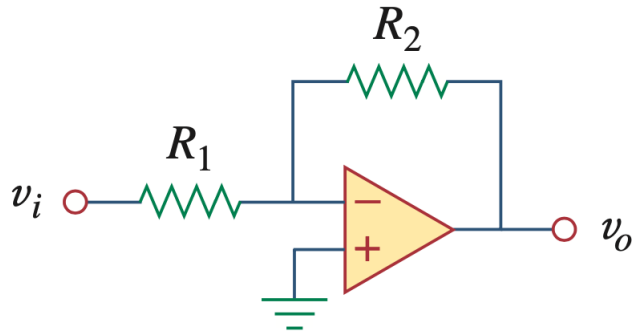


Inverting Amplifier

$$v_o = -\frac{R_2}{R_1}v_i$$

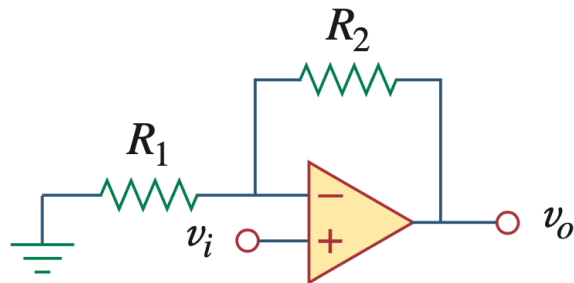

Noninverting Amplifier
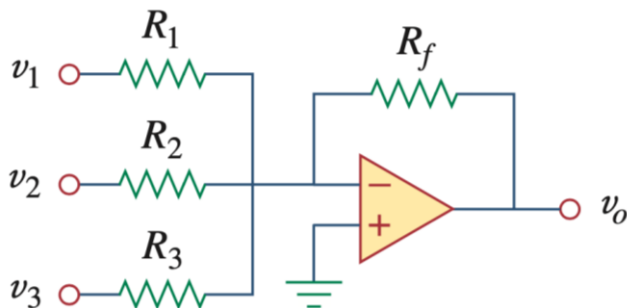
$$v_o = \left(1 + \frac{R_2}{R_1}\right)v_i$$



Summing Amplifier (Summer)

$$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$$