

Lab 2. CURRENT AND VOLTAGE IN A CIRCUIT

1. Notice

- Students must pay attention and follow all the regulations.
- Be careful with all devices.
- Check the functionalities of all components, wires, and boards.
- **Investigate and use a multimeter together with other devices carefully. If you make any of them broken, get punished immediately.**

2. Goals

- Verify Ohm's law and Kirchhoff's law of current and voltage in a circuit.
- Investigate the relationship between current and voltage in a circuit.

3. Exercises

Exercise 1. Investigate the current and voltage properties of a circuit in Figure 1 by utilizing Ohm's law, with $R_1 = 10\text{ k}\Omega$, $R_2 = 1\text{ k}\Omega$, $R_3 = 10\text{ k}\Omega$, $R_4 = 1\text{ k}\Omega$, $R_5 = 330\text{ }\Omega$, $V_s = 5\text{ V}$.

Requirements:

- Compute the current and voltage for each resistor theoretically.
- Implement the equivalent circuit in a board. Verify the implemented circuit carefully before setting the power supply $V_s = 5\text{ V}$.
- Using a multimeter to measure the current and voltage dropped across each resistor. Measure twice and record the corresponding values. Compare the numerical and theoretical results, then draw some main observations and conclusions.

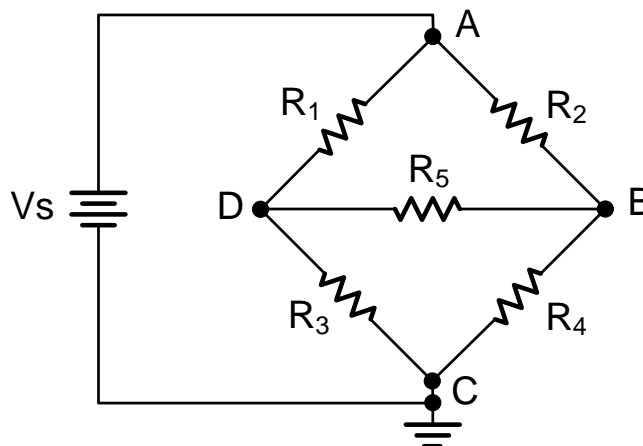


Figure 1. The considered circuit to investigate Ohm's law

Exercise 2. Investigate the current and voltage properties of the circuit in Figure 2 by utilizing the Kirchhoff's laws, with $R_1 = 1\text{ k}\Omega$, $R_2 = 330\text{ }\Omega$, $R_3 = 1\text{ k}\Omega$, $R_4 = 330\text{ }\Omega$, $R_5 = 10\text{ k}\Omega$, $R_6 = 1\text{ k}\Omega$, $R_7 = 330\text{ }\Omega$, $R_8 = 330\text{ }\Omega$, $V_s = 5\text{ V}$.

Requirements:

- Implement the equivalent circuit on a board. Verify the implemented circuit carefully before setting the power supply $V_s = 5V$.
- Investigate Kirchhoff's law on the current at the nodes A, B, C, D, E. Use a multimeter to measure the current at all the nodes. Record the results in a table.
- Investigate Kirchhoff's law on the voltage for the circuits V_1 , V_2 , V_3 , V_4 . Use a multimeter to measure the voltage dropped across each resistor and record the results in a table.

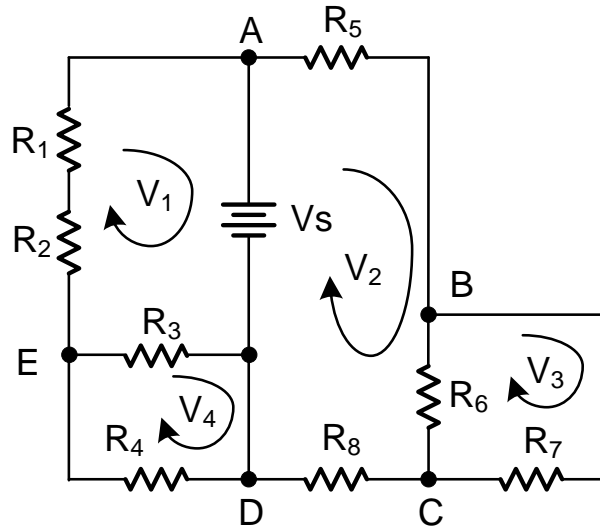


Figure 2. The considered circuit to investigate Kirchhoff's laws

Components and devices needed for the lab:

Component	Description	Amount
Resistor	330 Ω /1 k Ω /10 k Ω	5/5/3
DC Voltage	5-12V	1
Circuit board		1
Wires		Few
Multimeter		1