

LAB 3: RC FILTER AND SERIES RLC CIRCUIT

1. Goals

- Design, implement, and investigate the properties of RC filters.
- Design, simulate, and investigate the properties of a series RLC circuit.

2. Exercises

Exercise 1. Investigate a lowpass filter and a highpass filter with R, C components as shown in Figure 1. The cut-off frequency of both filters are determined by: $f_0 = \frac{1}{2\pi RC}$.

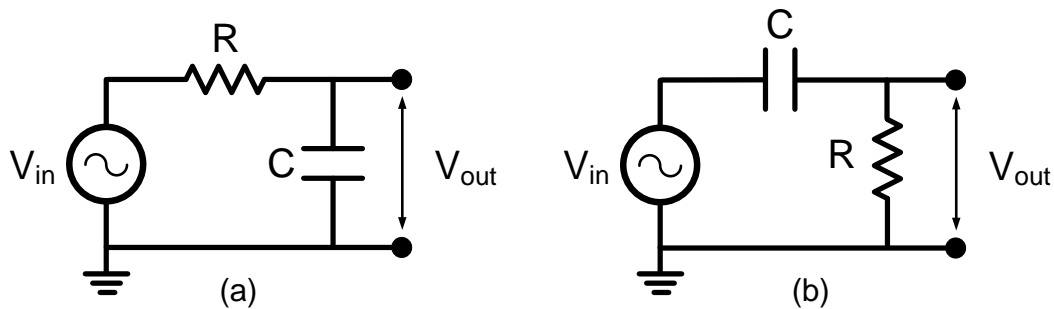


Figure 1. (a) Lowpass filter and (b) highpass filter.

Requirements:

a) Follow the steps below to investigate a lowpass RC filter:

- Use the components given in the table to assemble the lowpass RC filter (Fig. 1(a)) on a breadboard.
- Measure the real values of the resistor and capacitor used in the filter. Compare the measured values with the label value of each component.
- Use a function generator to produce V_{in} (input voltage) for the circuit.
- Use an oscilloscope to display V_{in} and V_{out} (output voltage).
- Set $V_{in} = 5V$ (peak value) and its frequency = 1 kHz. Measure and record the amplitude of V_{out} .
- Keep the amplitude of V_{in} fixed. Vary the frequency of V_{in} over a wide range (e.g., 1Hz, 10 Hz, 100 Hz, 10 kHz, 100 kHz). Measure and record the amplitude V_{out} . Comment on the obtained results. **Notice:** You may use the button on the function generator to make sure that $V_{in} = 5V$.
- Based on the obtained value of V_{out} corresponding to each frequency of V_{in} , plot the frequency response of the lowpass RC filter, with the vertical axis (y-axis) being the *gain* and the horizontal axis (x-axis) being the *frequency* (measured in dB).
- Find the frequency of V_{in} at which $\frac{\text{Amplitude of } V_{out}}{\text{Amplitude of } V_{in}} = \frac{1}{\sqrt{2}} = 0.707$. Compare this frequency value with the cut-off frequency calculated by $f_0 = \frac{1}{2\pi RC}$. Draw a conclusion.

- For a lowpass RC filter, the phase difference (or phase shift) between V_{out} and V_{in} is calculated by $\varphi = -\arctan(2\pi fRC)$. At the cut-off frequency (such that $\frac{\text{Amplitude of } V_{out}}{\text{Amplitude of } V_{in}} = \frac{1}{\sqrt{2}} = 0.707$), use the oscilloscope to display the phase difference φ ($\varphi = -\frac{\Delta t}{T} \times 360^\circ$). Comment on the obtained results.
- b) Investigate a highpass RC filter as shown in Fig. 1(b) by repeating the same above steps (which have been done for investigating a lowpass RC filter).

Exercise 2. Use Multisim Live or other open-source circuit simulators to investigate the properties of a series RLC circuit. (**Note:** Students can assemble the circuit on a breadboard and then investigate it.)

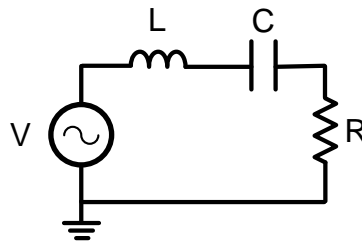


Figure 2. Series RLC circuit.

Requirements:

- Implement the circuit as shown in Figure 2 with $R = 330 \Omega$, $L = 10 \text{ mH}$, $C = 100 \mu\text{F}$, $V = 5\cos(2\pi 60t) \text{ (V)}$.
- Find the phase difference between V_R , V_L , V_C and V . Compare the simulation results with the theoretical calculation. Draw a conclusion.
- Vary the frequency of the V (1 Hz~10 kHz) to find the resonant frequency (f_{MAX}) of the series RLC circuit (Note: V_R is maximum at f_{MAX}). Compare the simulation results with the theoretical calculation ($f_{MAX} = \frac{1}{2\pi\sqrt{LC}}$). Draw a conclusion.

Components and devices for exercises:

| Components & Devices | Description | Amount |
|----------------------|--|--------|
| Ceramic Capacitor | 223(0.022 μF), 104(0.1 μF), 106(10 μF) | 1/1/1 |
| Inductor | 10 mH | 1 |
| Resistor | 1 k Ω , 5 k Ω , 10 k Ω , 47 k Ω | 1/1 |
| Oscilloscope | OWON SDS1102 | 1 |
| Function generator | UNI-T UTC962E | 1 |
| Power Supply | Aditeg PS-3030DD | 1 |
| Breadboard | | 1 |
| Wires | | Few |
| Multimeter | | 1 |